

# ALU & FSM

## Discussion 7

Huizhe Su

# Content




- Combinatorial Logic
  - Arithmetic and Logic Unit (ALU)
  - Logics & Circuits
- Sequential Logic
  - Timing Diagram
  - Time Calculation
- FSM

# Combinatorial Logic

# Arithmetic and Logic Unit (ALU)
   
## Combinatorial Logic


- Arithmetic and logic operations
- Simple example:
  - Input: A, B (32-bit input)
  - Control: S (2-bit input)
  - Output: R (32-bit output)
- Functions:
  - $R = A + B$ , when  $S = 00$
  - $R = A - B$ , when  $S = 01$
  - $R = A \text{ AND } B$ , when  $S = 10$
  - $R = A \text{ OR } B$ , when  $S = 11$



# RISC-V ALU

## Combinatorial Logic

- ALUSrc
- ALUOp/ALU control
- Zero

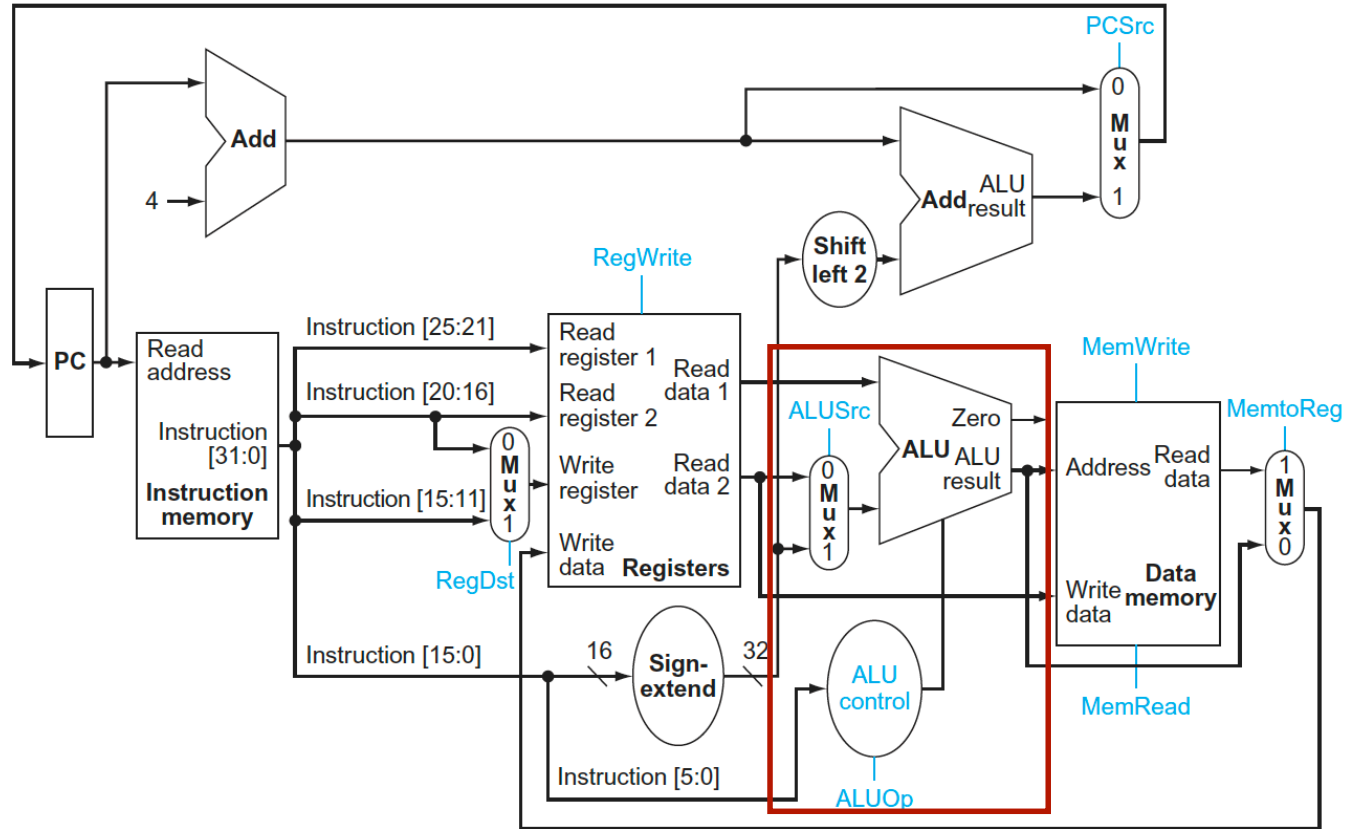

# Logics & Circuits


## Combinatorial Logic

- Basic things you need to know:
  - The name of each logic gate
  - Write the boolean expression directly from the circuits
  - Simplify the circuits (by boolean expression or truth table)
  - Draw the circuit from the given boolean expression

# Logics & Circuits - Example

## Combinatorial Logic

 - (a) The circuit shown below can be simplified. Please **write** down the boolean expression that exactly corresponds to the circuit shown (no simplification). Then simplify this prepossession step by step, applying one rule at a time. Then **draw** the circuit according to the simplified boolean expression using the minimum number of **one-** or **two-input** logic gates.




# Logics & Circuits - Solution

## Combinatorial Logic

Solution:

$$\begin{aligned}\overline{A\overline{B}C} + (A + \overline{B})(\overline{C}\overline{D}) &= \overline{A} + B + \overline{C} + (A + \overline{B})(\overline{C} + \overline{D}) \\ &= \overline{A} + B + \overline{C} + A\overline{C} + A\overline{D} + \overline{B}\overline{C} + \overline{B}\overline{D} \\ &= \overline{A} + B + \overline{C} + A\overline{D} + \overline{B}\overline{D} \\ &= \overline{A} + B + \overline{C} + \overline{D}\end{aligned}$$

One possible circuit:

 



# Karnaugh map (not covered in lecture)

## Combinatorial Logic

### Karnaugh Maps

CD \ AB	00	01	11	10
	00	01	11	10
00			1	1
01		1		1
11	1	1	1	1
10	1	1	1	1

$$F = C + AD' + A'B'C'D + AB'C$$

# Sequence Logic


# Timing diagram

## Sequential Logic

- Sequential Logic can remember their inputs even after the inputs change
- State changes are synchronized by clock.
- Some terminology:
  - Clk-to-q: ( $t_{prop}$ ) is the time for a signal to propagate through a flip-flop.
  - Propagation delay: ( $t_{combinational}$ ) is the longest delay for any combinational logic (which by definition is surrounded by two flip-flop)
  - Setup time: ( $t_{setup}$ ) is the time before the rising clock edge that the input to a flip-flop must be valid.
  - Hold time: The minimum time during which the input must be valid after the clock edge.

# Timing diagram

## Sequential Logic



 


# Timing diagram - example

# Sequential Logic

## 10. SDS

  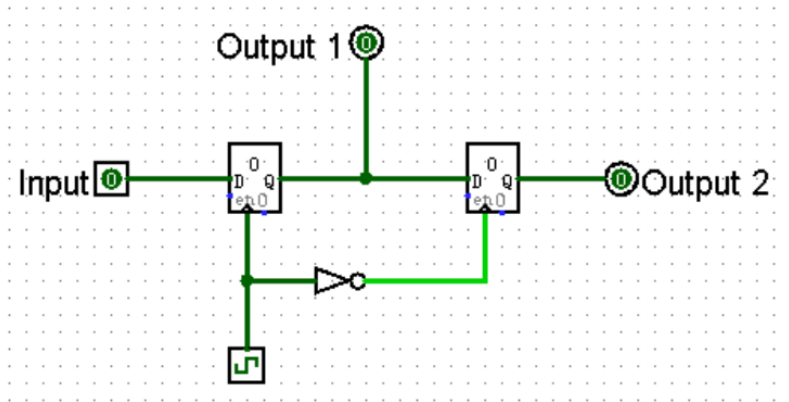- (a) Draw the Timing Diagram for the circuit below. NOT gates have a 2 ns propagation delay. For each register, the clk-to-q delay is 2 ns and setup time is 2 ns. The clock period is 8 ns, and each grid in the following diagram is a unit of 1 ns. The initial values of clock and output are given in the diagram. Use any of the two empty graphs to put in your answer (so you can re-do it). Clearly **mark your final answer** if you use more than one graph!





# Time Calculation


## Sequential Logic

- (Setup time violation) In a SDS, a system the clock period (or cycle time) must be at least as large as

$$t_{\text{prop}} + t_{\text{combinational}} + t_{\text{setup}}$$

- (Hold time violation) In a feedback SDS (circuits contain register to register propagation), the hold time must not exceed:

 
$$t_{\text{prop}} + t_{\text{combinational}}$$



# Time Calculation - example
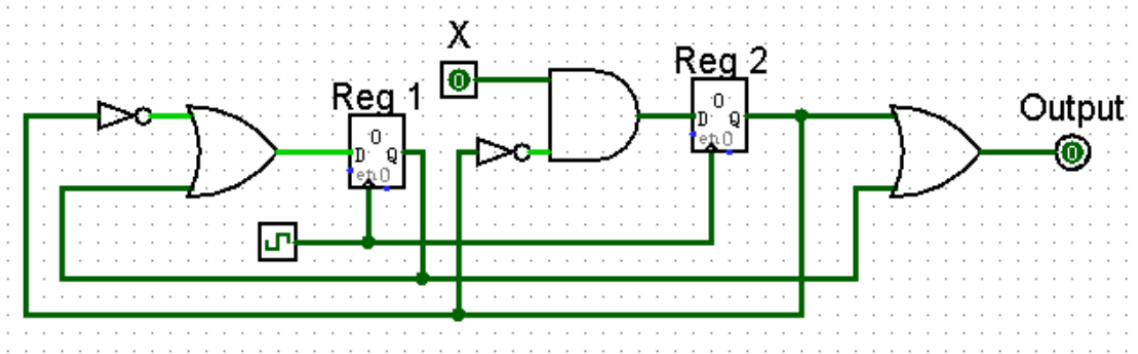
## Sequential Logic

Consider the following circuit. Assume the clock has a frequency of 50 MHz, all gates have a propagation delay of 6 ns, X changes 10 ns after the rising edge of clk, Reg1 and Reg2 have a clk-to-q delay of 1 ns.



- What is the longest possible setup time such that there is no setup time violations?
- What is the longest possible hold time such that there is no hold time violations?



# Time Calculation - solution

## Sequential Logic

### Solution:

The clock period is  $\frac{1}{50 \times 10^6} s = 20 \text{ ns}$ .

Reg1 longest possible setup time: the path is *the output of Reg2*  $\rightarrow$  NOT  $\rightarrow$  OR, with a delay of  $1 \text{ ns} + 6 \text{ ns} + 6 \text{ ns} = 13 \text{ ns}$ . So  $20 - 13 = 7 \text{ ns}$ .

Reg2 longest possible setup time: the path is *X changes*  $\rightarrow$  AND, with a delay of  $10 \text{ ns} + 6 \text{ ns} = 16 \text{ ns}$ . So  $20 - 16 = 4 \text{ ns}$ .


**So longest setup time:  $\min(7 \text{ ns}, 4 \text{ ns}) = 4 \text{ ns}$ .**

Reg1 longest possible hold time: the path is *the output of Reg1*  $\rightarrow$  OR, with a delay of  $1 \text{ ns} + 6 \text{ ns} = 7 \text{ ns}$ .

Reg2 longest possible hold time: the path is *the output of Reg2*  $\rightarrow$  NOT  $\rightarrow$  AND, with a delay of  $1 \text{ ns} + 6 \text{ ns} + 6 \text{ ns} = 13 \text{ ns}$ .

 **So longest hold time:  $\min(7 \text{ ns}, 13 \text{ ns}) = 7 \text{ ns}$ .**

Consider the following circuit. Assume the clock has a frequency of 50 MHz, all gates have a propagation delay of 6 ns, X changes 10 ns after the rising edge of clk, Reg1 and Reg2 have a clk-to-q delay of 1 ns.



FSM


# FSM

## FSM

- A convenient way to conceptualize computation over time
- Start at a state, given an input, follow some edge to another
- With combinational logic and registers, any FSM can be implemented in hardware
- edge: input/output

# Example 1


## FSM

 

state bit1	state bit0	input	next state bit1	next state bit0	output
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

# Example 1 - solution

## FSM

 


### Solution:

state bit1	state bit0	Input	next state bit1	next state bit0	Output
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	1

# Example 2


## FSM

 

- Given input: 0100101010
- What is the output? What does this FSM describe (when it outputs 1)?

# Example 2 - solution

## FSM

 

- Given input: 0100101010
- What is the output?
- Output: 0000001010
- Whenever the FSM receives 101

# Example 3

## FSM

- Draw a FSM that outputs 1 when it receives two or more successive '0'.





# Example 3 - solution

## FSM

- Draw a FSM that outputs 1 when it receives two or more successive '0'.

Solution:

