

Course Info

- Lab 5 will be released, get yourself prepared before going to lab sessions! (FSM preview, FSM background knowledge not a must, just use sum of minterm/Karnaugh map)
- Project 1.1! Start early! Do not waste your slip days (CS110P)! DDL March 13th.
- Project 1.2 will be available this week, and will be marked in lab sessions. Deadline March 31th.
- HW3 ddl March 18th.
- Next week discussion on synchronized digital system (SDS)



信息科学与技术学院

School of Information Science and Technology

CS 110

Computer Architecture

Combinational & Sequential Circuits

Instructors:

Siting Liu & Chundong Wang


Course website: [https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/
Spring-2023/index.html](https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2023/index.html)

School of Information Science and Technology (SIST)

ShanghaiTech University

2023/3/5


Where are we?

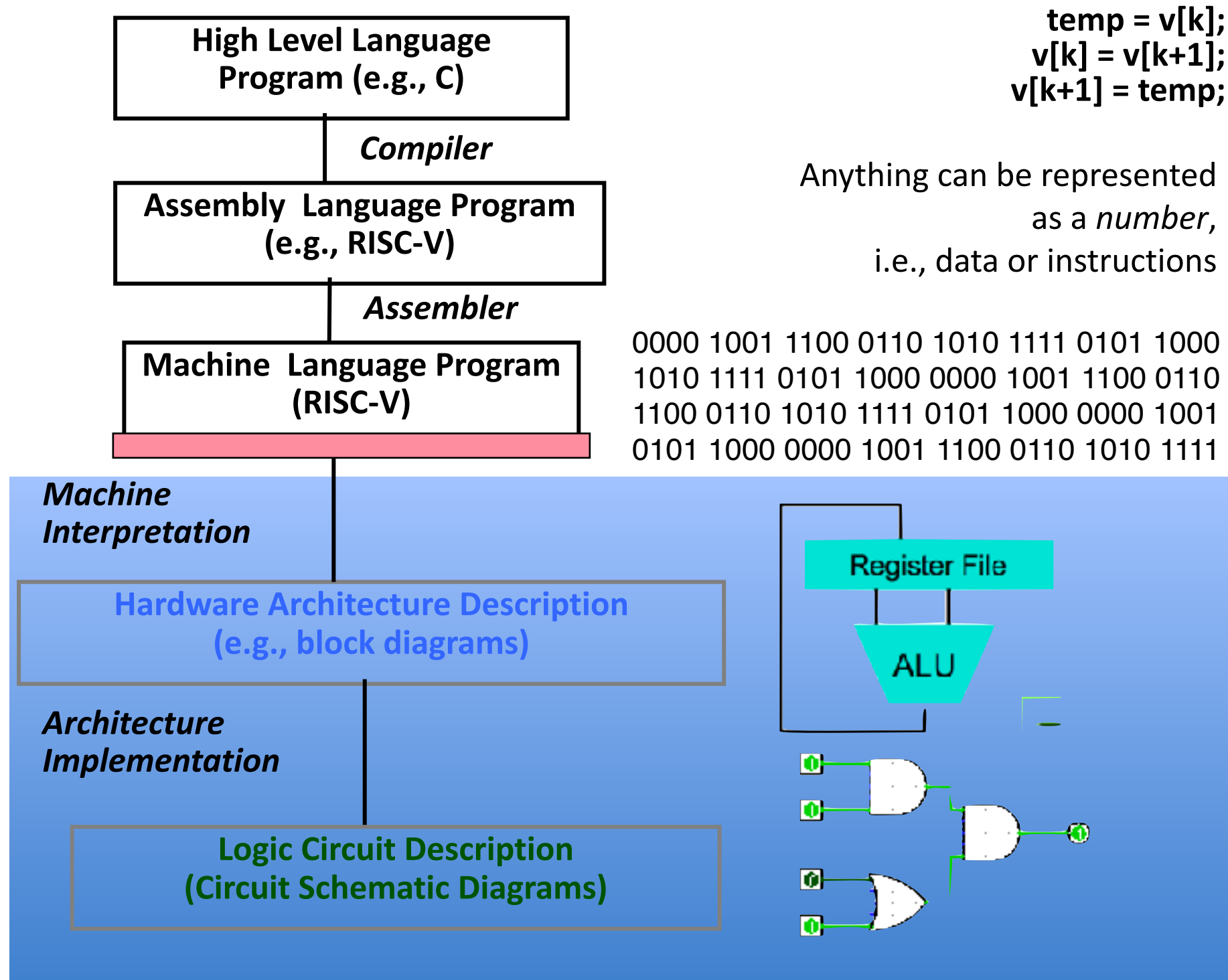

Basic Symbols

- Standard symbols for logic gates

– Buffer, NOT

 

- Universal sets

– NOT, AND, OR

Can be combined to implement any logics

– AND, NAND



– NAND

– OR, NOR



– NOR

Through Boolean algebra!

Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
- Step 1: Write down truth table of the desired logic

For example build an XOR
with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
 - Step 2: Pick the lines with 1 as the output; write them down in *Sum of Minterms (Product)* form;

For example build an XOR
with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Minterms

$\bar{A}\bar{B}$	m_0
$\bar{A}B$	m_1
$A\bar{B}$	m_2
AB	m_3

Build Combinational Circuits with Basic Logic Gates

- Combinational circuits: the ones that the output of the digital circuits depends solely on its inputs; usually built with logic gates without feedback
- Step 3: Simplify using Laws of Boolean algebra;

For example build an XOR
with AND/OR/NOT

A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Your turn!

- Build a half adder:

	Sum	Carry
• $0 + 0 = 0$	0	
• $0 + 1 = 1$	1	0
• $1 + 0 = 1$	1	0
• $1 + 1 = 0$	0	1

- Build a 2-bit adder:

	Sum	Carry
• $00 + 00 = 00$	00	0
• $00 + 01 = 01$	01	0
• $00 + 10 = 10$	10	0
• $00 + 11 = 11$	11	0
• $01 + 00 = 01$	01	0
• $01 + 01 = 10$	10	0
• $01 + 10 = 11$	11	0
• $01 + 11 = 00$	00	1

AB CD

	Sum	Carry
• $10 + 00 = 10$	10	0
• $10 + 01 = 11$	11	0
• $10 + 10 = 00$	00	1
• $10 + 11 = 01$	01	1
• $11 + 00 = 11$	11	0
• $11 + 01 = 00$	00	1
• $11 + 10 = 01$	01	1
• $11 + 11 = 10$	10	1

Another Simplification Method —Karnaugh Map


		A B		Gray coded	
		00	01	11	10
CD	00				
	01			1	
	11		1	1	1
	10			1	1

Gray coded

Each cell corresponds to a minterm

Online Karnaugh map solver: <http://www.32x8.com/index.html>

Representations of Combinational Logic

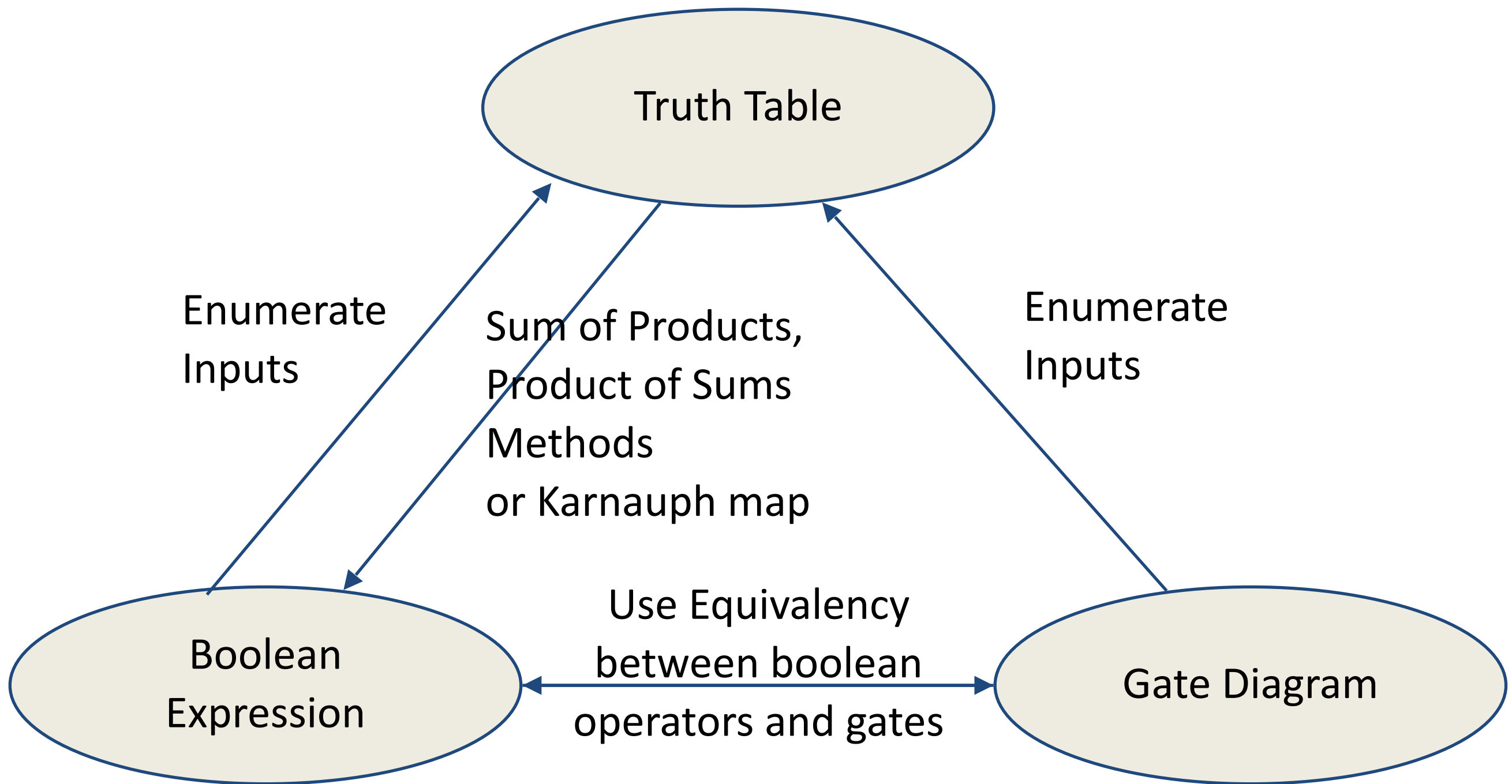


Build Larger Blocks—like LEGO®

$$\begin{array}{r} 01010101 \\ + \underline{01110011} \end{array}$$


- Build a full adder (FA): truth table

Carry in	A	B	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Other Useful Combinational Circuits

- Multiplexer (2-to-1)

 

- Multiplexer (2^n -to-1)

 


Tree structure

Timing Diagram—Signal & Waveform



Transistors:
non-ideal
switches

 

Timing Diagram—Signal Grouping



A

a₀

a₁

a₂

b₀

b₁

b₂

O₀

O₁

O₂

O



Build an ALU

Instructions are Abstract of Hardware

imm[31:12]				rd	0110111	LUI
imm[31:12]				rd	0010111	AUIPC
imm[20 10:1 11 19:12]				rd	1101111	JAL
imm[11:0]		rs1	000	rd	1100111	JALR
imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011	BNE
imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011	BLT
imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011	BGE
imm[12 10:5]	rs2	rs1	110	imm[4:1 11]	1100011	BLTU
imm[12 10:5]	rs2	rs1	111	imm[4:1 11]	1100011	BGEU
imm[11:0]		rs1	000	rd	0000011	LB
imm[11:0]		rs1	001	rd	0000011	LH
imm[11:0]		rs1	010	rd	0000011	LW
imm[11:0]		rs1	100	rd	0000011	LBU
imm[11:0]		rs1	101	rd	0000011	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	SB
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW
imm[11:0]		rs1	000	rd	0010011	ADDI
imm[11:0]		rs1	010	rd	0010011	SLTI
imm[11:0]		rs1	011	rd	0010011	SLTIU
imm[11:0]		rs1	100	rd	0010011	XORI
imm[11:0]		rs1	110	rd	0010011	ORI
imm[11:0]		rs1	111	rd	0010011	ANDI



Instructions are Abstract of Hardware

0000000	shamt	rs1	001	rd	0010011	SLLI	
0000000	shamt	rs1	101	rd	0010011	SRLI	
0100000	shamt	rs1	101	rd	0010011	SRAI	
0000000	rs2	rs1	000	rd	0110011	ADD	
0100000	rs2	rs1	000	rd	0110011	SUB	
0000000	rs2	rs1	001	rd	0110011	SLL	
0000000	rs2	rs1	010	rd	0110011	SLT	
0000000	rs2	rs1	011	rd	0110011	SLTU	
0000000	rs2	rs1	100	rd	0110011	XOR	
0000000	rs2	rs1	101	rd	0110011	SRL	
0100000	rs2	rs1	101	rd	0110011	SRA	
0000000	rs2	rs1	110	rd	0110011	OR	
0000000	rs2	rs1	111	rd	0110011	AND	
0000	pred	succ	00000	000	00000	0001111	FENCE
0000	0000	0000	00000	001	00000	0001111	FENCE.I
0000000000000			00000	000	00000	1110011	ECALL
0000000000001			00000	000	00000	1110011	EBREAK
csr	rs		d		1110011	CSRRW	
csr	rs		d		1110011	CSRRS	
csr	rs		d		1110011	CSRRC	
csr	zimm		101	rd	1110011	CSRRWI	
csr	zimm		110	rd	1110011	CSRRSI	
csr	zimm		111	rd	1110011	CSRRCI	


Not in CS110

An Arithmetic & Logic Unit (ALU)

 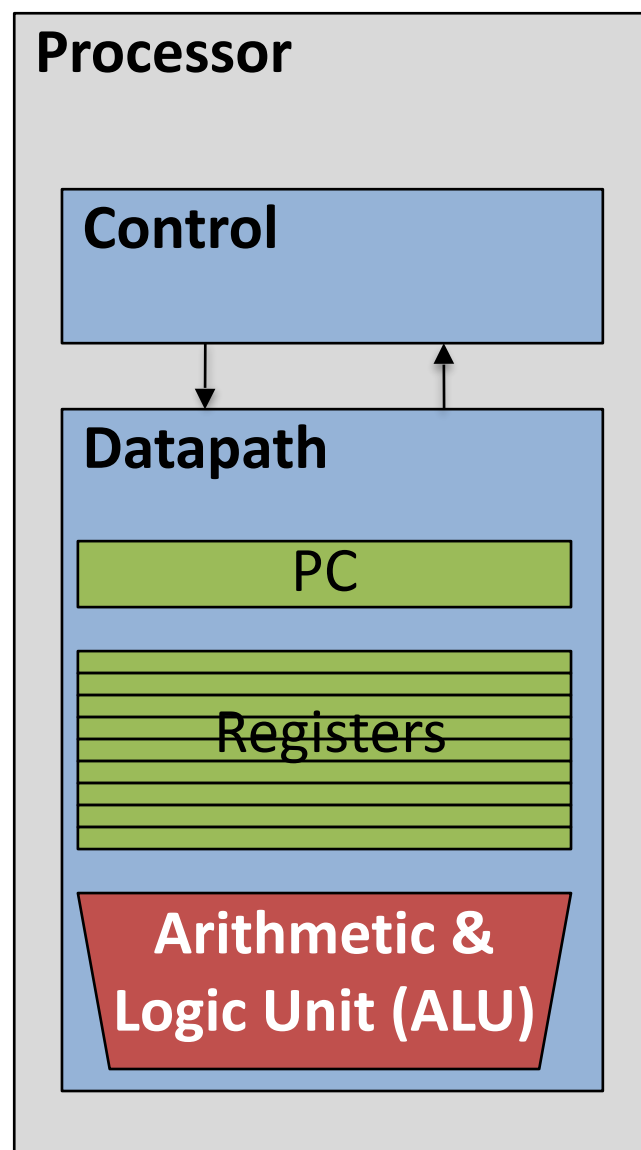- Arithmetic: Add/Sub/Addi
- Logic: **And**/Or/Xor(i) (bit-wise)





Or/Xor similar

 

An Arithmetic & Logic Unit (ALU)


 
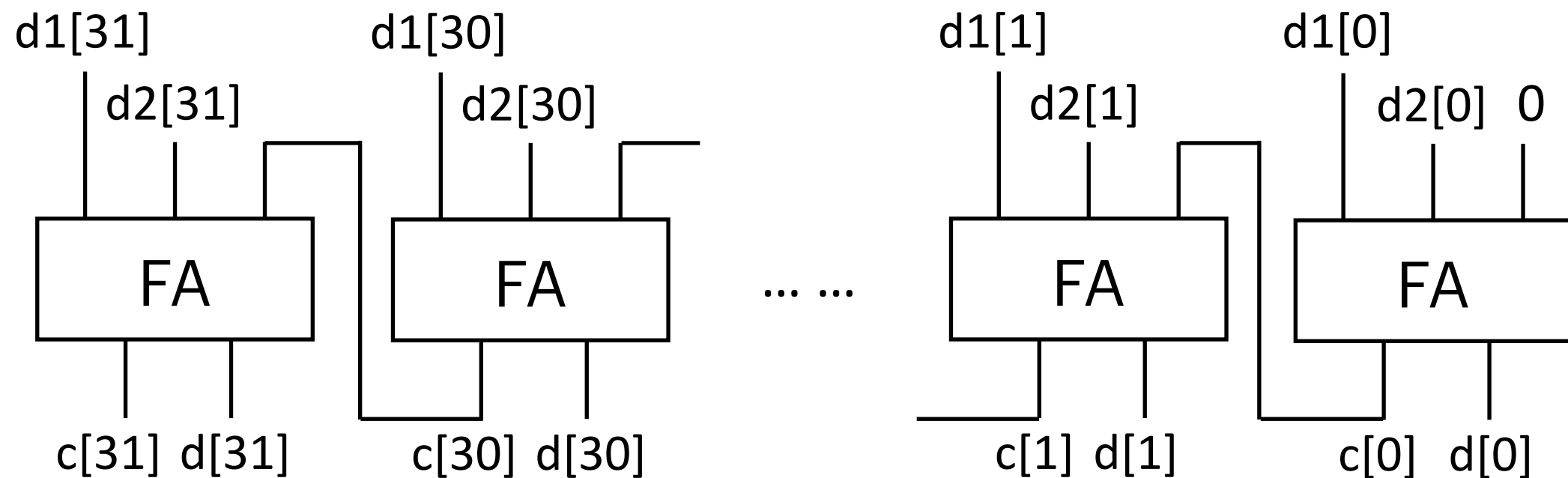
- Arithmetic: **Add**/Sub/**Addi**
- Logic: And/Or/Xor(i) (bit-wise)



An Arithmetic & Logic Unit (ALU)

- Arithmetic: Add/**Sub**/Addi
- Logic: And/Or/Xor(i) (bit-wise)

 
 
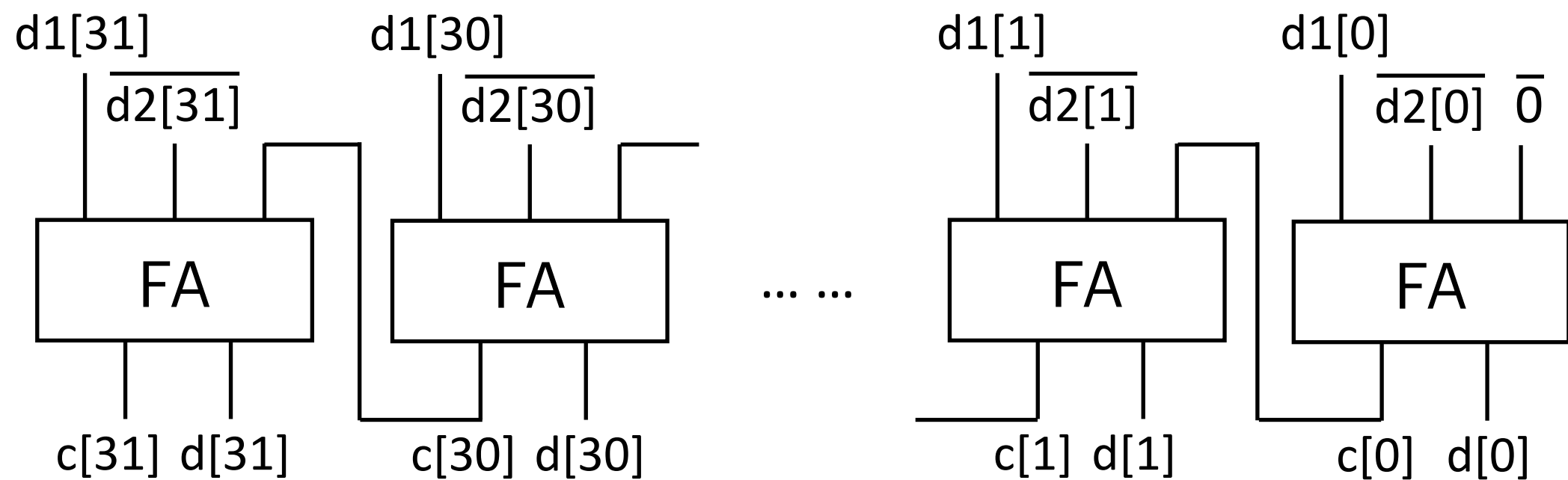
$$A - B = A + (-B) = A + \bar{B} + 1 \pmod{2^{N-1}}$$



An Arithmetic & Logic Unit (ALU)


- Arithmetic: Add/**Sub**/Addi
- Logic: And/Or/Xor(i) (bit-wise)
  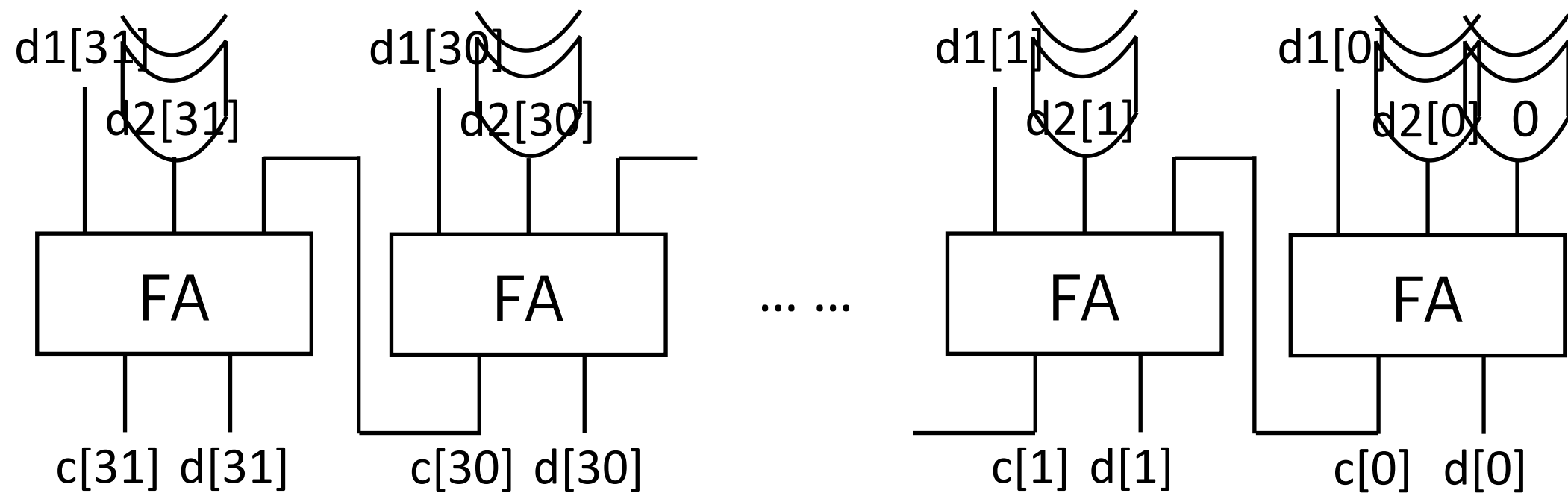
$$A - B = A + (-B) = A + \bar{B} + 1 \pmod{2^{N-1}}$$




An Arithmetic & Logic Unit (ALU)

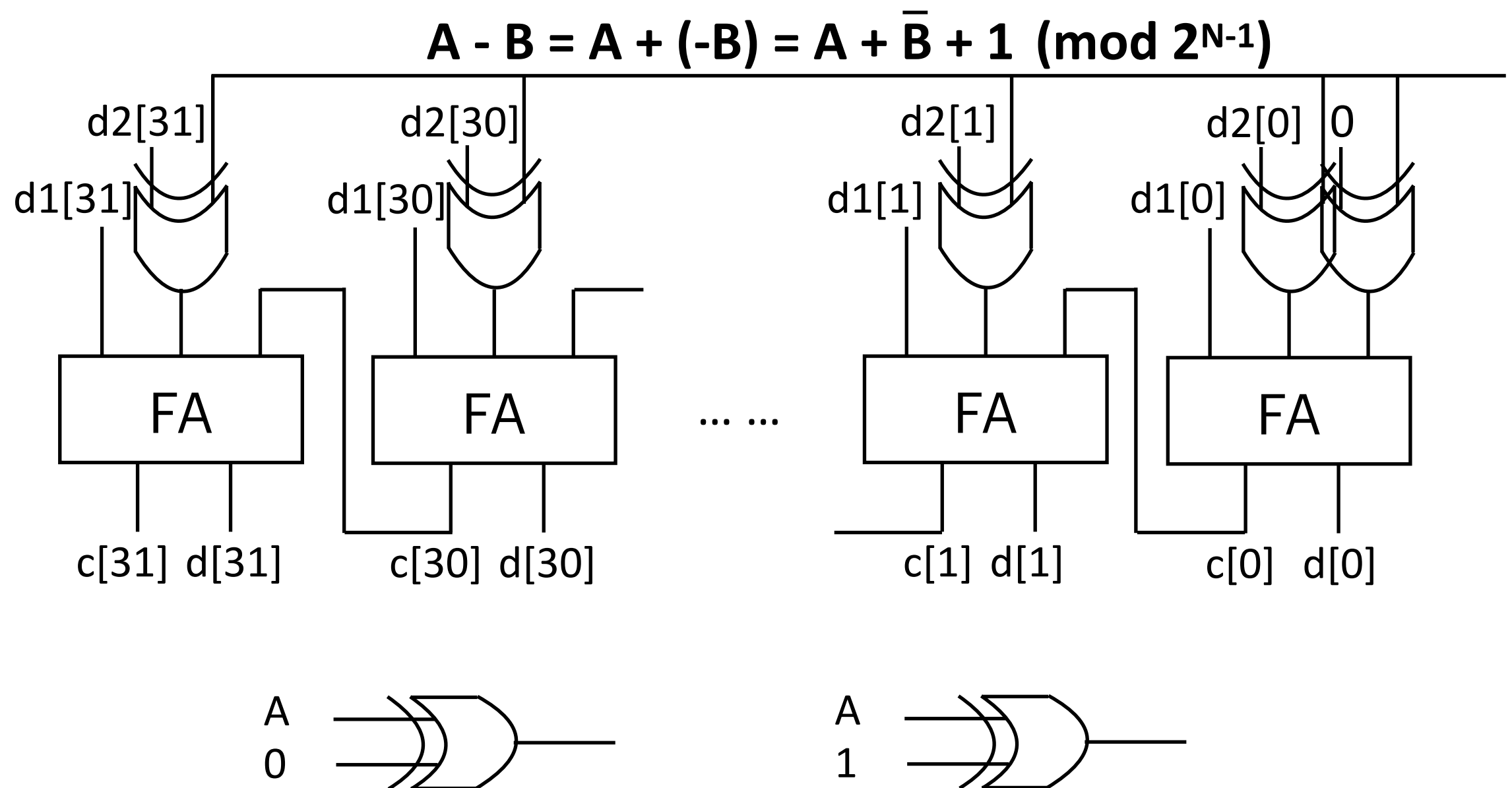- Arithmetic: Add/**Sub**/Addi
- Logic: And/Or/Xor(i) (bit-wise)




An Arithmetic & Logic Unit (ALU)

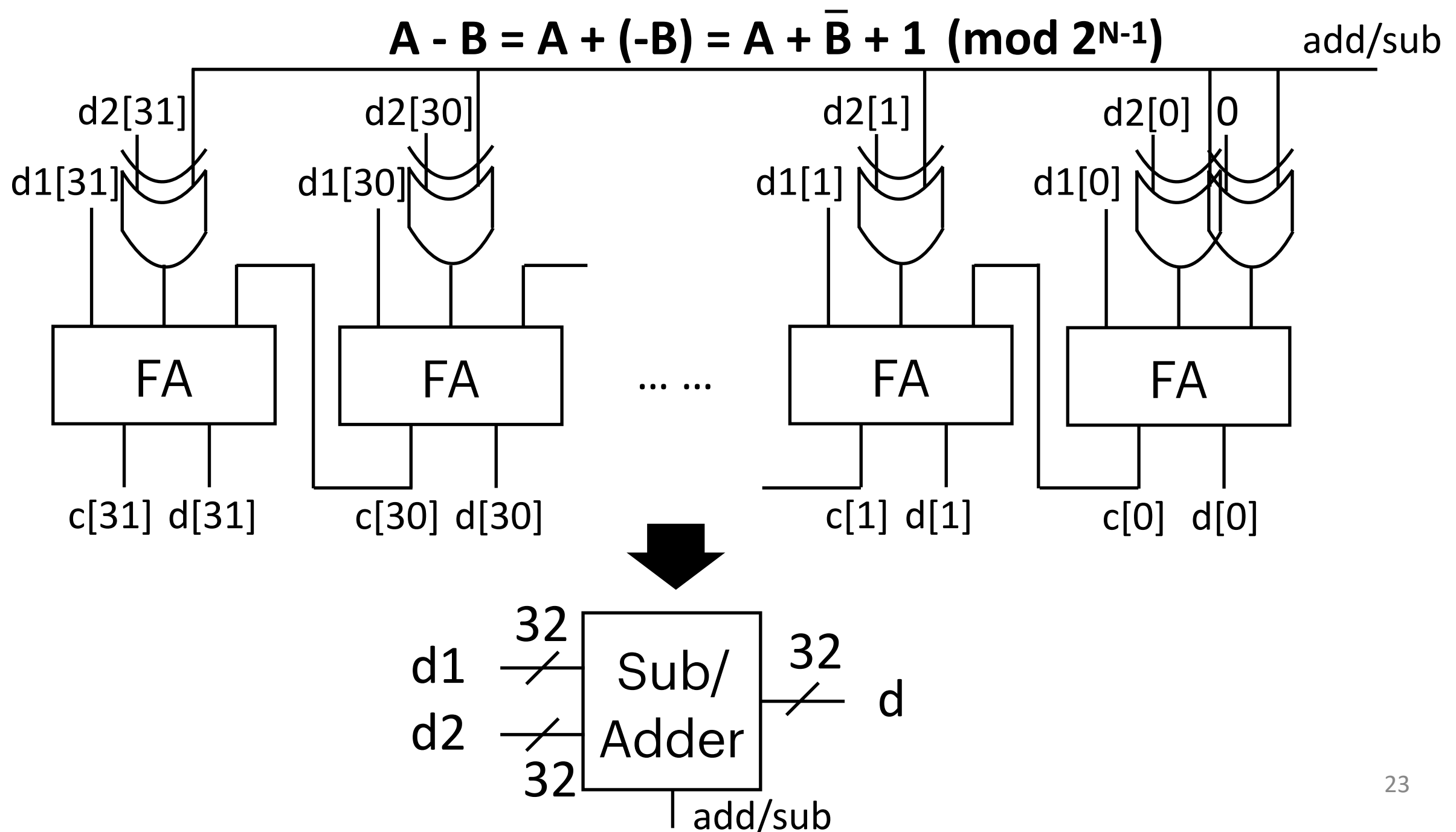- Arithmetic: Add/**Sub**/Addi
- Logic: And/Or/Xor(i) (bit-wise)




An Arithmetic & Logic Unit (ALU)

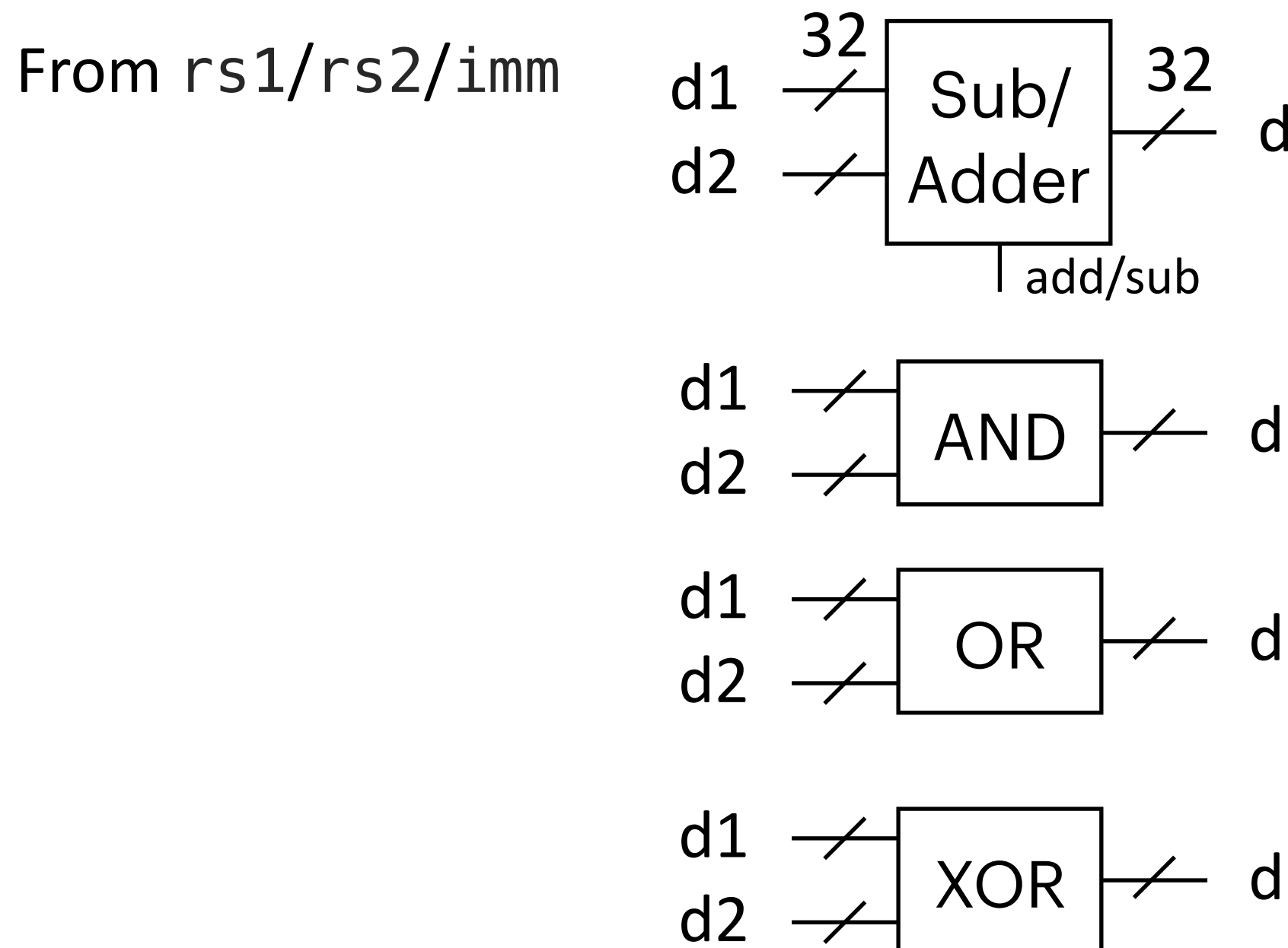- Arithmetic: Add/Sub/Addi
- Logic: And/Or/Xor(i) (bit-wise)



An Arithmetic & Logic Unit (ALU)

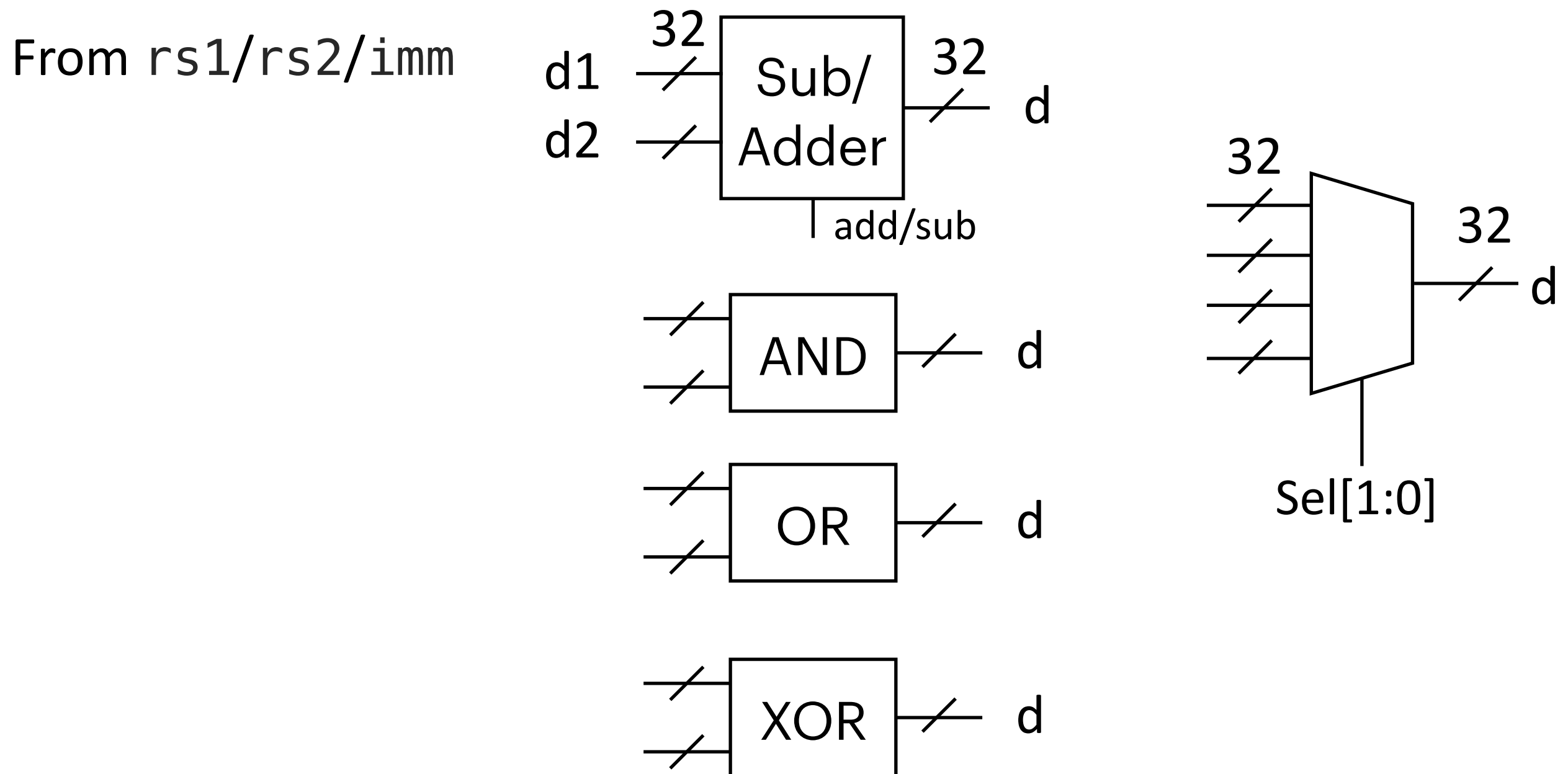- Arithmetic: Add/Sub/Addi
- Logic: And/Or/Xor(i) (bit-wise)




Recall: RISC-V Instruction Format

00000000	rs2	rs1	000	rd	0110011	ADD
01000000	rs2	rs1	000	rd	0110011	SUB
00000000	rs2	rs1	100	rd	0110011	XOR
00000000	rs2	rs1	110	rd	0110011	OR
00000000	rs2	rs1	111	rd	0110011	AND

imm	rs1	000	rd	0010011	ADDI
imm	rs1	100	rd	0010011	XORI
imm	rs1	110	rd	0010011	ORI
imm	rs1	111	rd	0010011	ANDI

Recall: RISC-V Instruction Format

funct3		sel
000	ADD(I)	00
000	SUB	00
100	XOR(I)	11
110	OR(I)	10
111	AND(I)	01

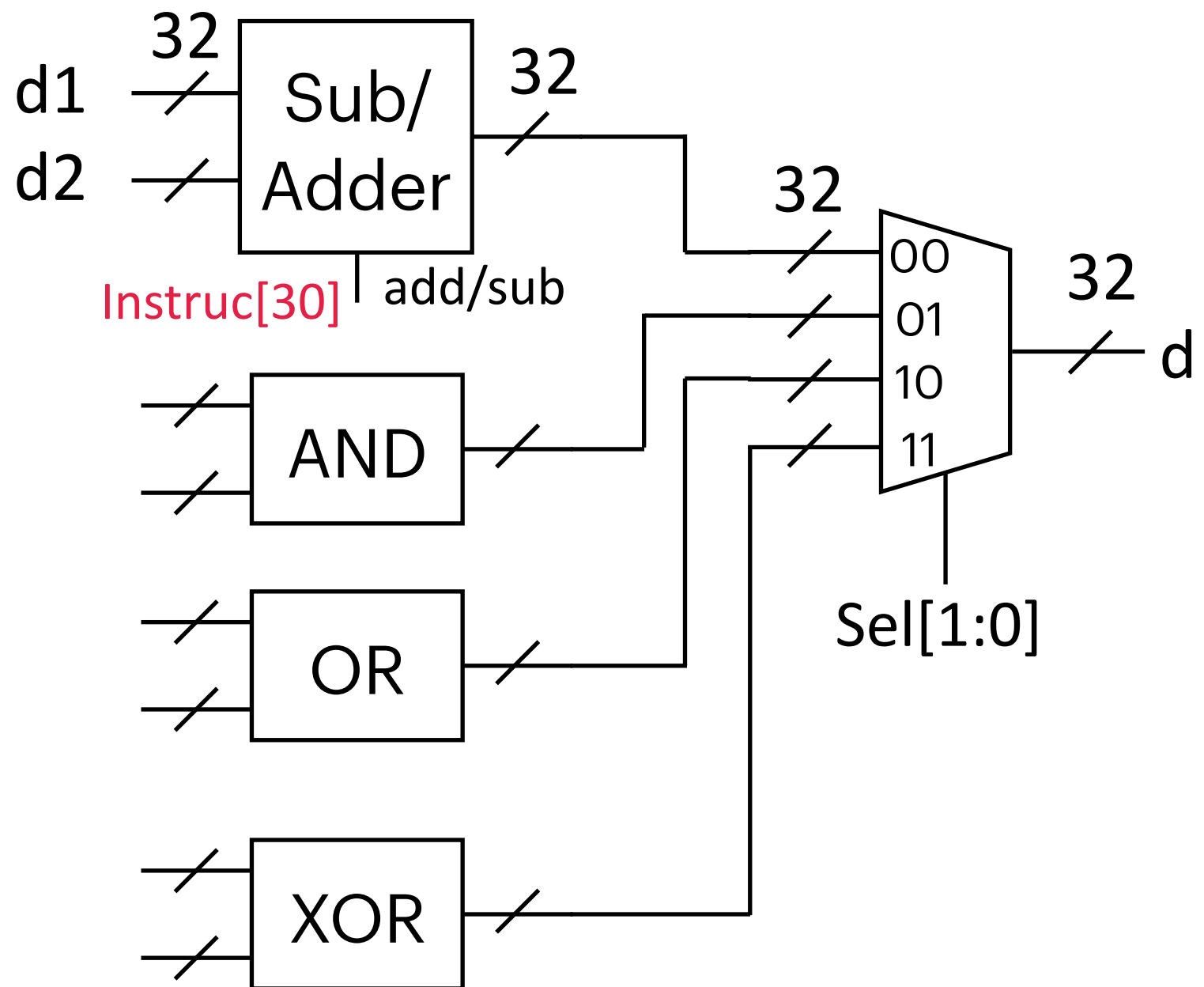


Sequential Elements

What about the registers?

Combinational Circuits with Feedbacks

 
- Circuits that can remember or store information (steady state only)
- Output depends on not only input but also current state



This structure can implement SRAM/ latches/FFs.


D Latches & D Flip-Flops

 - Latches & Flip-Flops are basic sequential circuits
 - **D**/R-S/J-K/T





One possible implementation of a D latch.



D Latches

 


A	B	Q0	Q1
0	0		
0	1		
1	0		
1	1		

  



D Latches

  


A	B	Q0	Q1
0	0		
0	1		
1	0		
1	1		

 


D Latches

  

A	B	$Q_0^{(n+1)}$	$Q_1^{(n+1)}$
0	0		
0	1		
1	0		
1	1		

 


D Latches

 


C	D	A	B	$Q_0^{(n+1)}$	$Q_1^{(n+1)}$
0	0				
0	1				
1	0				
1	1				

D Latches—Timing Diagram

 


A symbol.

C	D	A	B	$Q_0^{(n+1)}$	$Q_1^{(n+1)}$
0	0				
0	1				
1	0				
1	1				

 


Level-triggered

D Flip-Flops

 


A symbol.

C	D	$Q'^{(n+1)}$	$Q^{(n+1)}$
0	0		
0	1		
1	0		
1	1		

 


Edge-triggered

Registers & Synchronized Circuits

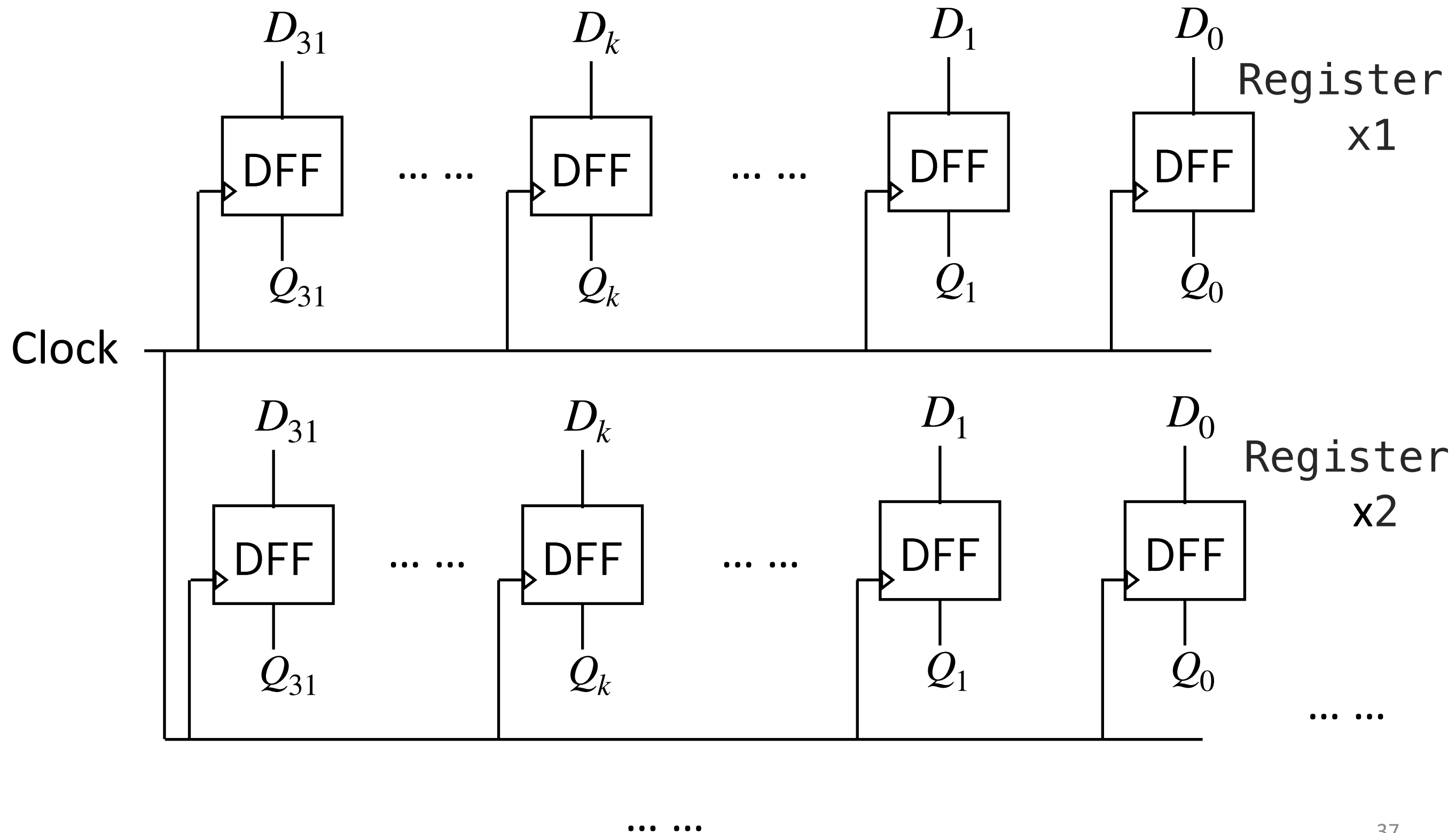


Registers & Synchronized Circuits

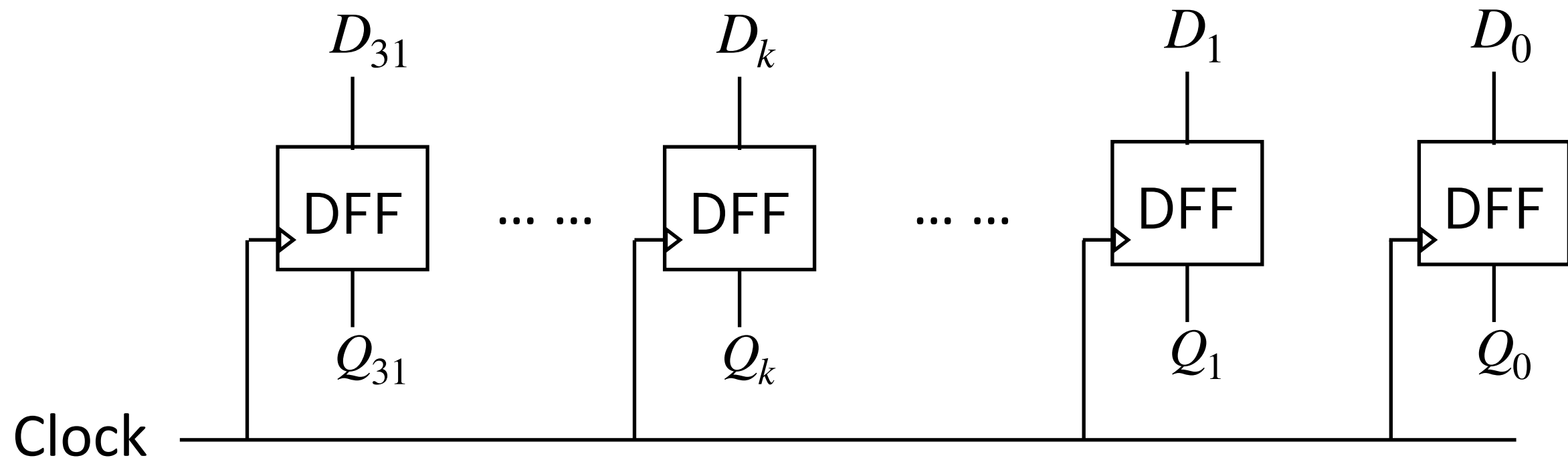

Clock: operations coordinated by it;
Help control flow of combinational
blocks; “Heartbeat” of the system


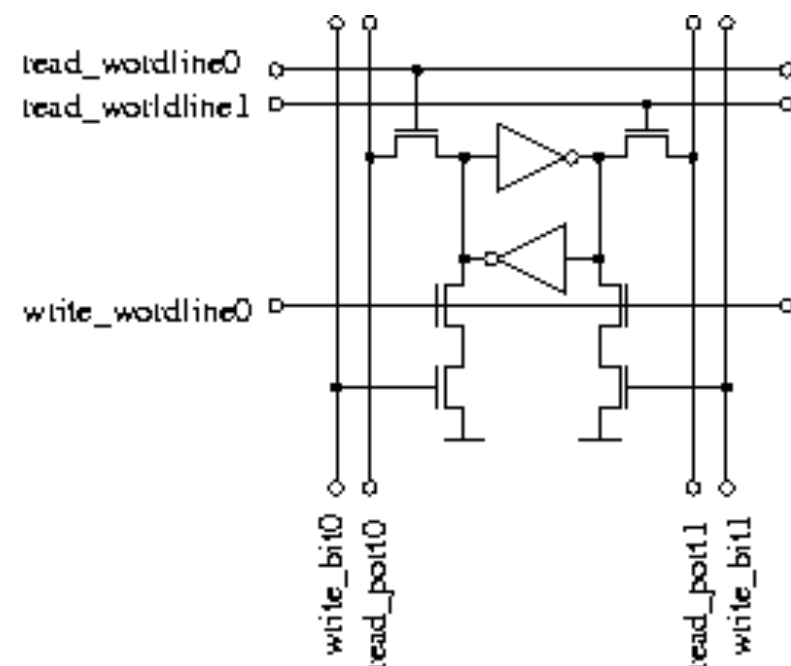
Modern CPUs use fast SRAMs
with multiple (dedicated read
and write) ports as register files.



From Wikipedia.


Other Usage of Synchronized Circuits

 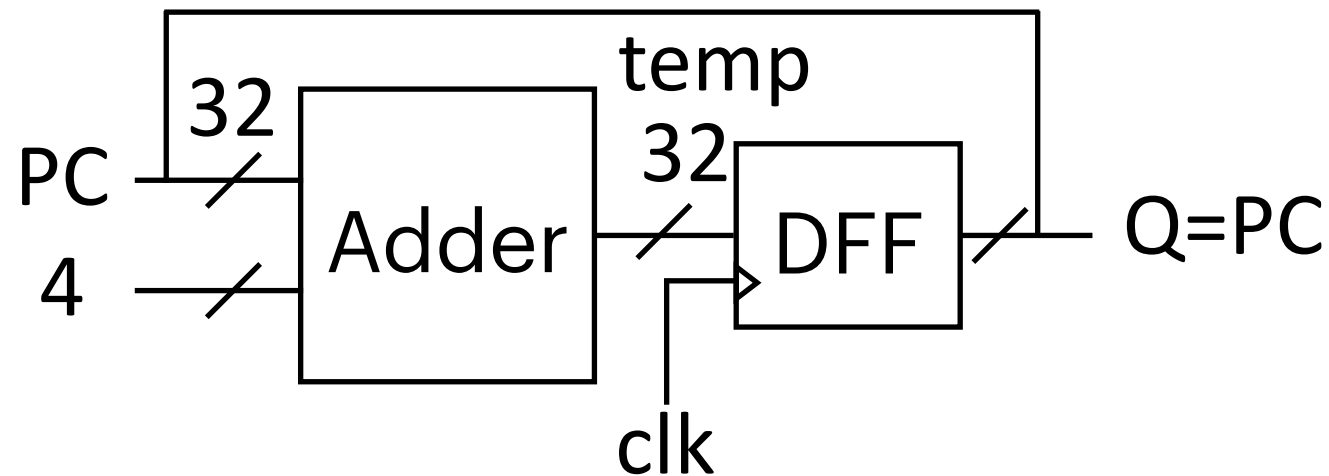- PC counter: $PC = PC + 4$ (w/o considering branch/jump)




Other Components: Shift Register

- Cascaded DFFs

 


Timing Issues

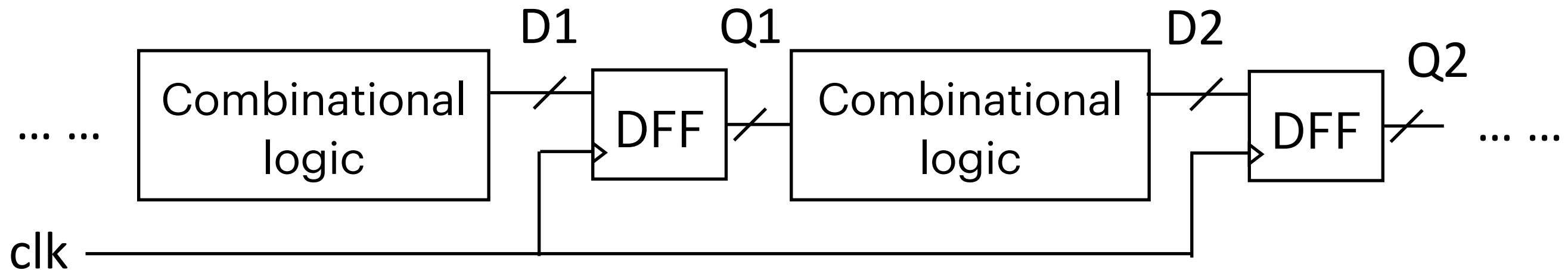- Why clk frequency cannot go to infinity?



Typical digital system: a mix of combinational & sequential circuits


1. Setup/hold time of FF

 

Like "undefined behavior" in C


Timing Issues

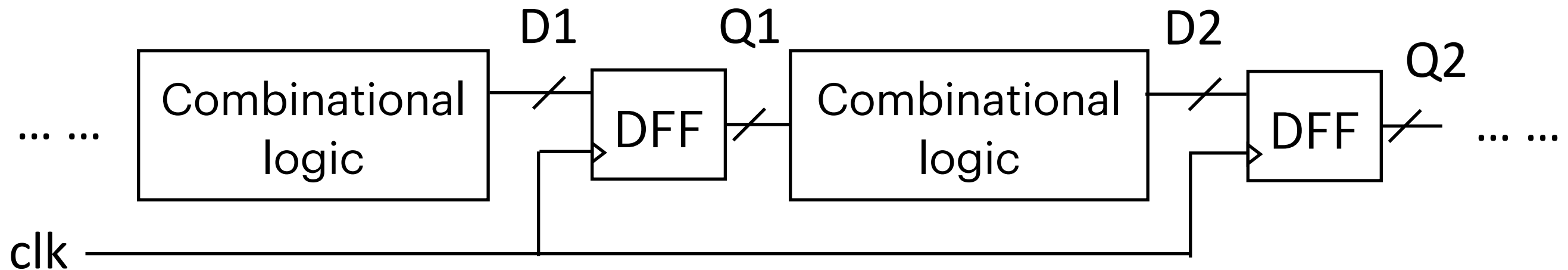- Why clk frequency cannot go to infinity?




Typical digital system: a mix of combinational & sequential circuits

1. Setup/hold time of FF

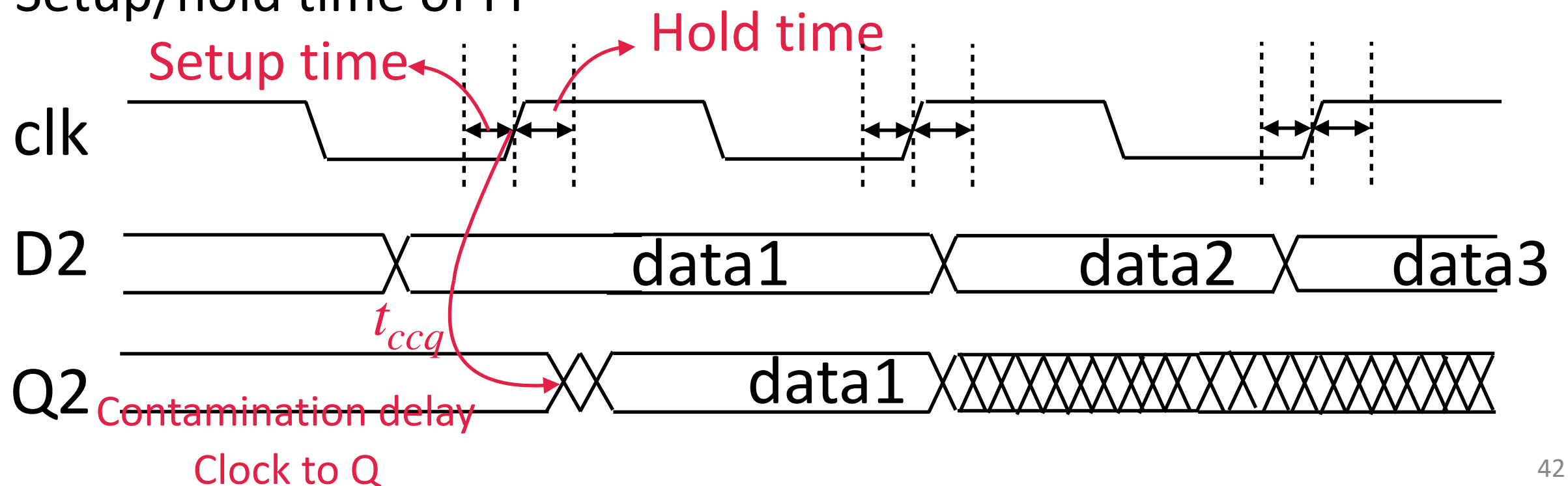


Timing Issues

 - Why clk frequency cannot go to infinity?




Typical digital system: a mix of combinational & sequential circuits

1. Setup/hold time of FF

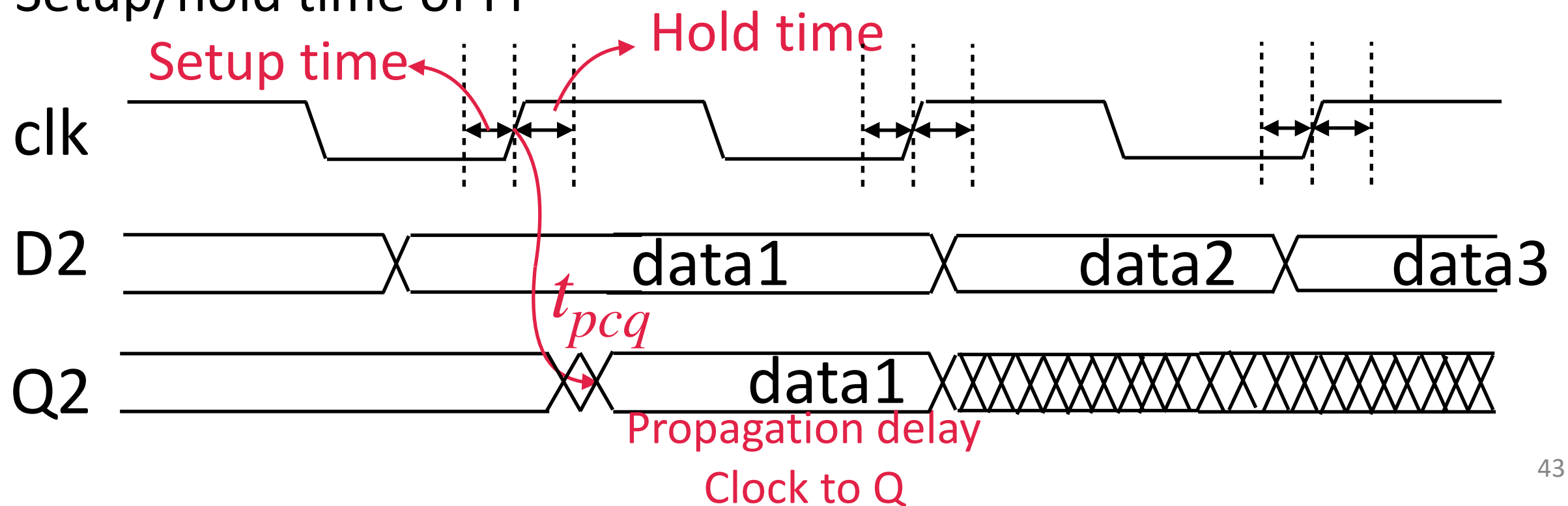

Max-Delay Constraints

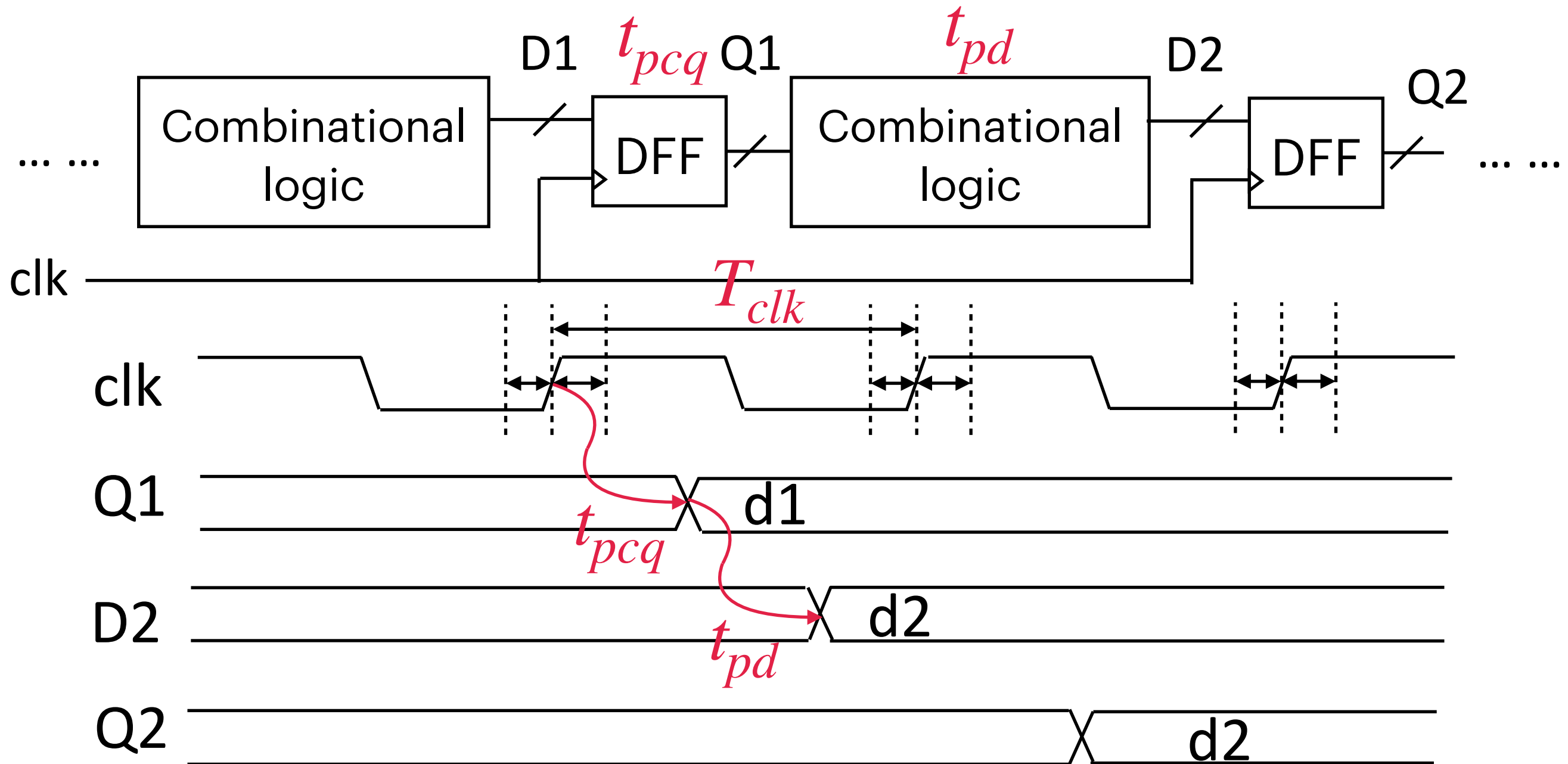
- Why clk frequency cannot go to infinity?



$$T_{clk} \geq t_{pcq} + t_{pd} + \text{setup time}$$

Max-Delay Constraints

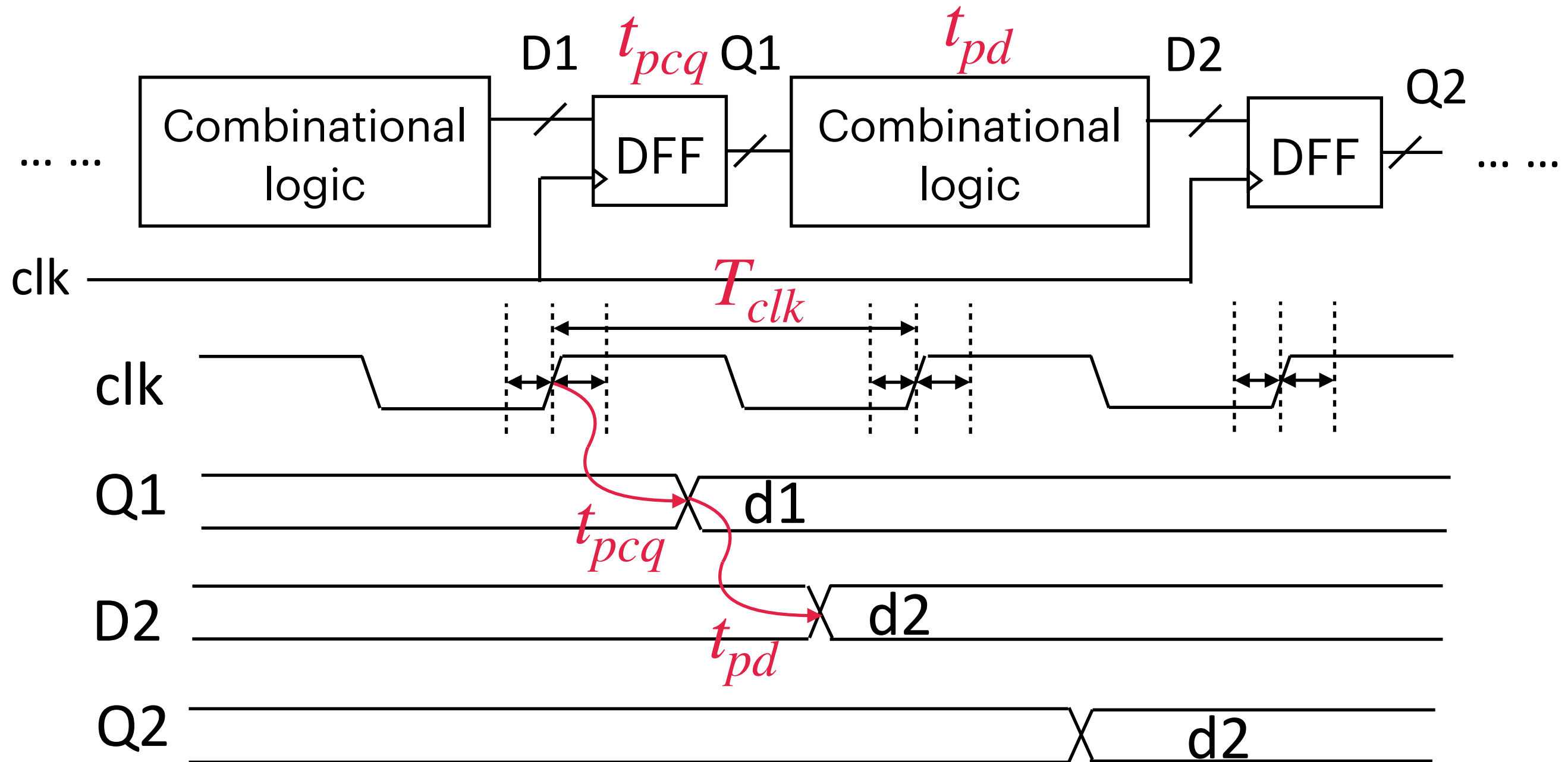
- Why clk frequency cannot goes to infinity?




$$T_{clk} \geq t_{pcq} + t_{pd} + \text{setup time} \quad \text{Critical path}$$

Min-Delay Constraints

- Avoid hold time violation

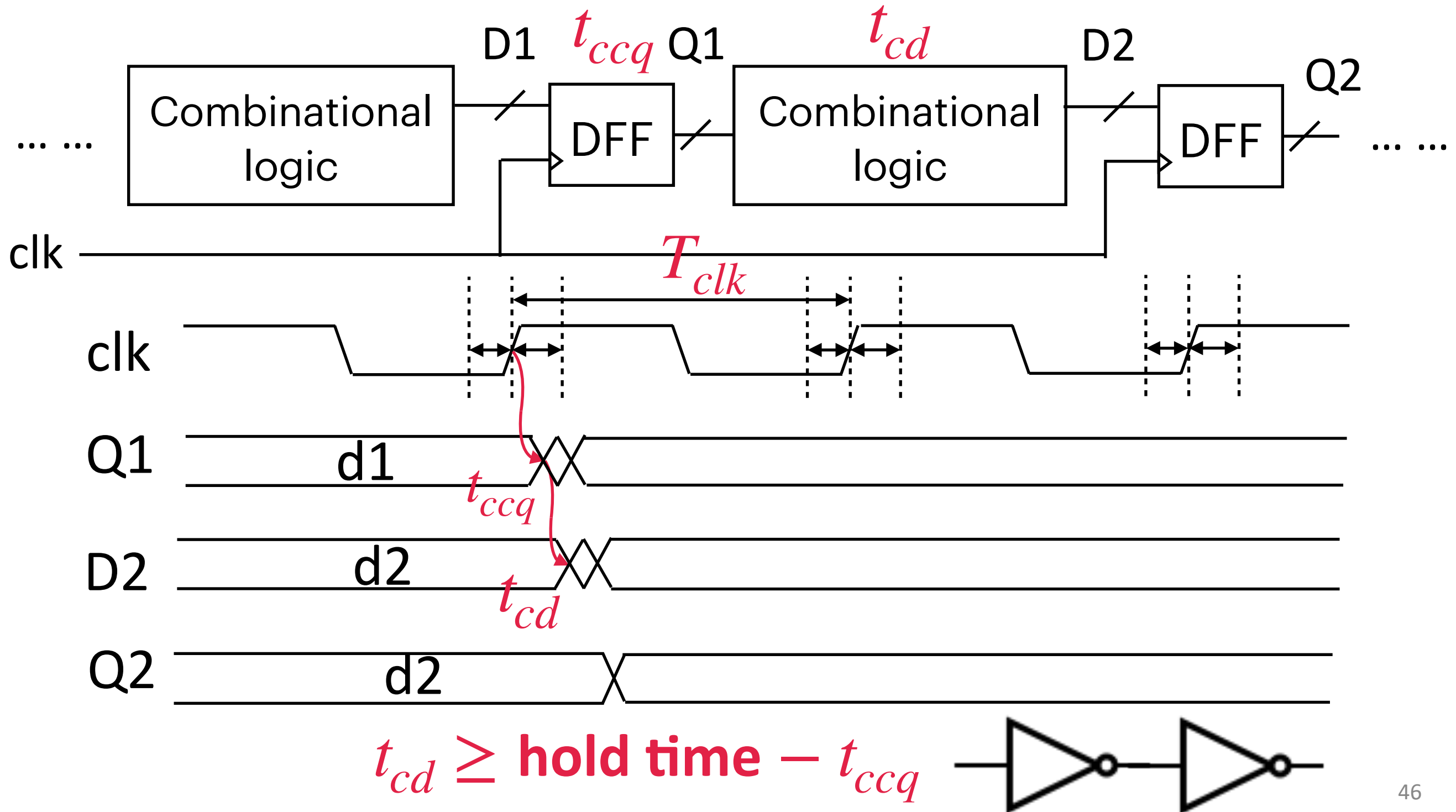

Question

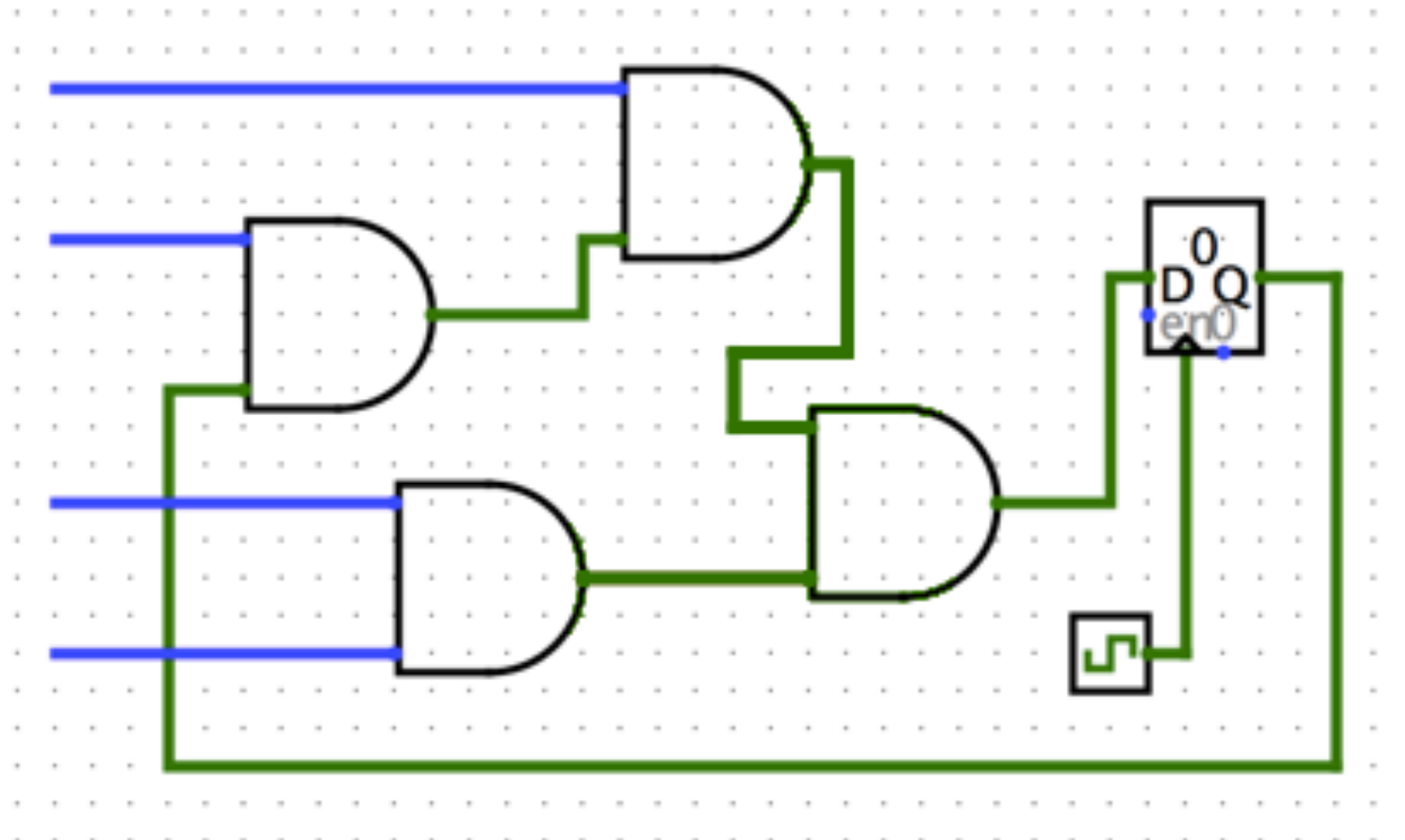

Clock->Q (P) 1ns
Setup 1ns
Hold 1ns
AND delay 1ns

What is maximum clock frequency?


- A: 5 GHz
- B: 500 MHz
- C: 200 MHz
- D: 250 MHz
- E: 1/6 GHz

Finite-State Machine (FSM)

“Give me the place to stand, and I shall move the [earth](#).” — Archimedes

FSM

 
- FSMs consists of states, transitions, an entrance (initial state) and input/output (optional)



C Program as an FSM


- FSMs consists of states, transitions, an entrance (initial state) and input/output (optional)
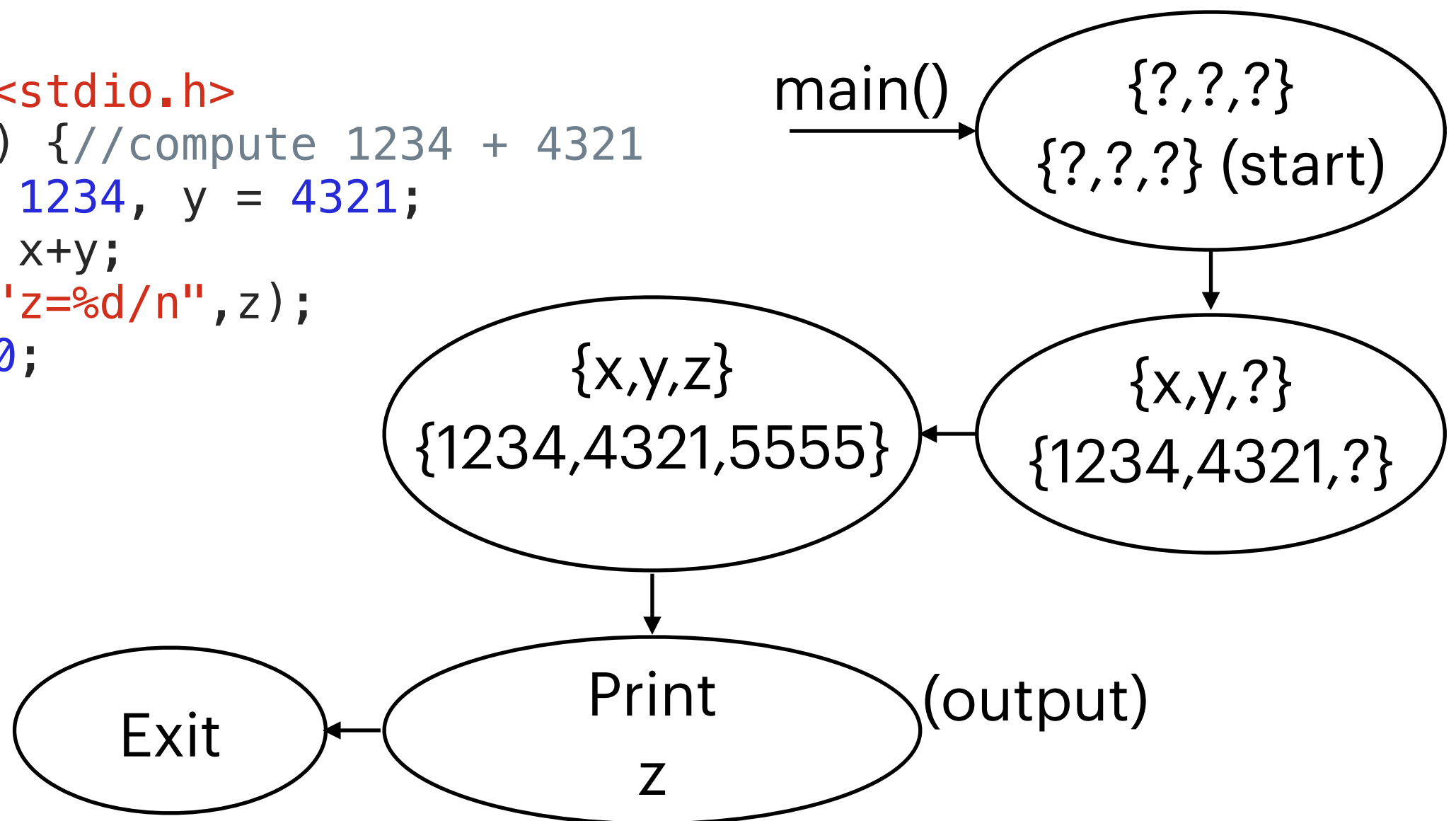
```
#include <stdio.h>
int main() { //compute 1234 + 4321
    int x = 1234, y = 4321;
    int z = x+y;
    printf("z=%d/n", z);
    return 0;
}
```



ISA as an FSM


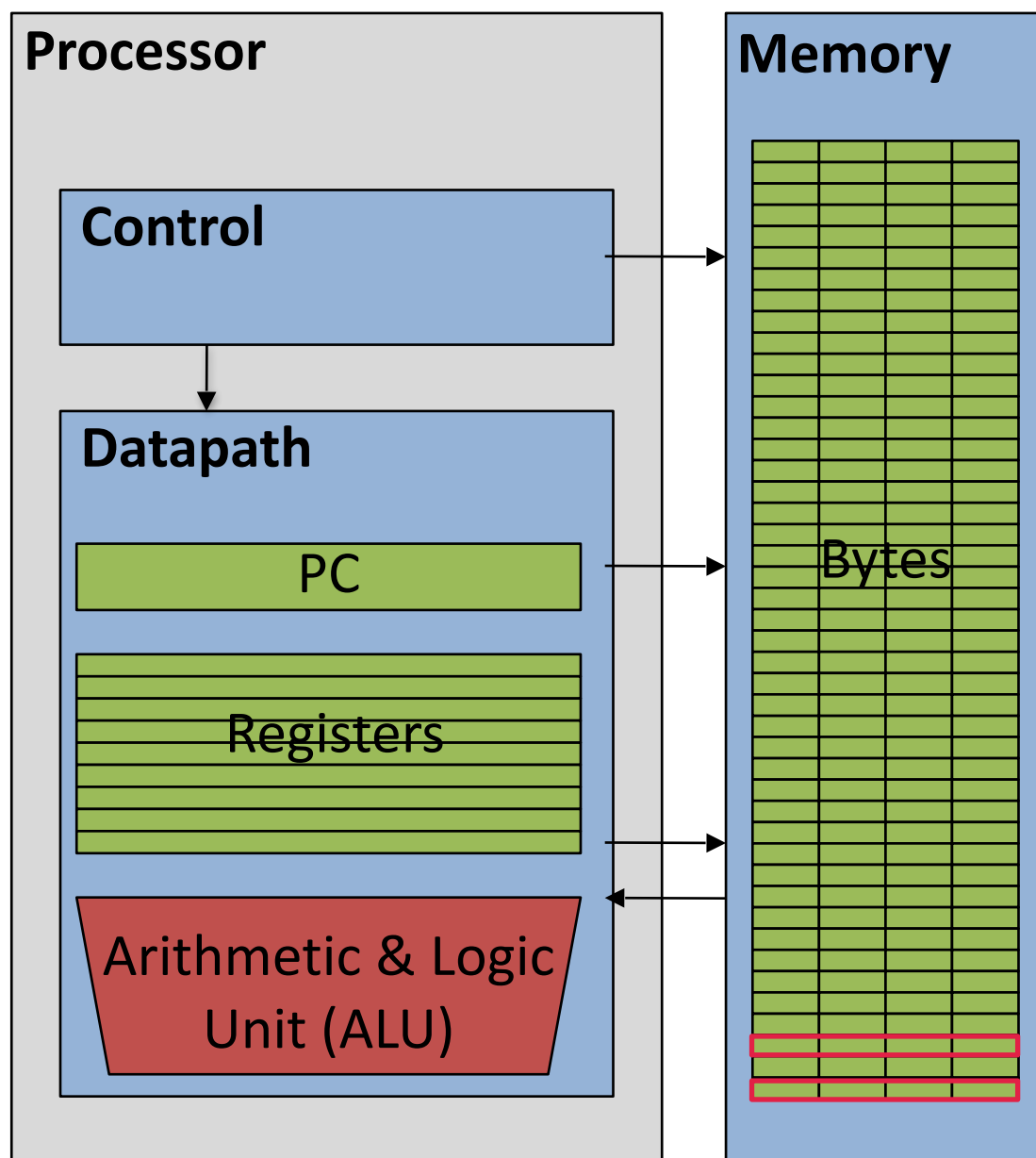
- FSMs consists of states, transitions, an entrance (initial state) and input/output (optional)



- States: all registers & memory
- Transition: register/memory value change
- Entrance: power on
- Input: instructions, can change registers/memory value
- Output: states of each registers/memory

Digital Systems as FSMs

  
- FSMs consists of states, transitions, an entrance (initial state) and input/output (optional)



State transition diagram

A Classic Problem: Build Digital Circuit for Sequence Detection

 - Build a digital circuit, detecting the occurrence of {101} in the input 0/1 sequence (non-overlapping)



input: 0 or 1 in a sequence, one bit at a clock cycle


Output: 1 after {101} detected, otherwise 0;

States: ?

Transition: ?

A Classic Problem: Build Digital Circuit for Sequence Detection

 - Build a digital circuit, detecting the occurrence of {101} in the input 0/1 sequence (non-overlapping)





input: 0 or 1 in a sequence, one bit at a clock cycle

Output: 1 after {101} detected, otherwise 0;


States:

Transition:

  


A Classic Problem: Build Digital Circuit for Sequence Detection

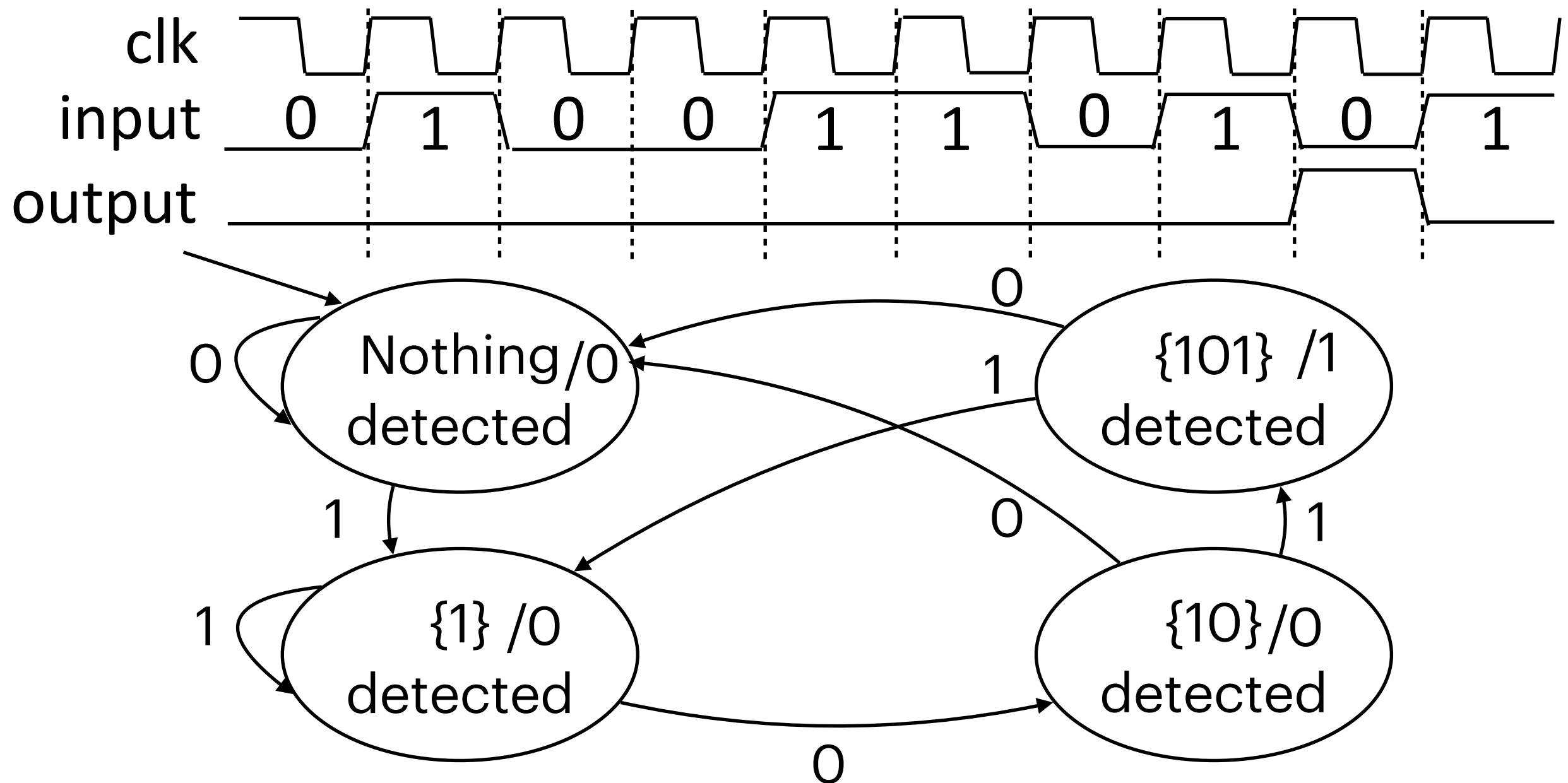- Build a digital circuit, detecting the occurrence of {101} in the input 0/1 sequence (non-overlapping)




A Classic Problem: Build Digital Circuit for Sequence Detection

 - Everything is a number. Use binary numbers to encode states: {00, 01, 10, 11}



A Classic Problem: Build Digital Circuit for Sequence Detection

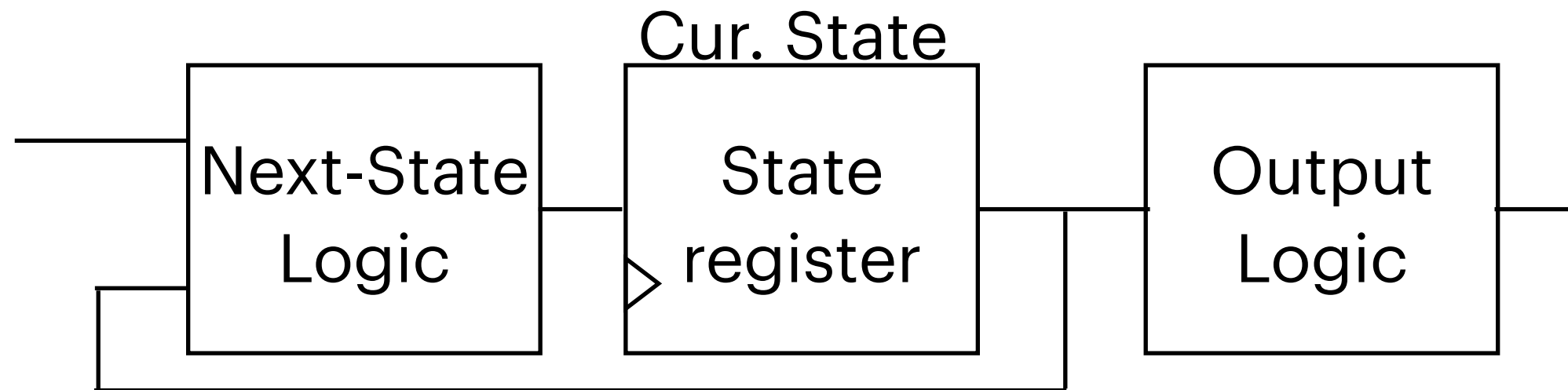
- A digital circuit model (TaoLu) for FSM (Moore machine)



- Timing diagram

A Classic Problem: Build Digital Circuit for Sequence Detection

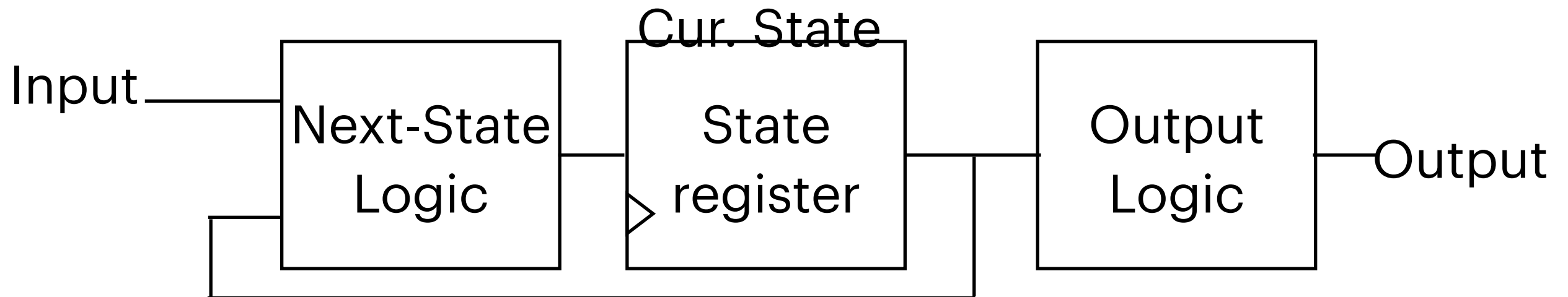- A digital circuit model for FSM (Moore machine)




- Truth table

Cur.State	Input	Next State	Output
00	0	00	0
00	1	01	0
01	0	10	0
01	1	01	0
10	0	00	0
10	1	11	0
11	0	00	1
11	1	01	1

A Classic Problem: Build Digital Circuit for Sequence Detection

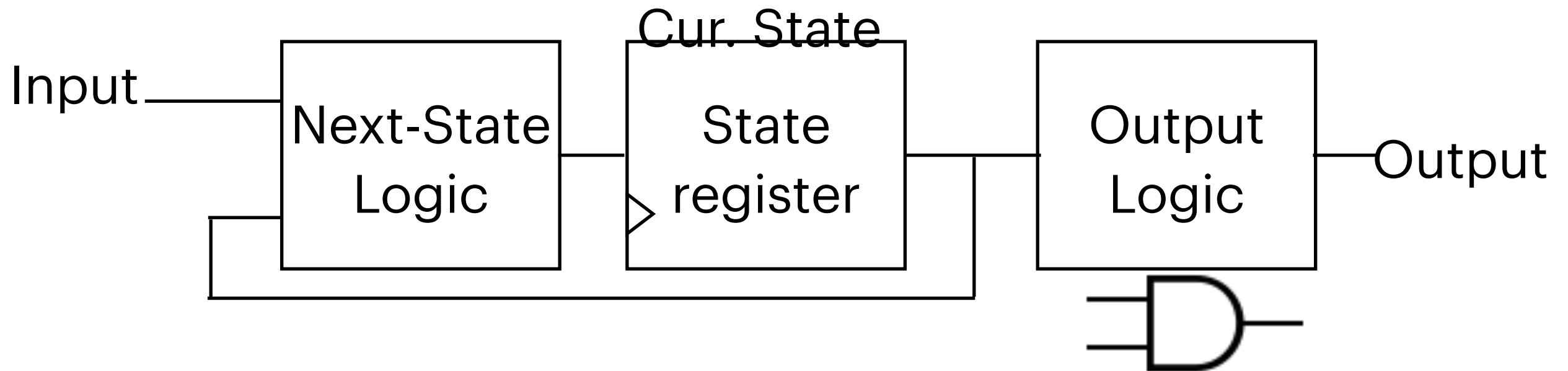- A digital circuit model for FSM (Moore machine)



- Truth table

Cur.State	Input	Next State	Output
00	0	00	0
00	1	01	0
01	0	10	0
01	1	01	0
10	0	00	0
10	1	11	0
11	0	00	1
11	1	01	1