

Synchronous Digital Systems - SDS

LiHan

2023/03/17

Synchronous Digital Systems

- ▶ Synchronous: All operations coordinated by a central clock
- ▶ Digital: All operations are limited by 0 and 1
- ▶ SDS: Combinational Logic and Sequential Logic

Switch - MOSFET

 
 
 


Figure: NMOS

Switch - MOSFET


 
 
 


Figure: NMOS AND PMOS

CMOS TO LOGIC

 


IN	OUT
0	1
1	0

Basic Logic Gates

- ▶ NOT
- ▶ AND
- ▶ OR




IN1	IN2	OUT
0	0	0
0	1	0
1	0	0
1	1	1

 

IN1	IN2	OUT
0	0	1
0	1	1
1	0	1
1	1	0



IN1	IN2	OUT
0	0	0
0	1	1
1	0	1
1	1	1

 

IN1	IN2	OUT
0	0	1
0	1	0
1	0	0
1	1	0



IN1	IN2	OUT
0	0	0
0	1	1
1	0	1
1	1	0



IN1	IN2	OUT
0	0	1
0	1	0
1	0	0
1	1	1

Figure: LOGIC GATES AND TRUTH TABLE


COMBINATIONAL LOGIC

$$Y = A_3A_2A_1A_0 + B_3B_2B_1B_0$$

$$\begin{array}{r} C_2C_1 \\ A_3A_2A_1A_0 \\ + \quad B_3B_2B_1B_0 \\ \hline Y_1 \end{array}$$

A_i	B_i	C_i	C_{i+1}	Y_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$Y_i = A_i \oplus B_i \oplus C_i$$

 

$$C_{i+1} = A_iB_i + A_iC_i + B_iC_i$$


 
 
 



Figure: COMPLEX LOGIC

SEQUENTIAL LOGIC

IN1	IN2	OUT
0	0	1
0	1	1
1	0	1
1	1	0

 

$CLK = 1 \quad Q = D$

 

 


Figure: SDS