

Course Info

- No Lab next week, prepare your mid-term exam!
- Project 1.2 deadline March 31th. Start early!!!
- HW3 ddl March 18th! HW4 will be released next week, keep an eye on piazza.
- Next week discussion on ALU & FSM.
- Update on slip-day policy: automatic slip-day deduction if submission after ddl. No need to email TA/instructor. If you want to test your code after ddl, contact TAs directly.
- Mid-term next Tuesday 8:00 am-10:00 am, we will use teaching center Room 301/404/405. Arrive 7:45 am to check-in and find your seat. Bring your student ID card!



信息科学与技术学院

School of Information Science and Technology

CS 110

Computer Architecture

Datapath & Controller

Instructors:

Siting Liu & Chundong Wang


Course website: [https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/
Spring-2023/index.html](https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2023/index.html)

School of Information Science and Technology (SIST)


ShanghaiTech University

2023/3/5

Components of a Computer

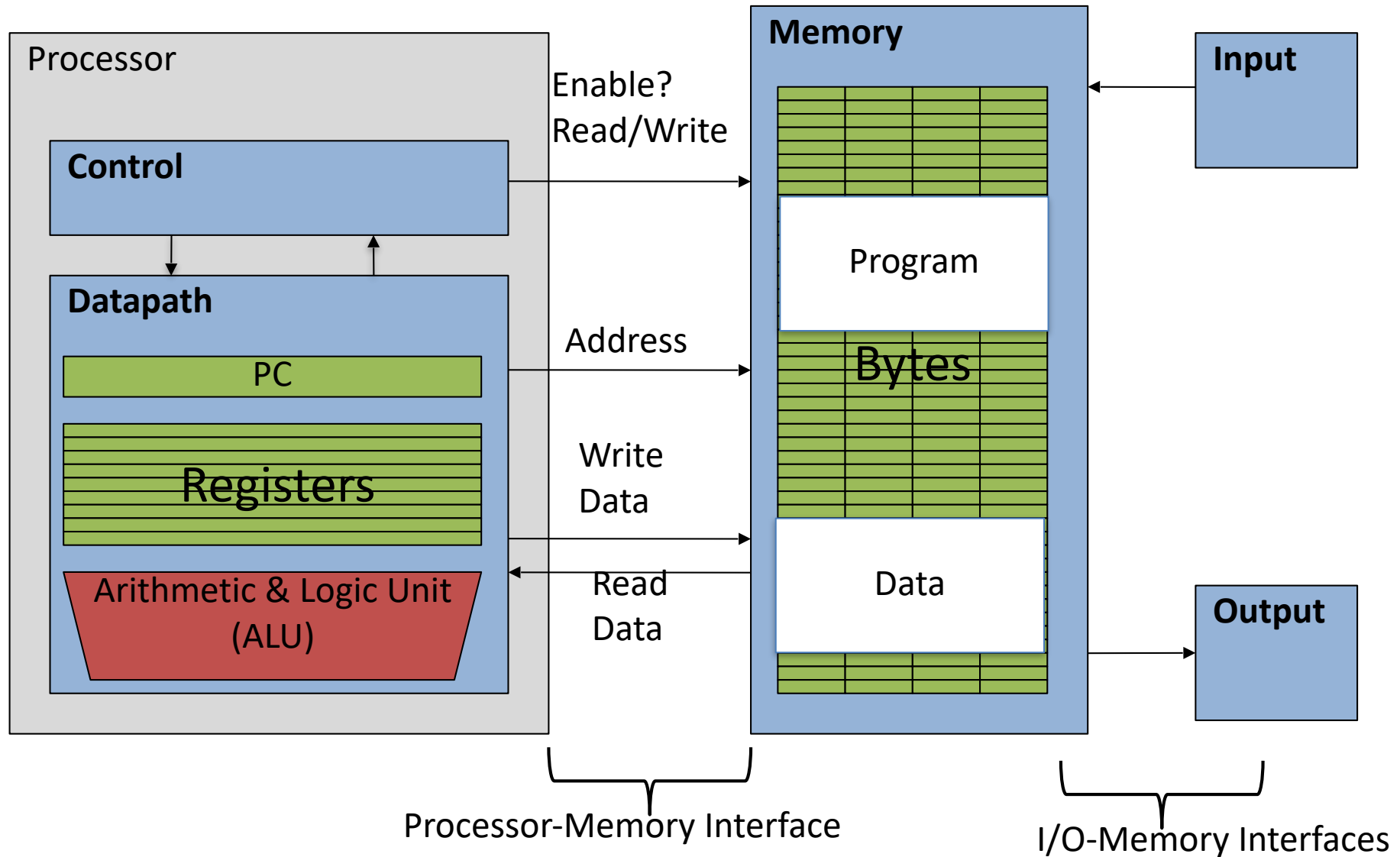


Full Register File

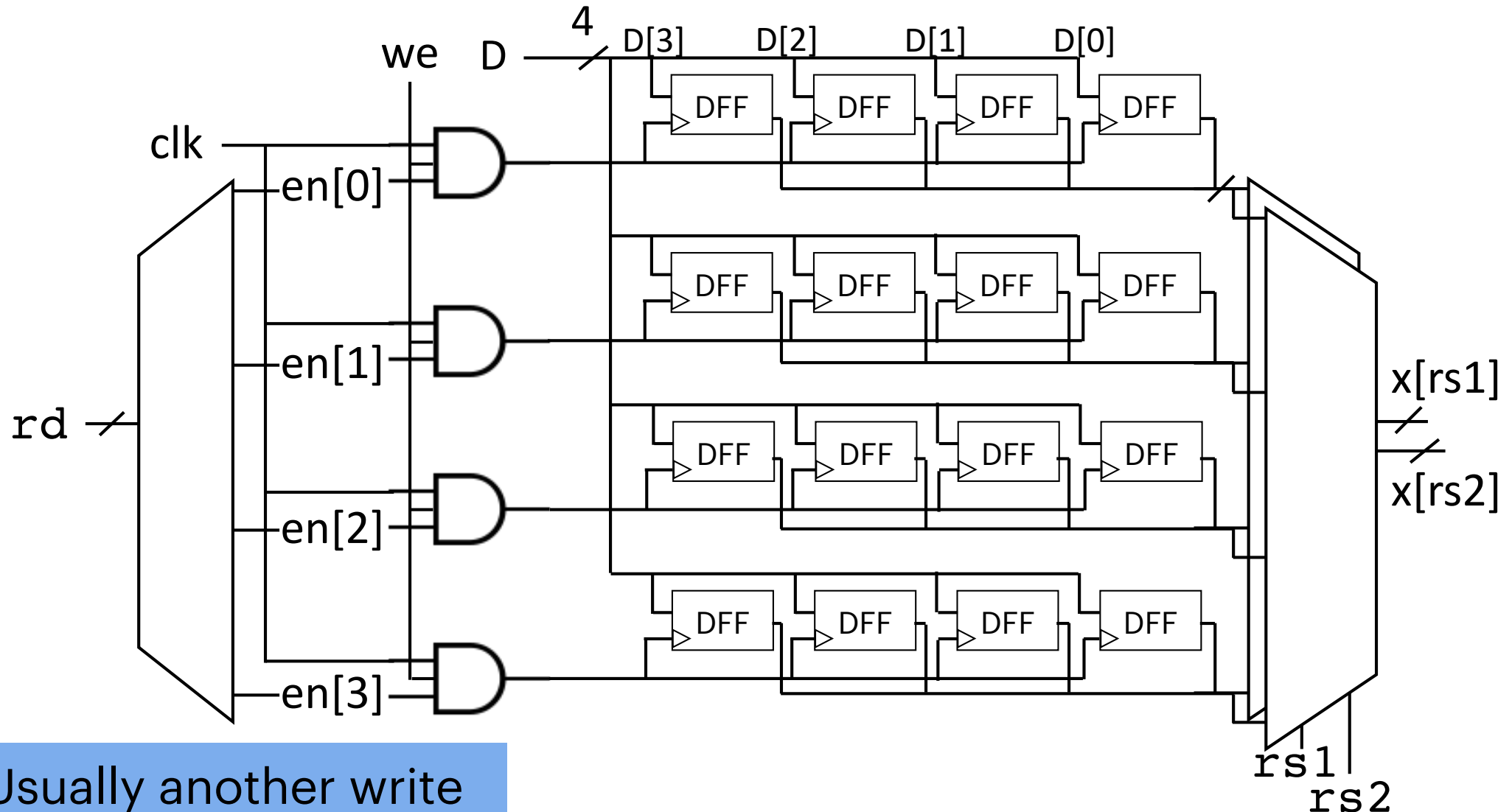



Usually another write enable signal

Full Register File—a Symbol

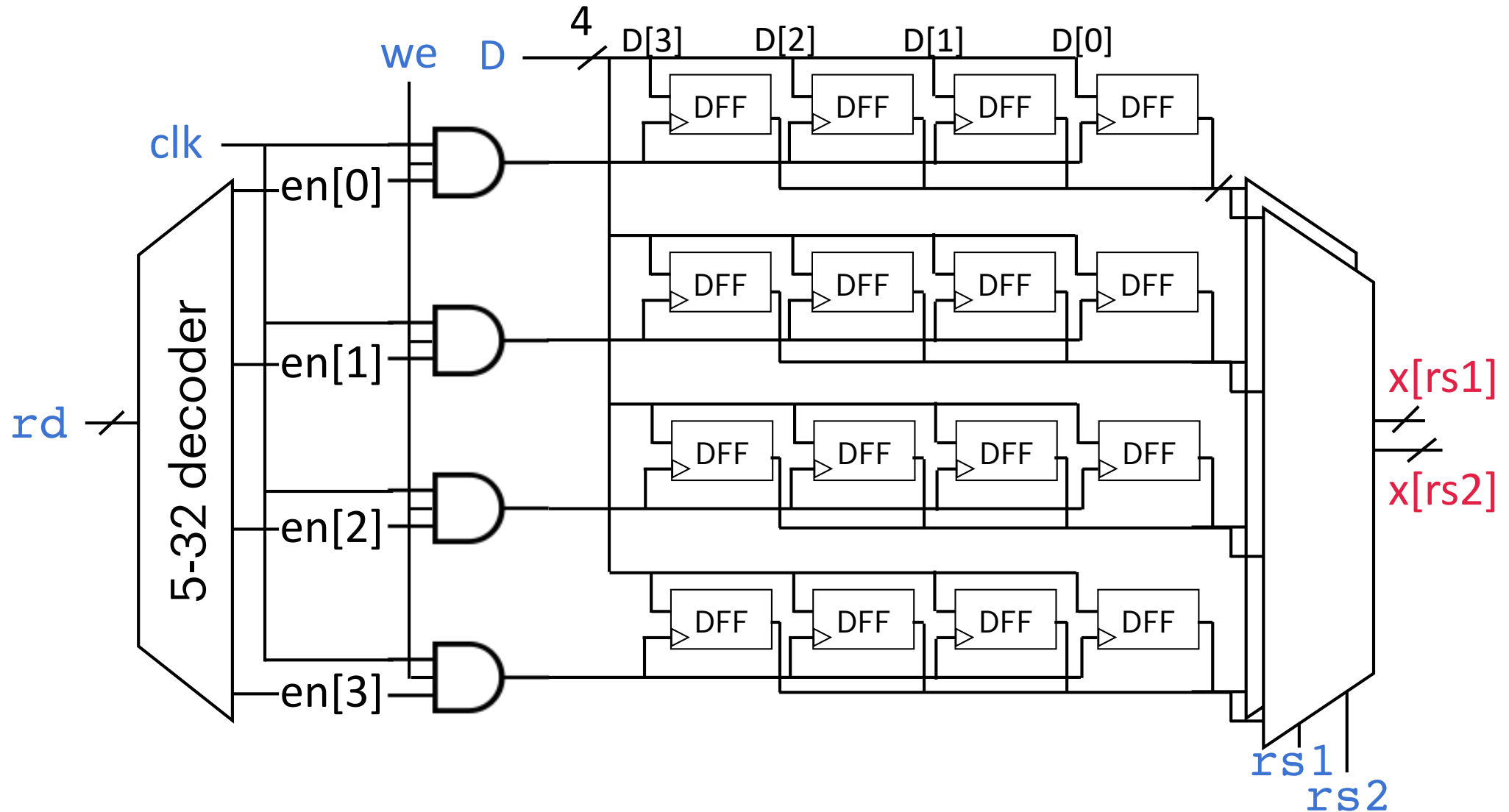


Full Register File—a Symbol

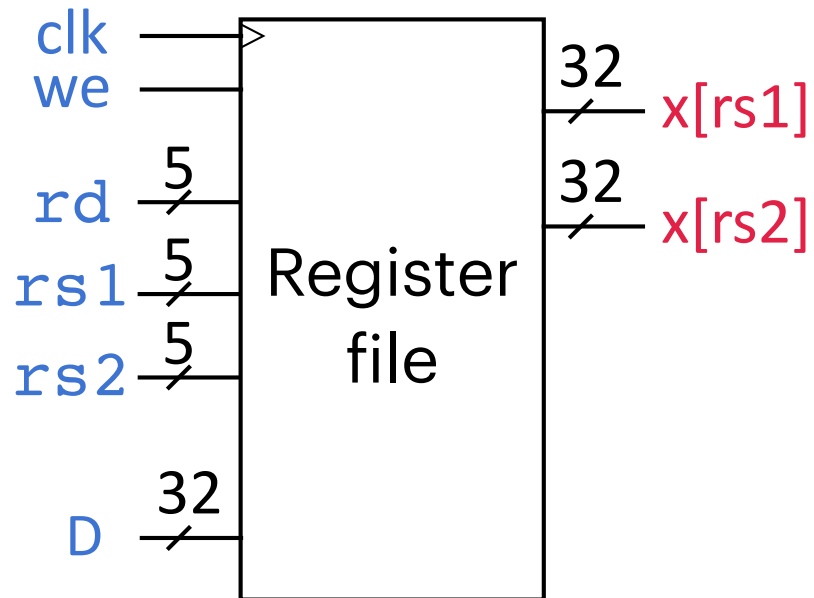


 



Datapath Construction

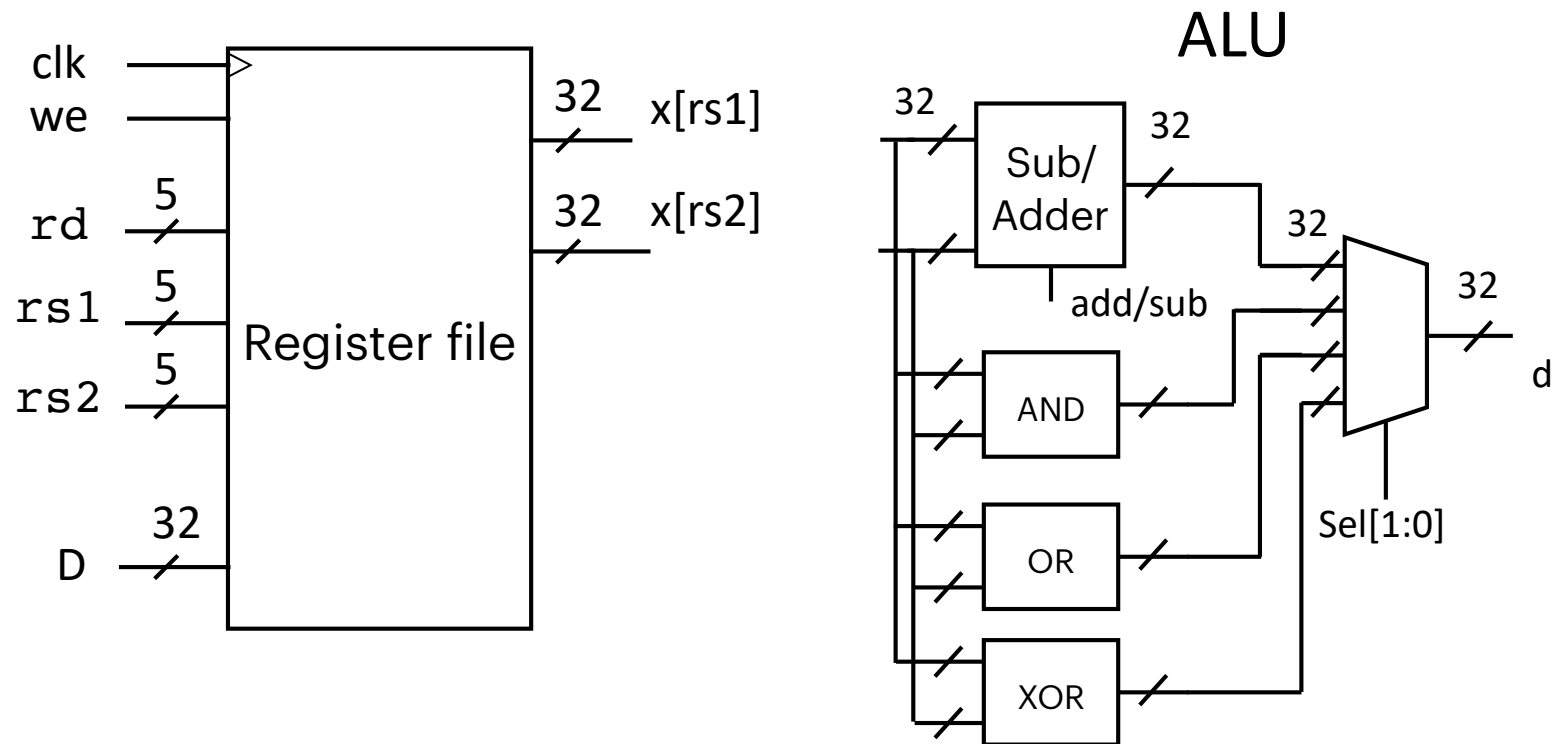


Datapath Construction

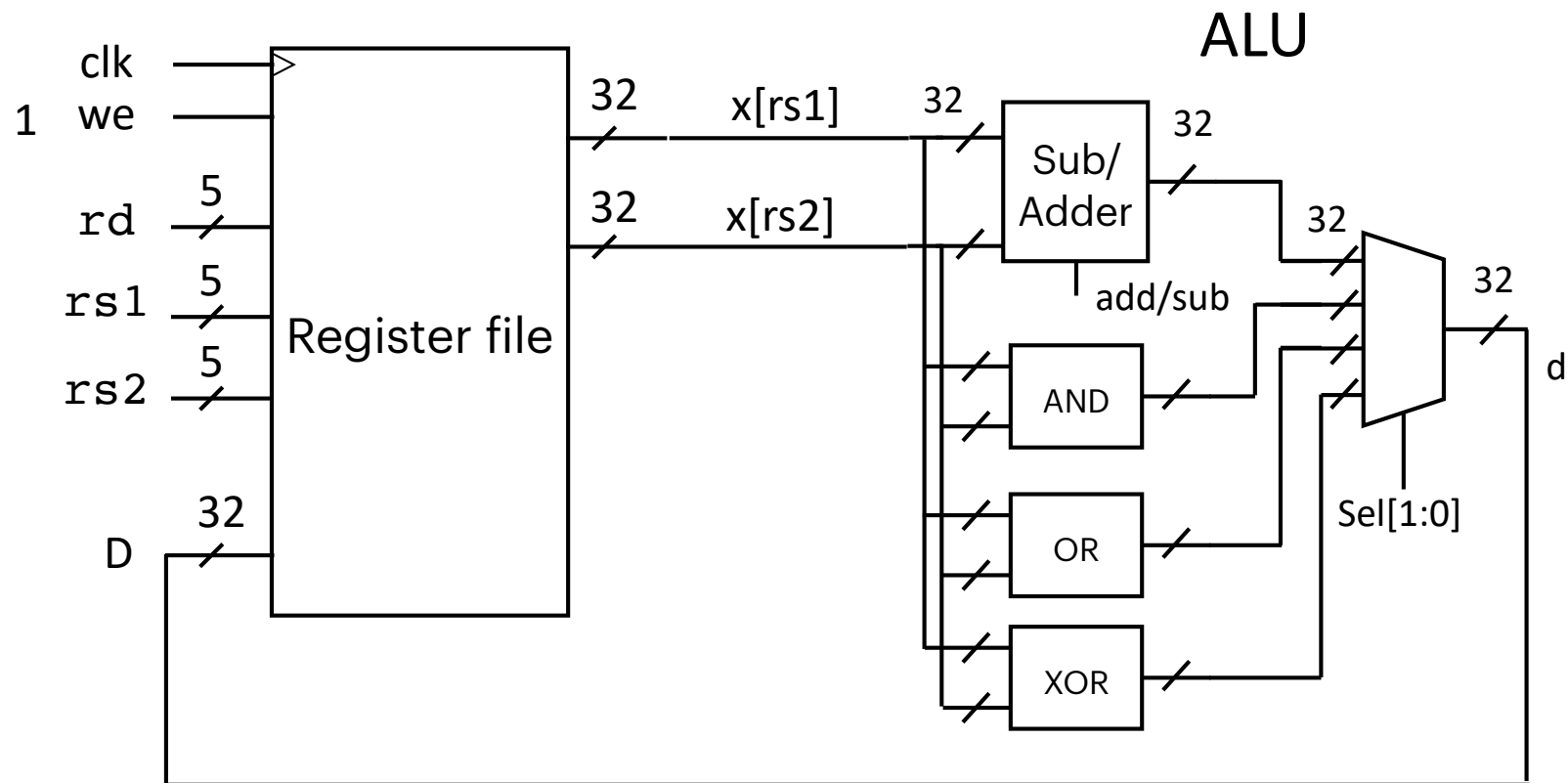



Datapath Construction

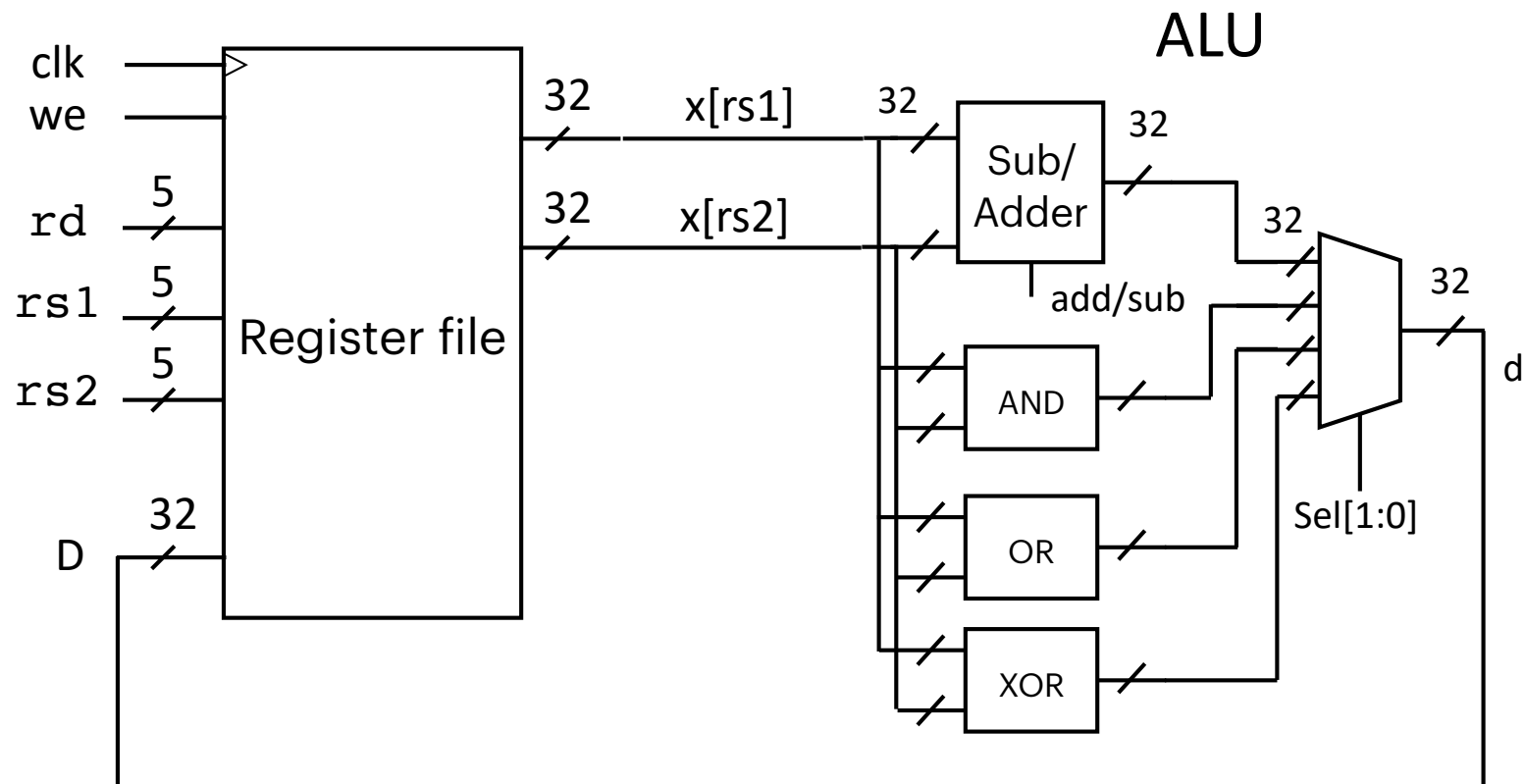 



Datapath Construction

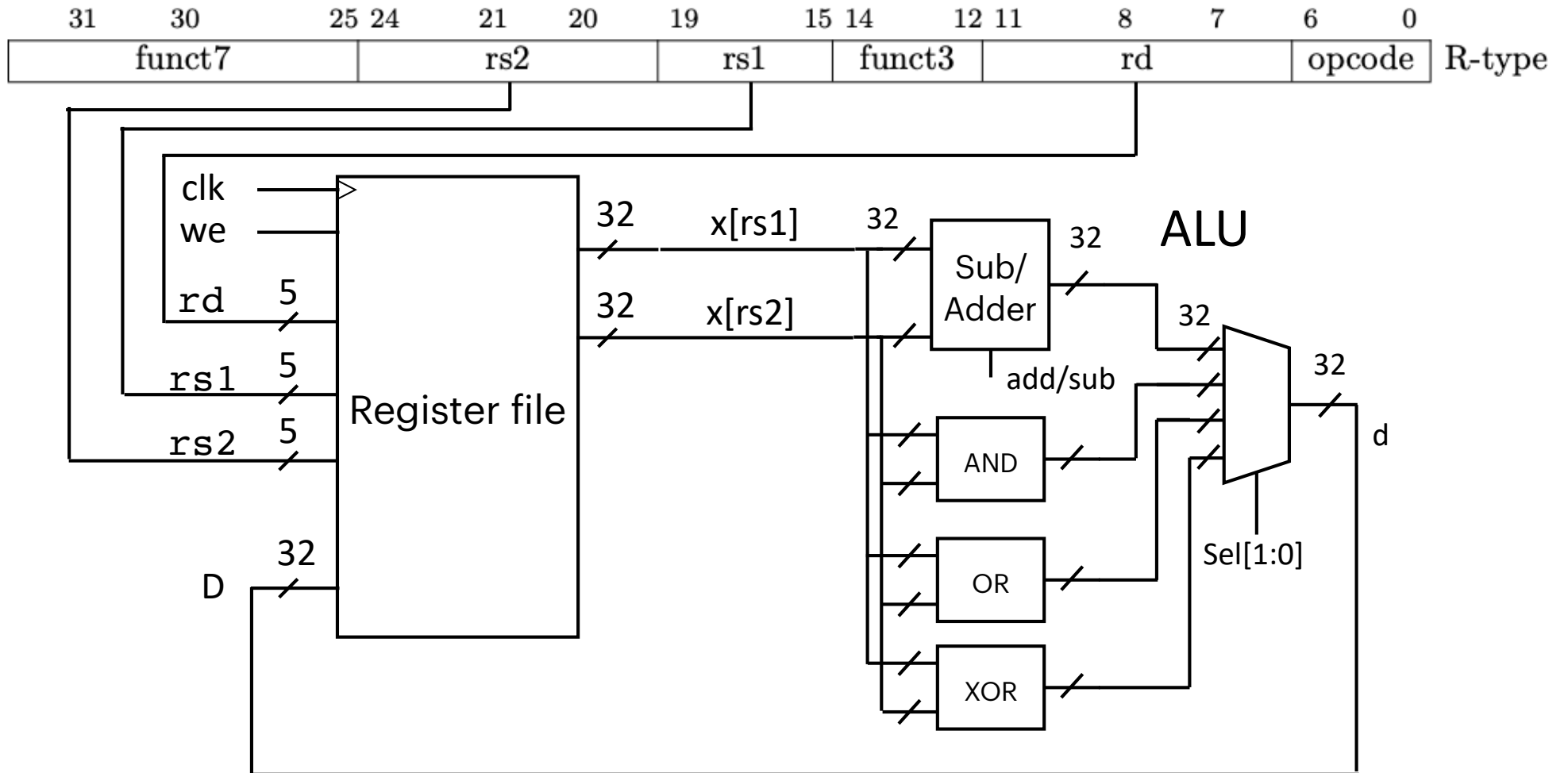


Datapath Construction

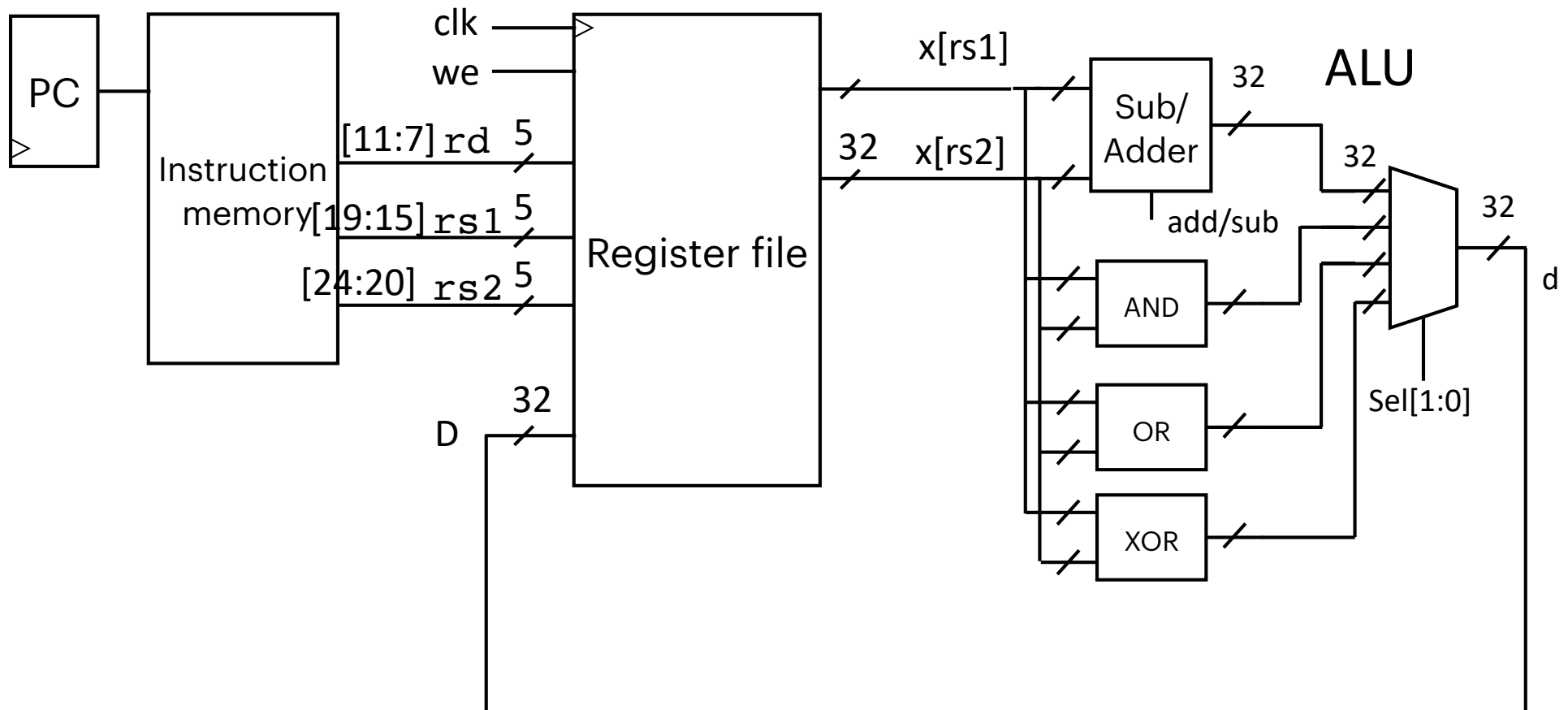 


Datapath Construction

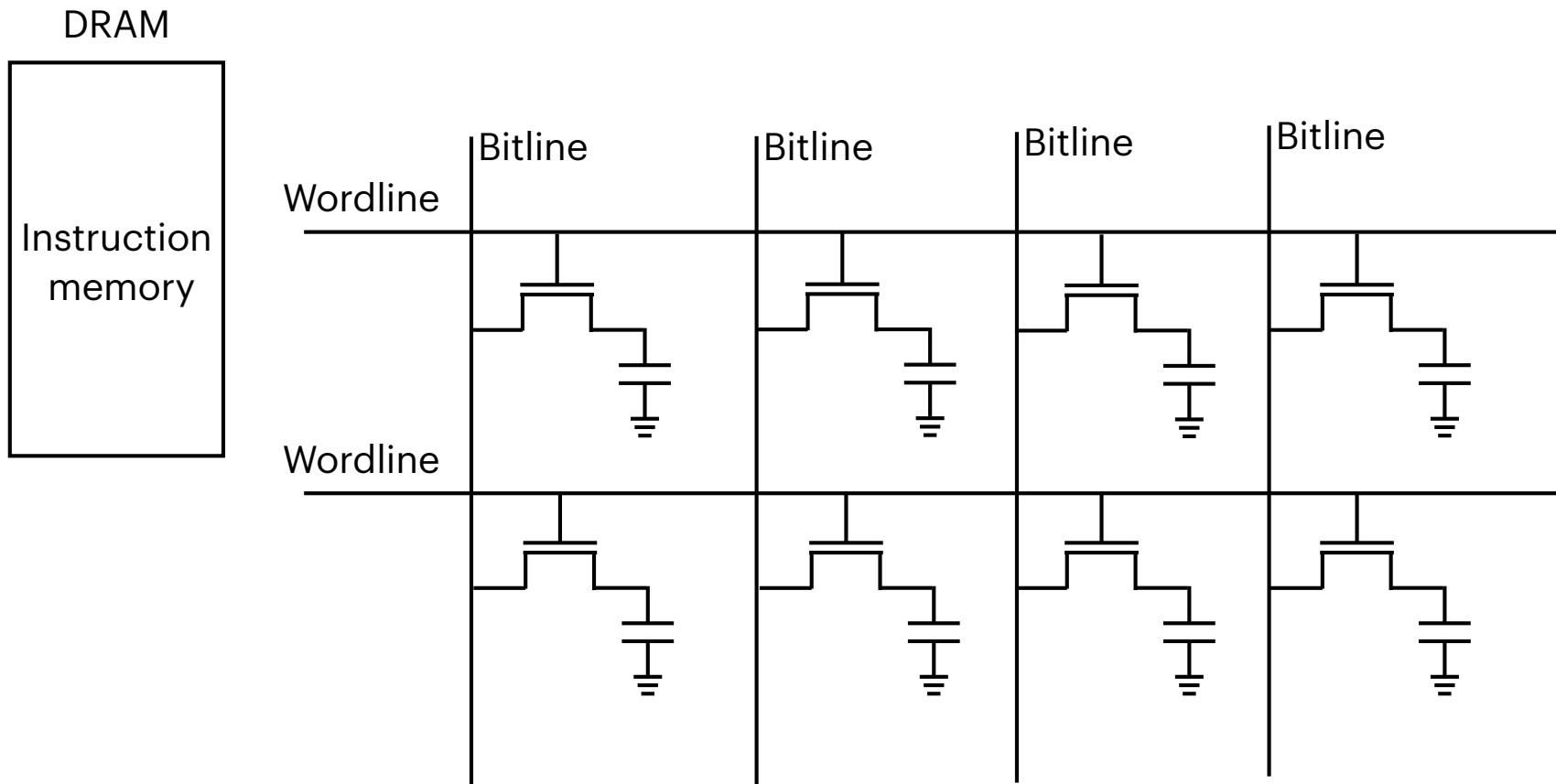 



Datapath Construction

 


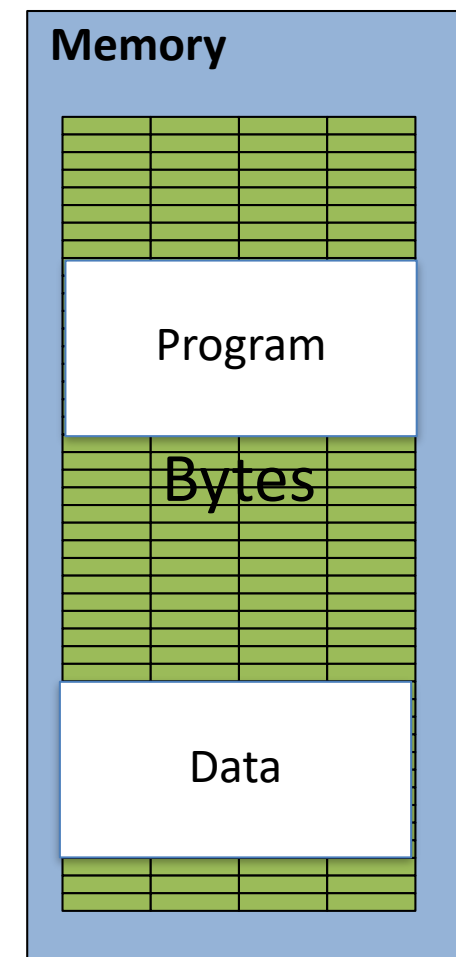
- Other memory considerations
 - Assume separate instruction/data memory
 - Synchronous write & asynchronous read so that all the state elements update at `posedge`
 - Registers behave similarly





Datapath Construction

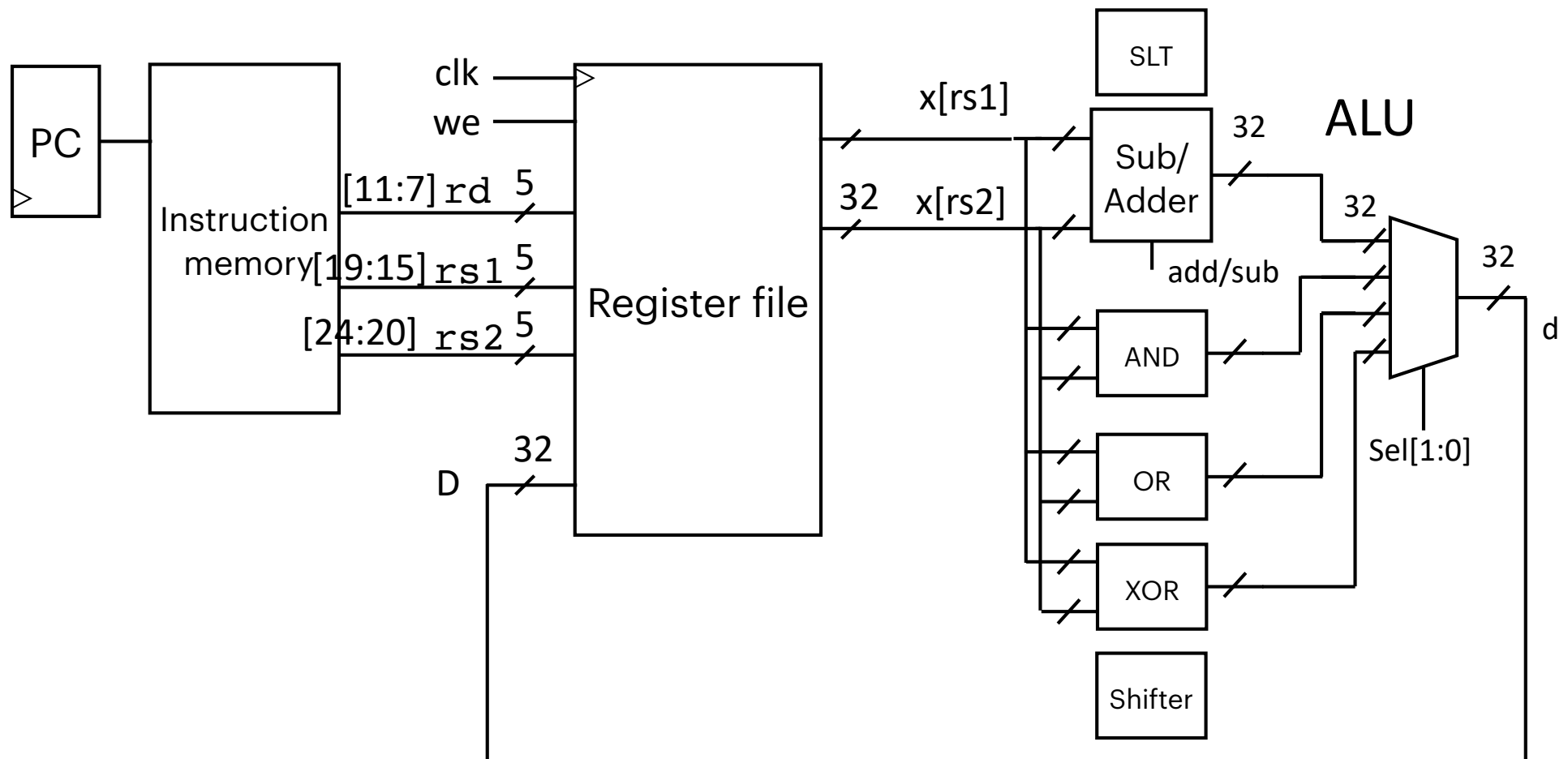 

Datapath Construction

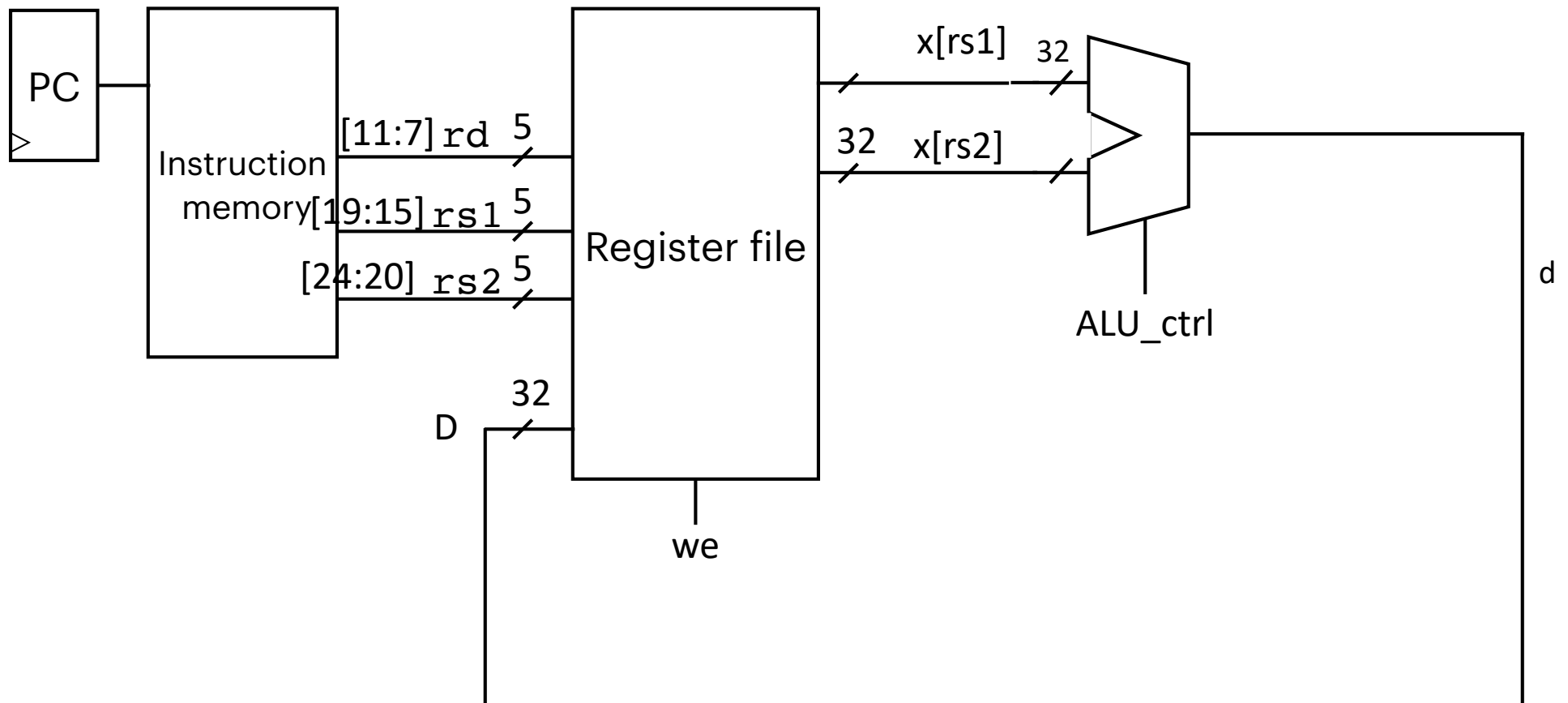
 


I-type Arithmetic & Logic

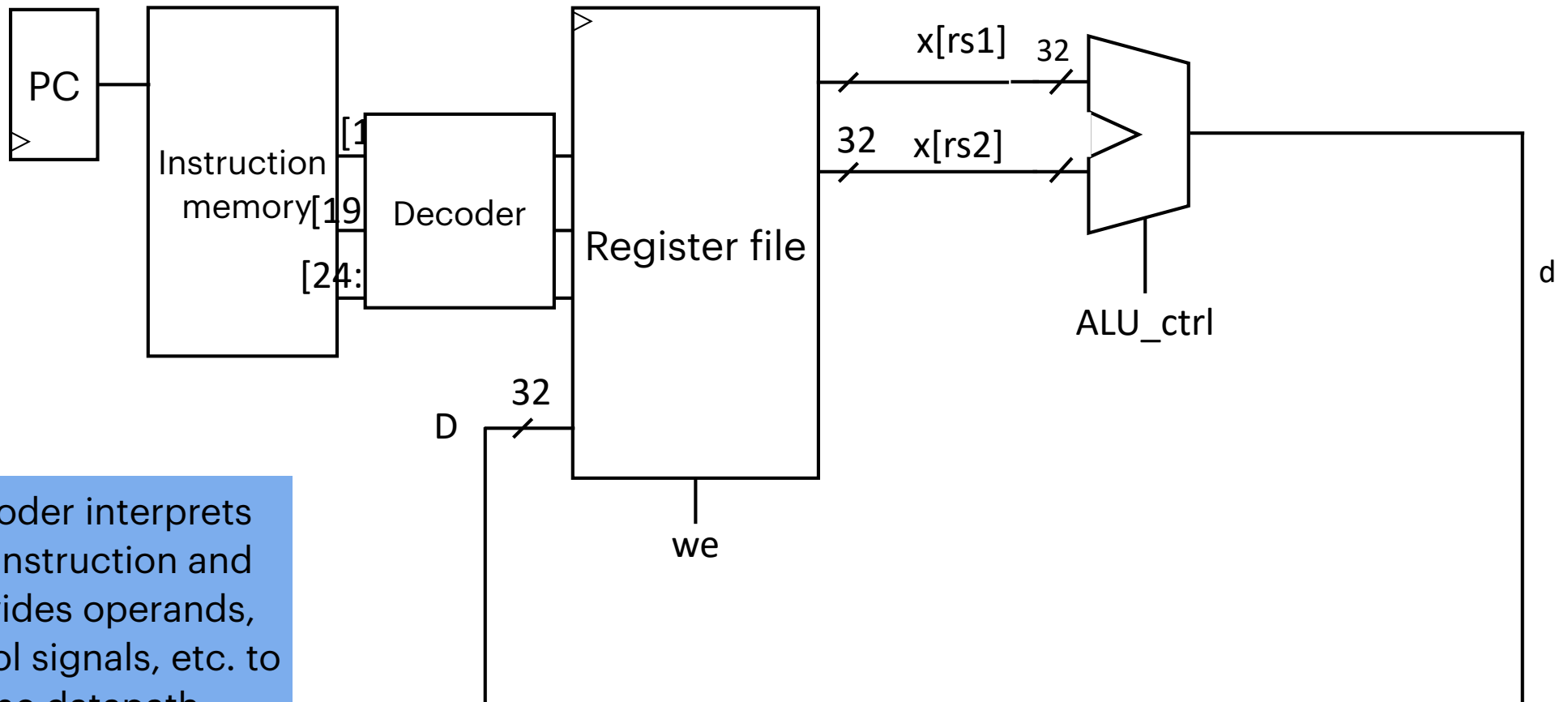 



Decoder interprets the instruction and provides operands, control signals, etc. to the datapath

Arithmetic & Logic

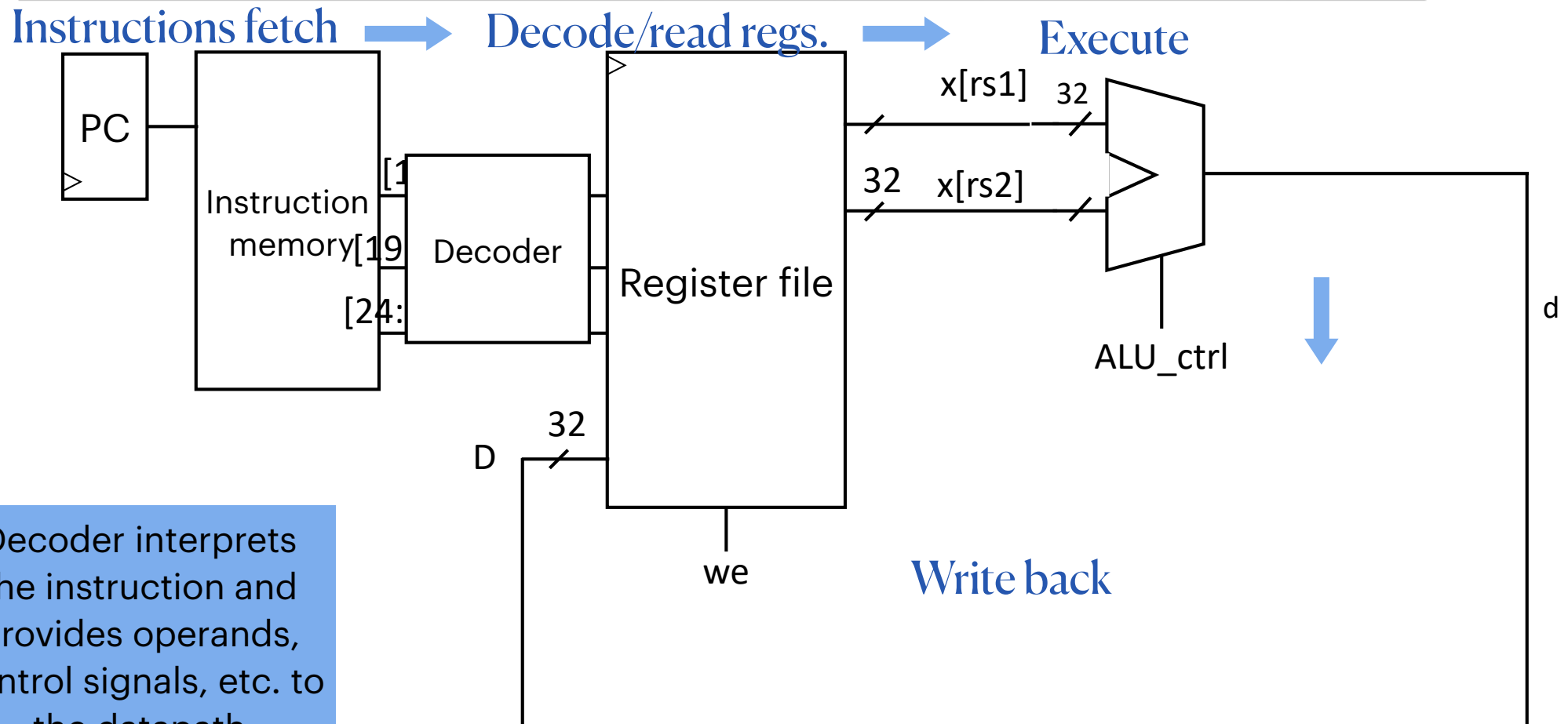 


Decoder interprets the instruction and provides operands, control signals, etc. to the datapath



Arithmetic & Logic

  


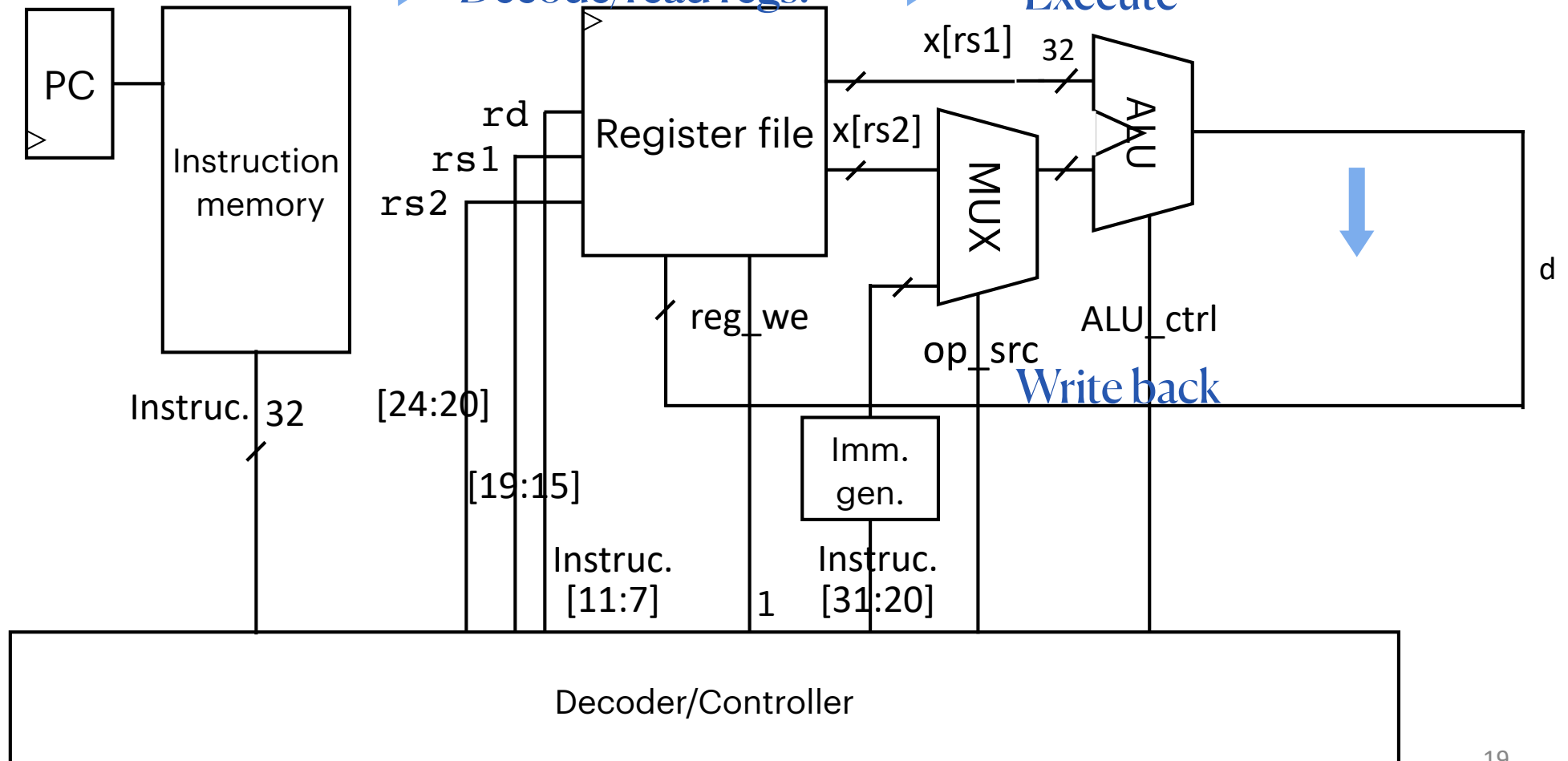
Instructions fetch → Decode/read regs. → Execute





Immediate Generation

  


Immediate Generation

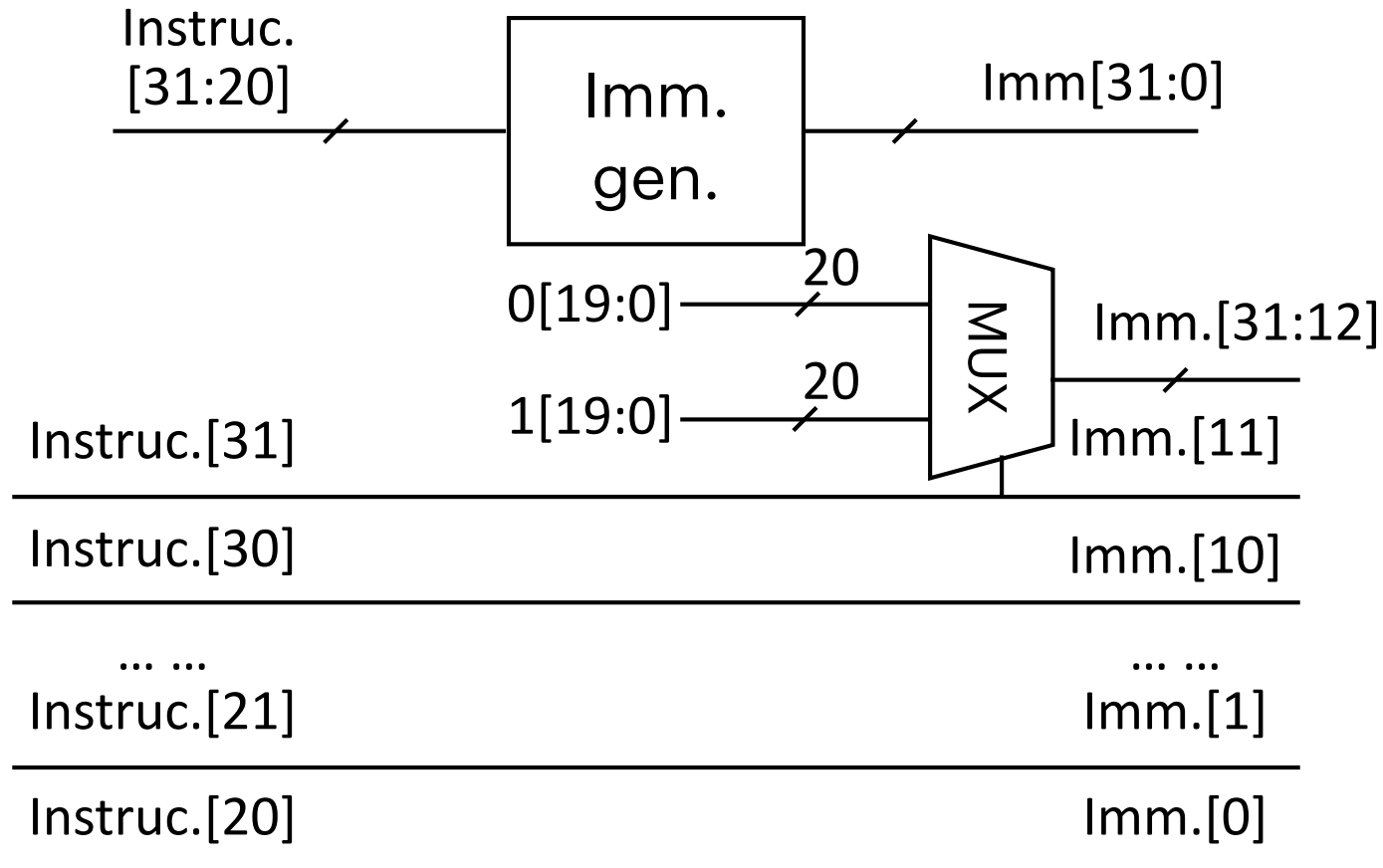 




Arithmetic & Logic

  

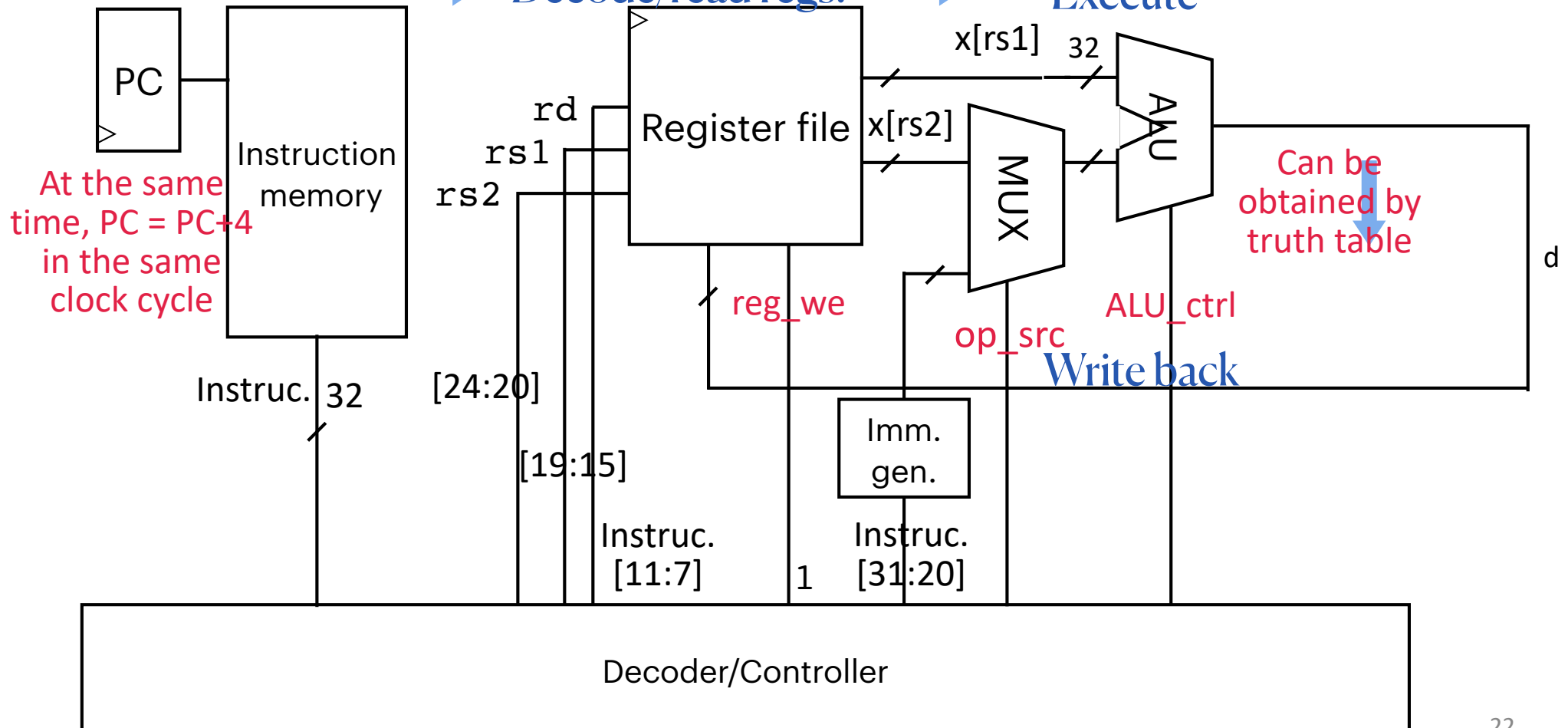
Instructions fetch → Decode/read regs. → Execute






I-type Load

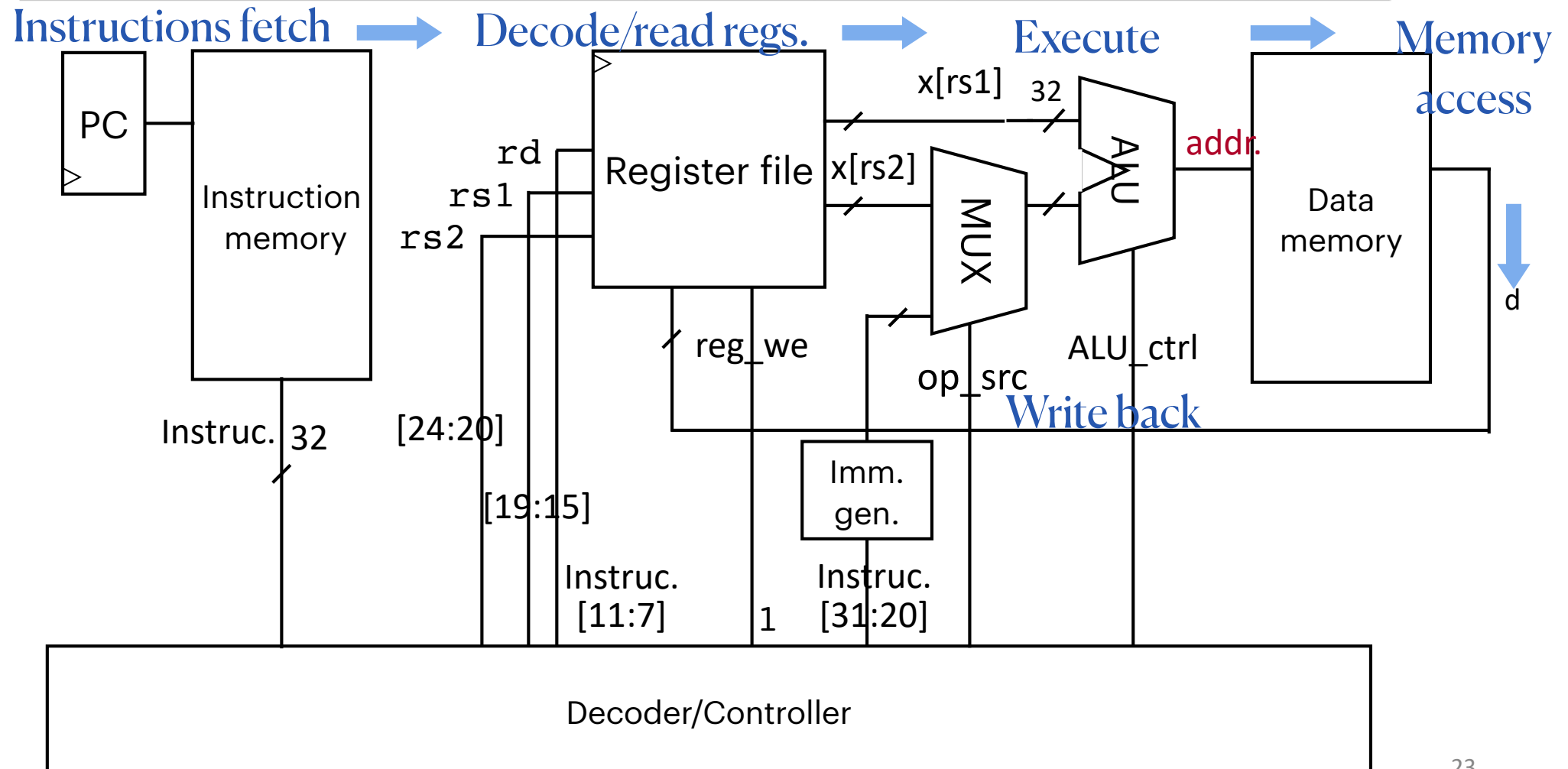  


I-type Load

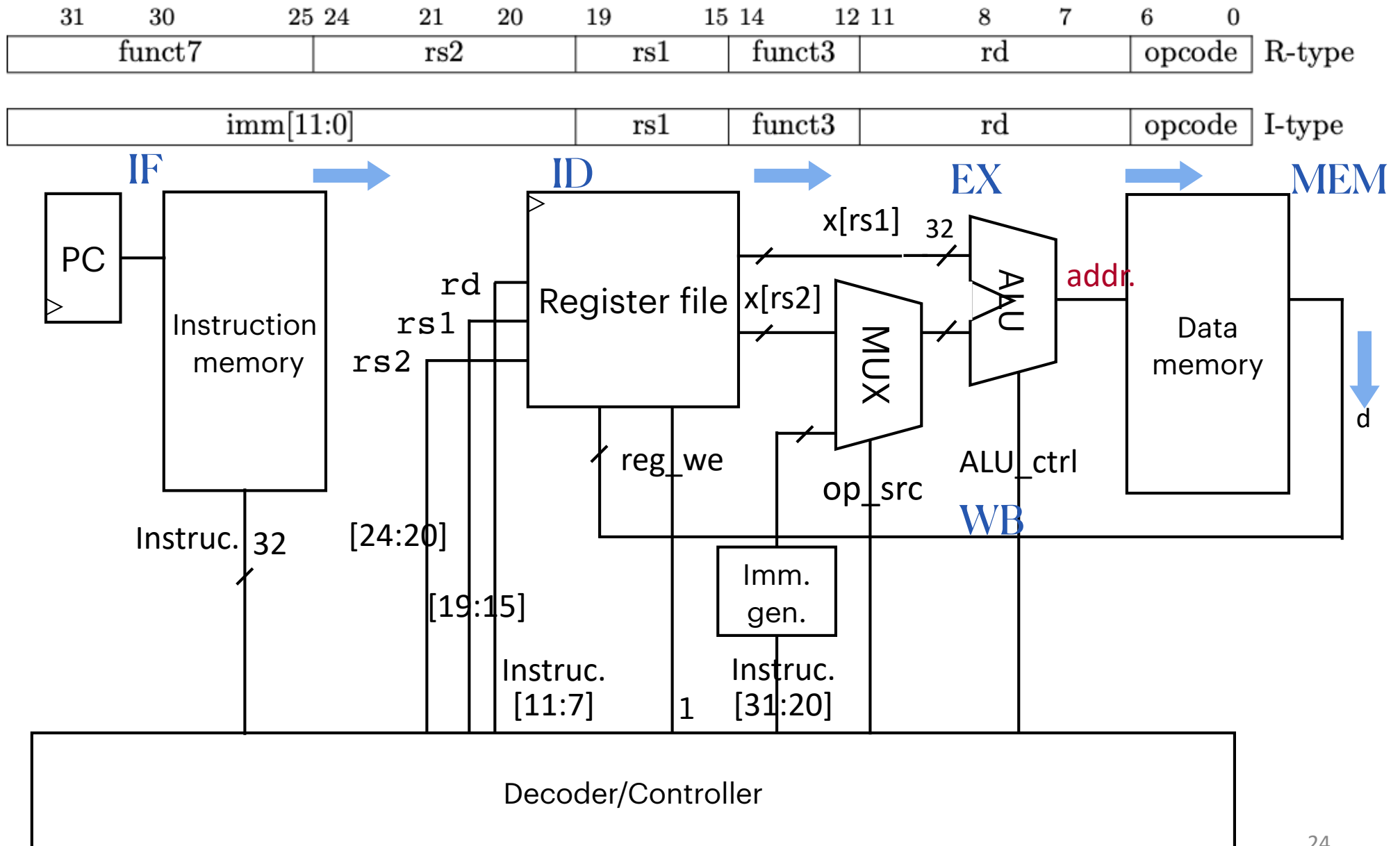


I-type Load

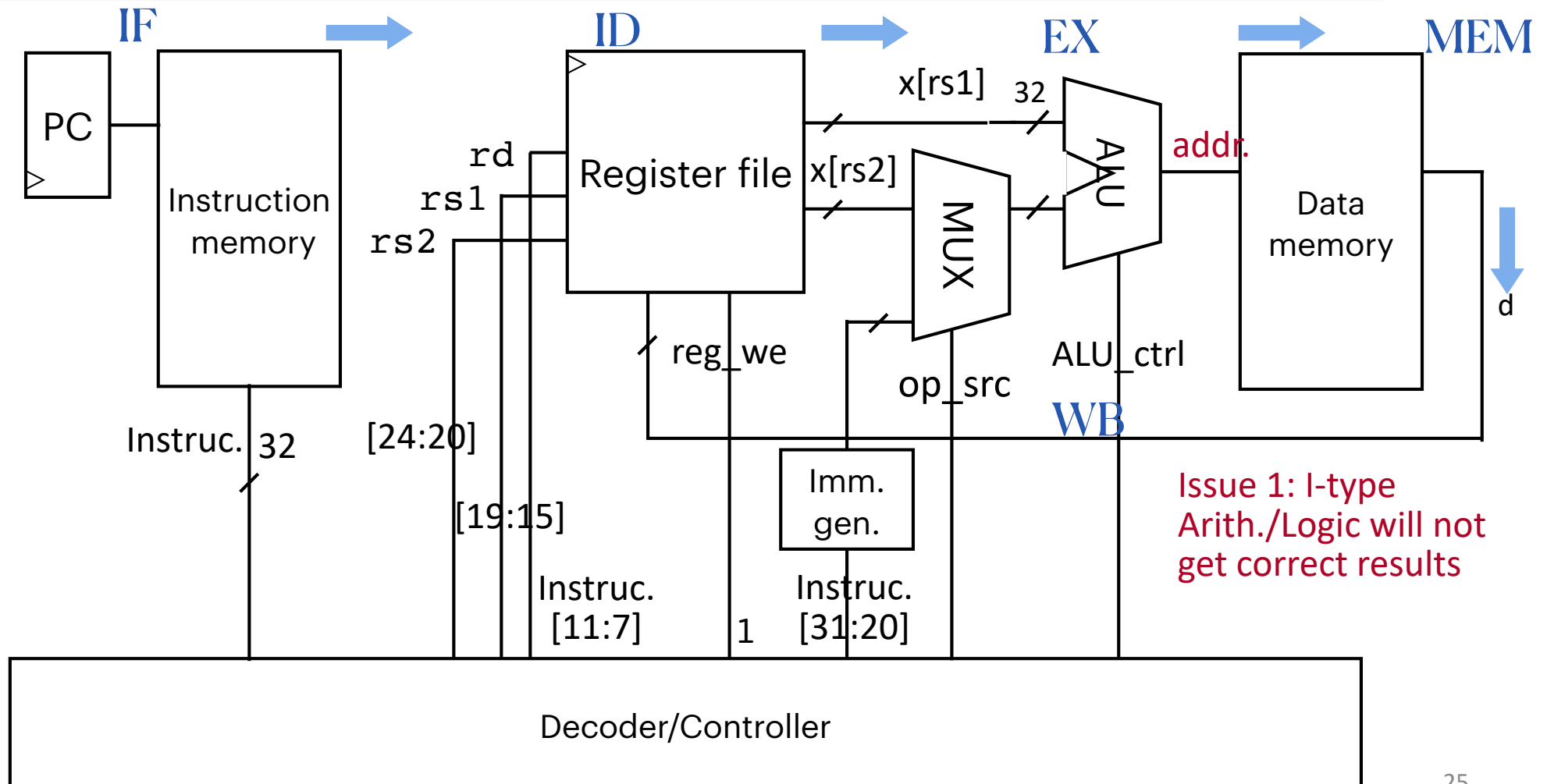  





I-type Load

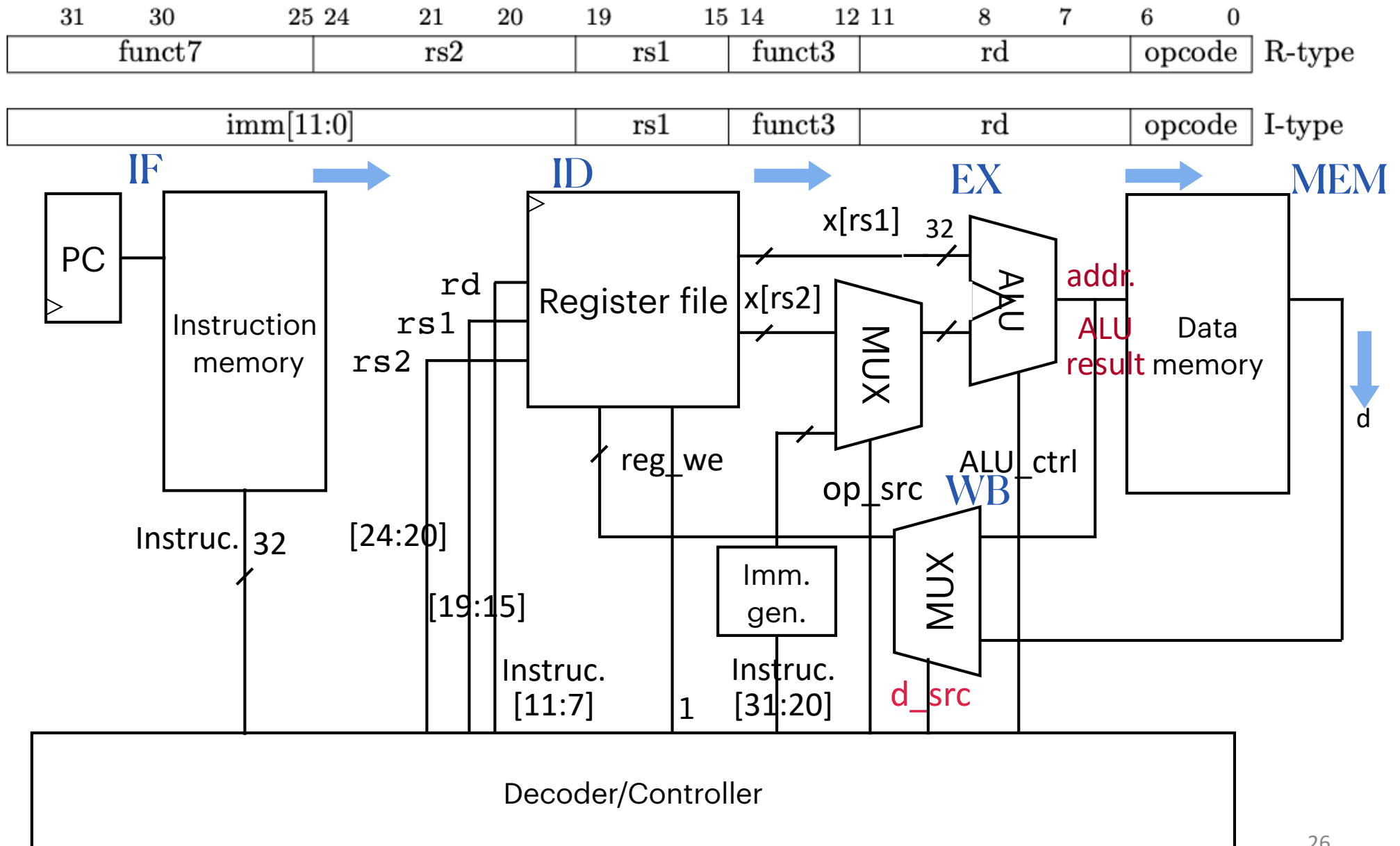





I-type Load

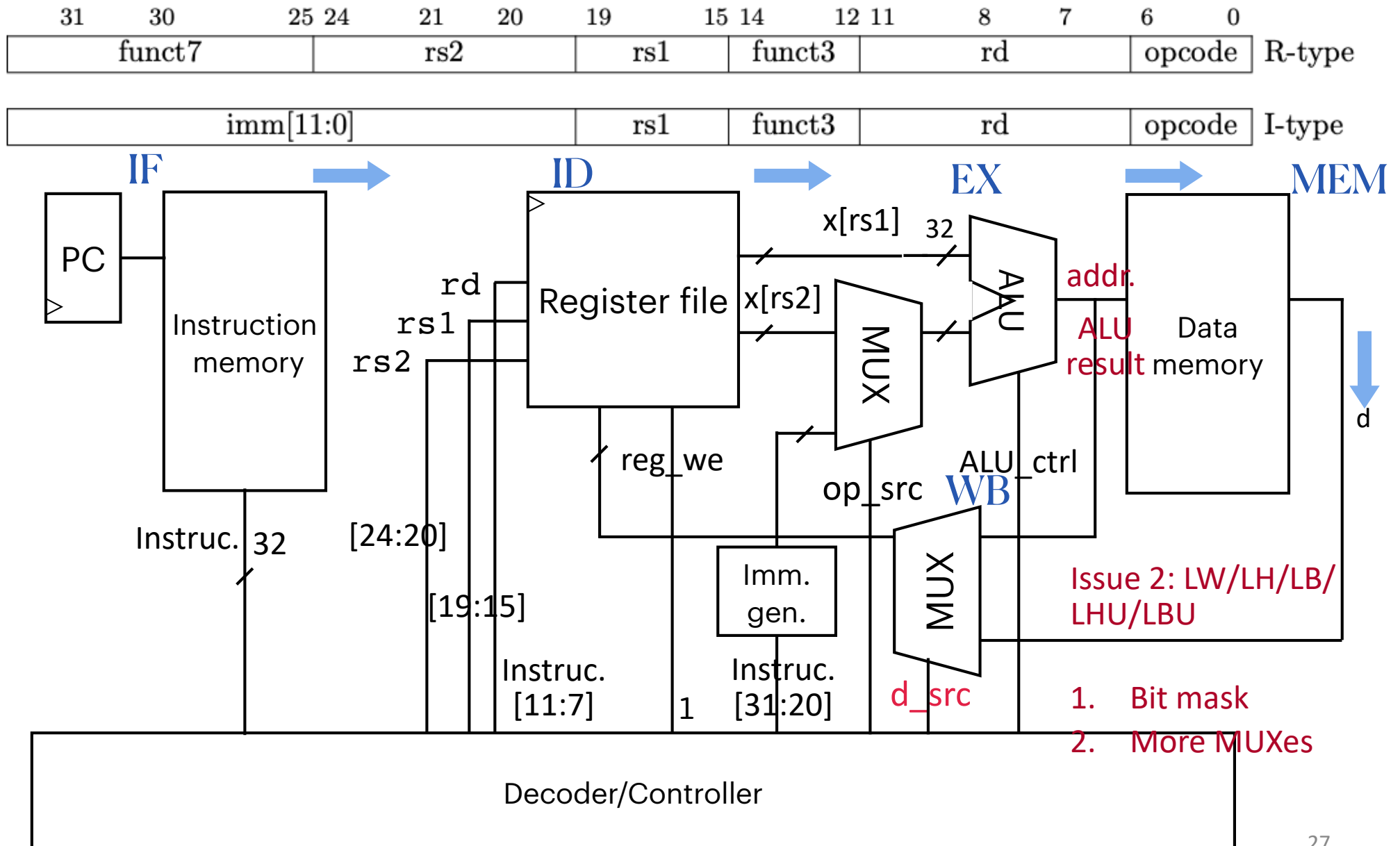


S-type Store

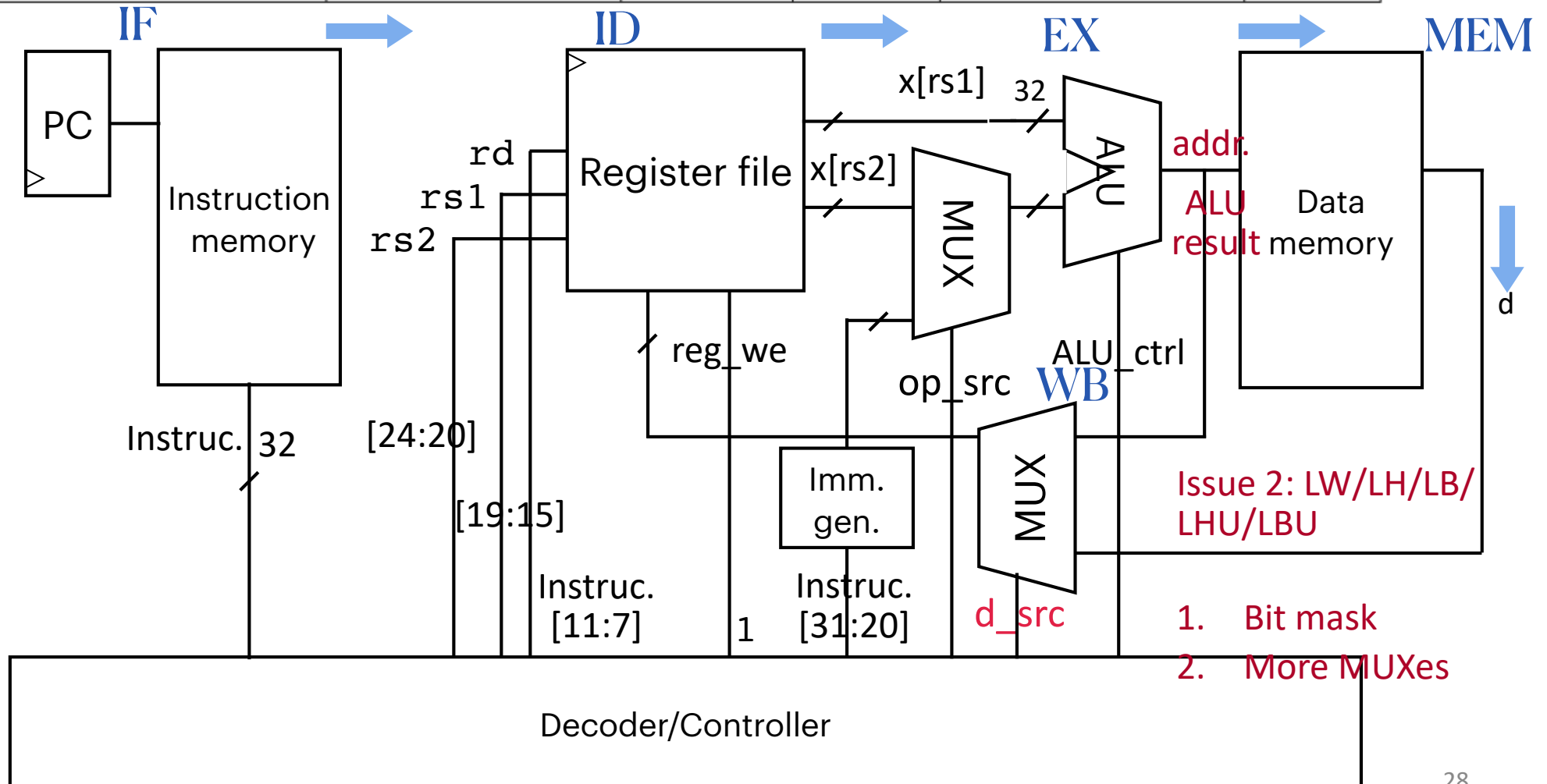   


S-type Store

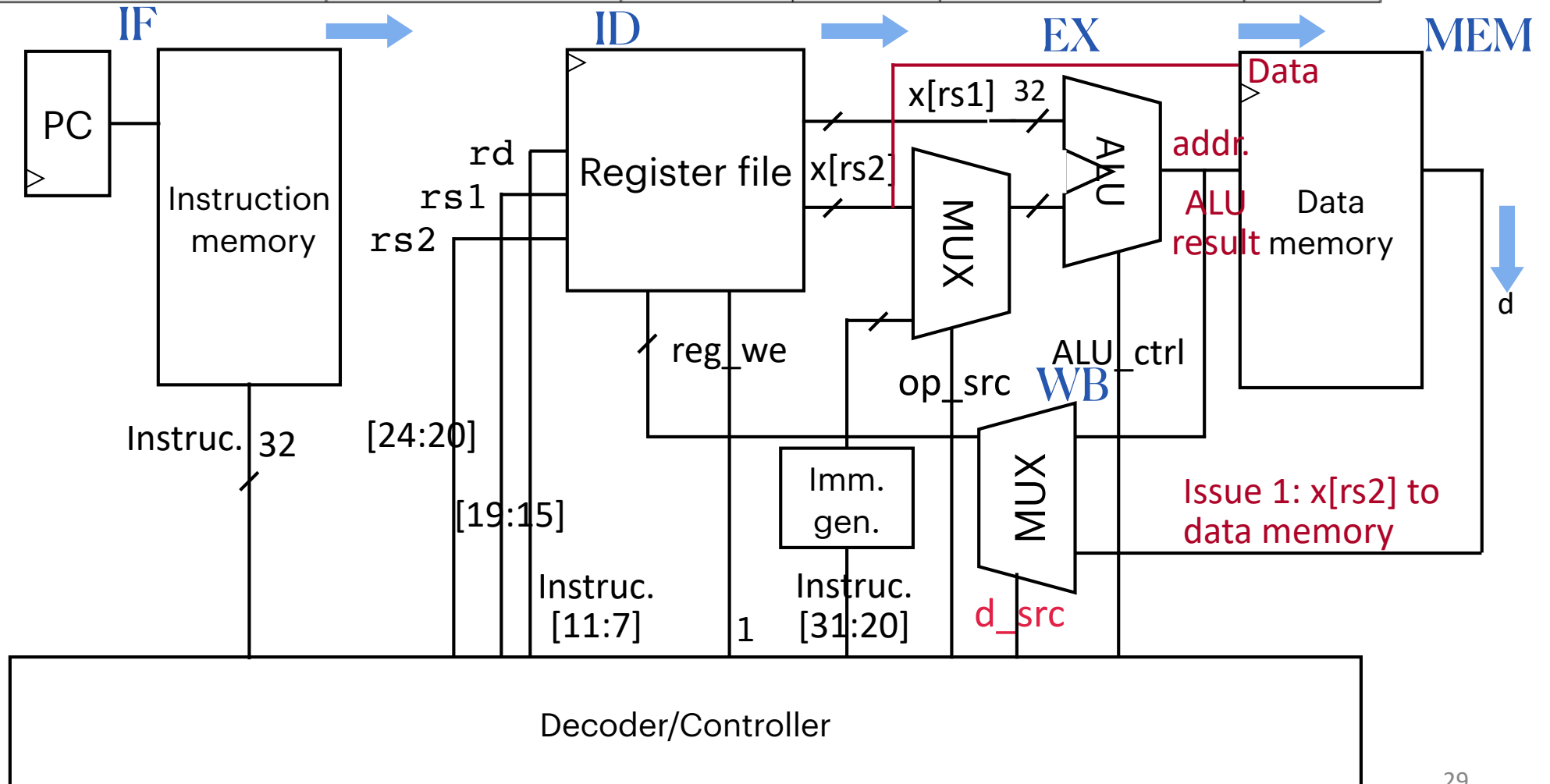   


S-type Store

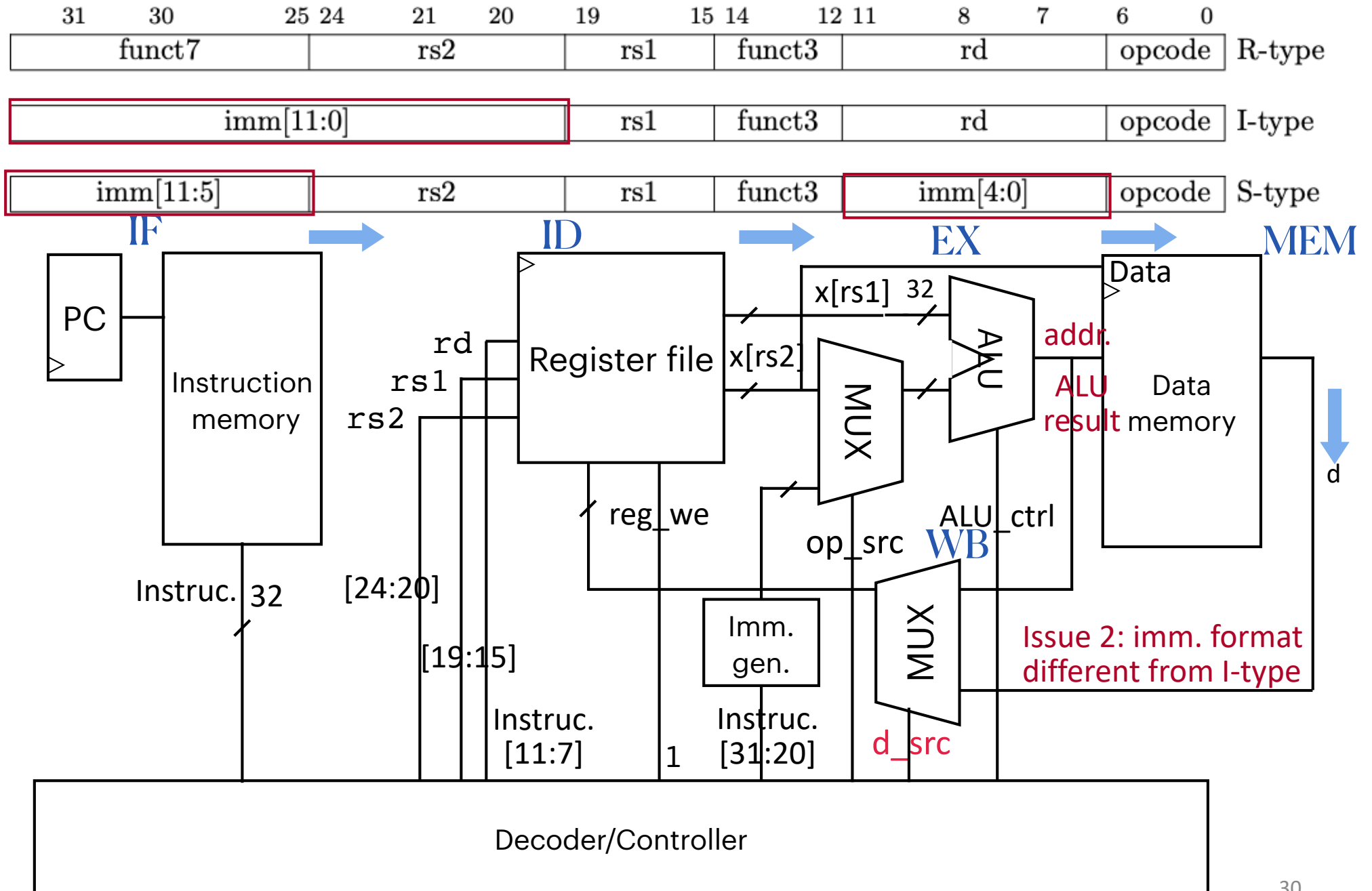


S-type Store

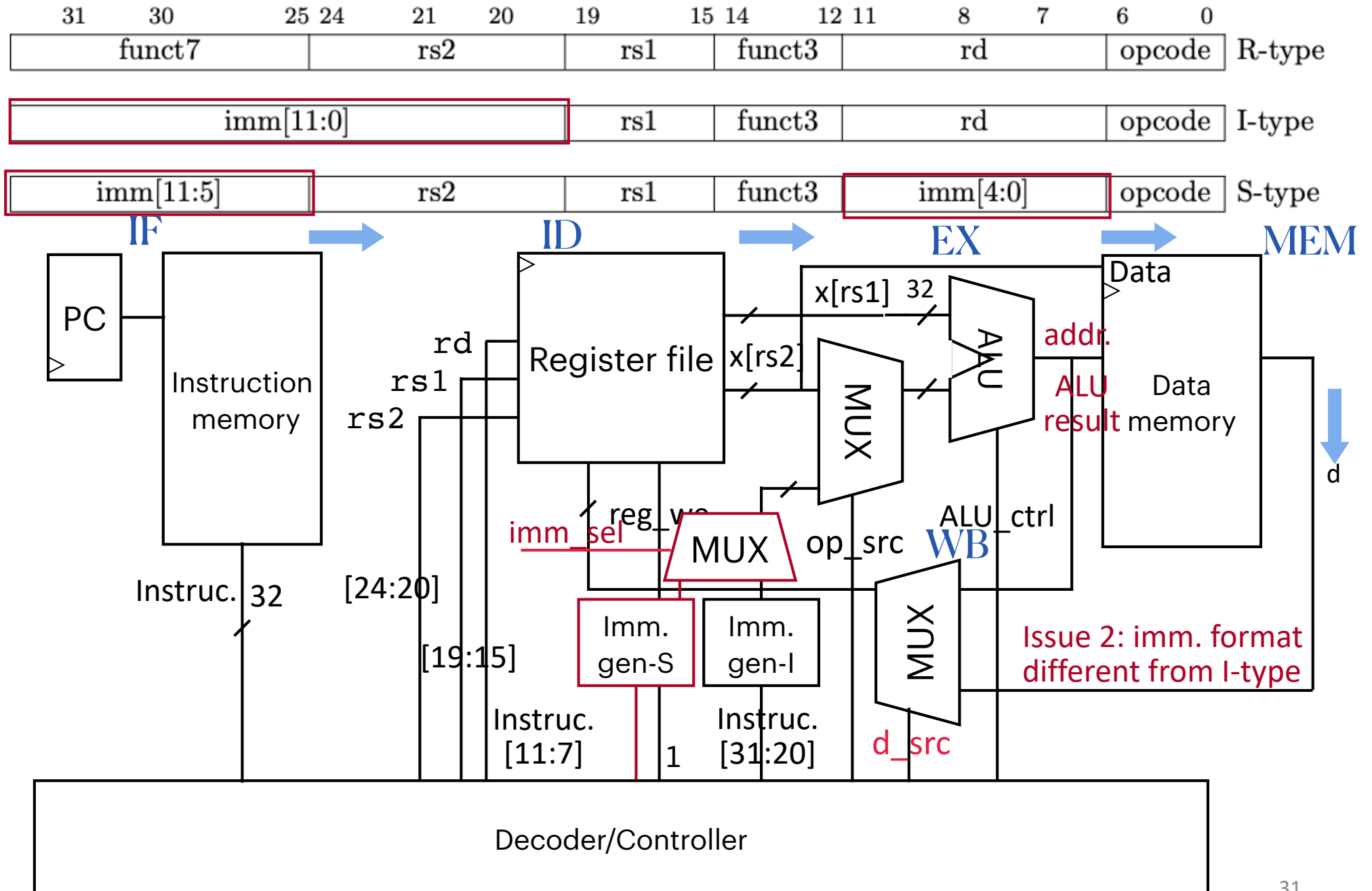


S-type Store

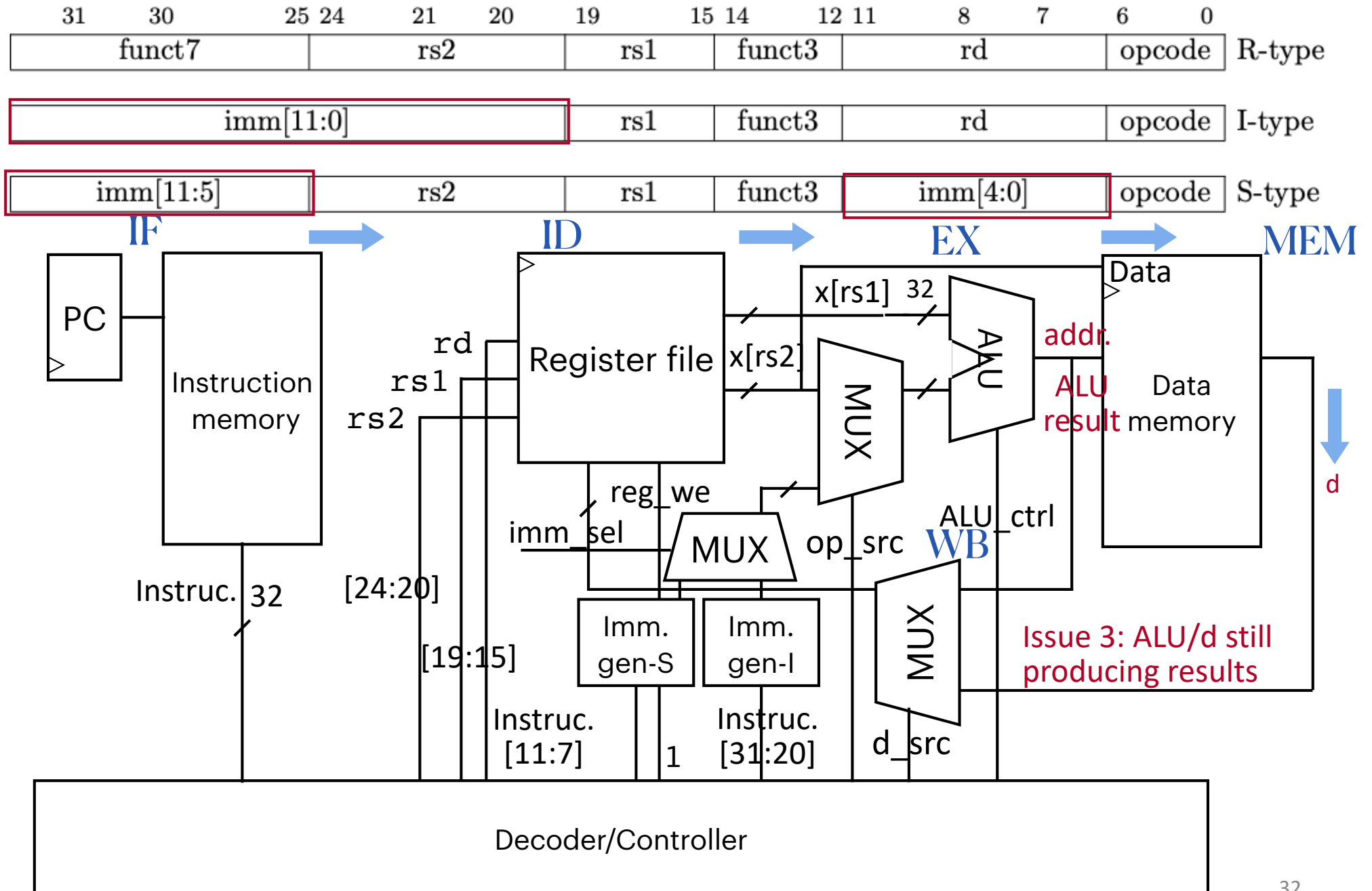

S-type Store


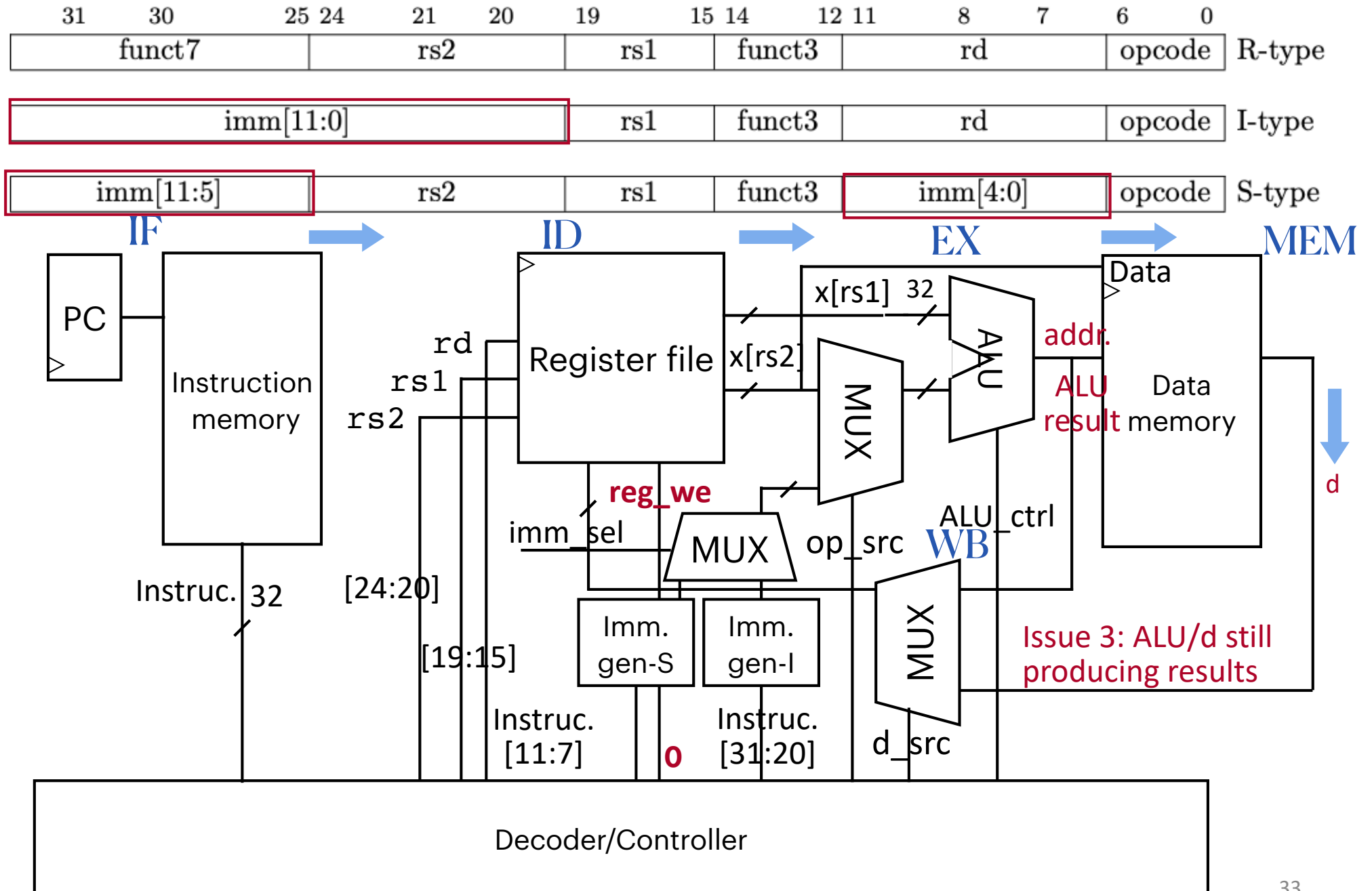




S-type Store


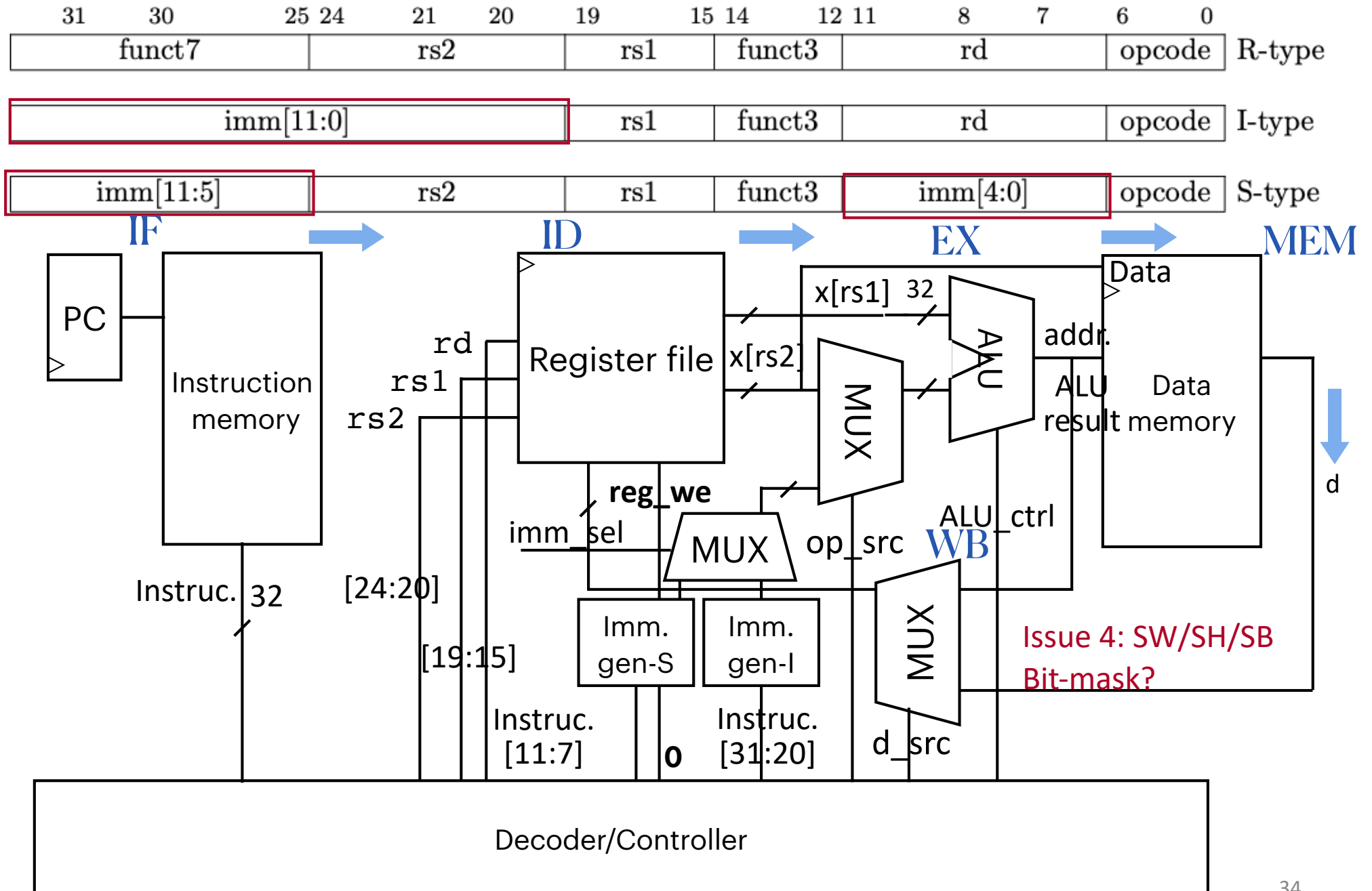




Take a Break!



	IF	ID	EX	MEM	WB
R-type					
I-type arith. & logic					
I-type load					
S-type store					

 
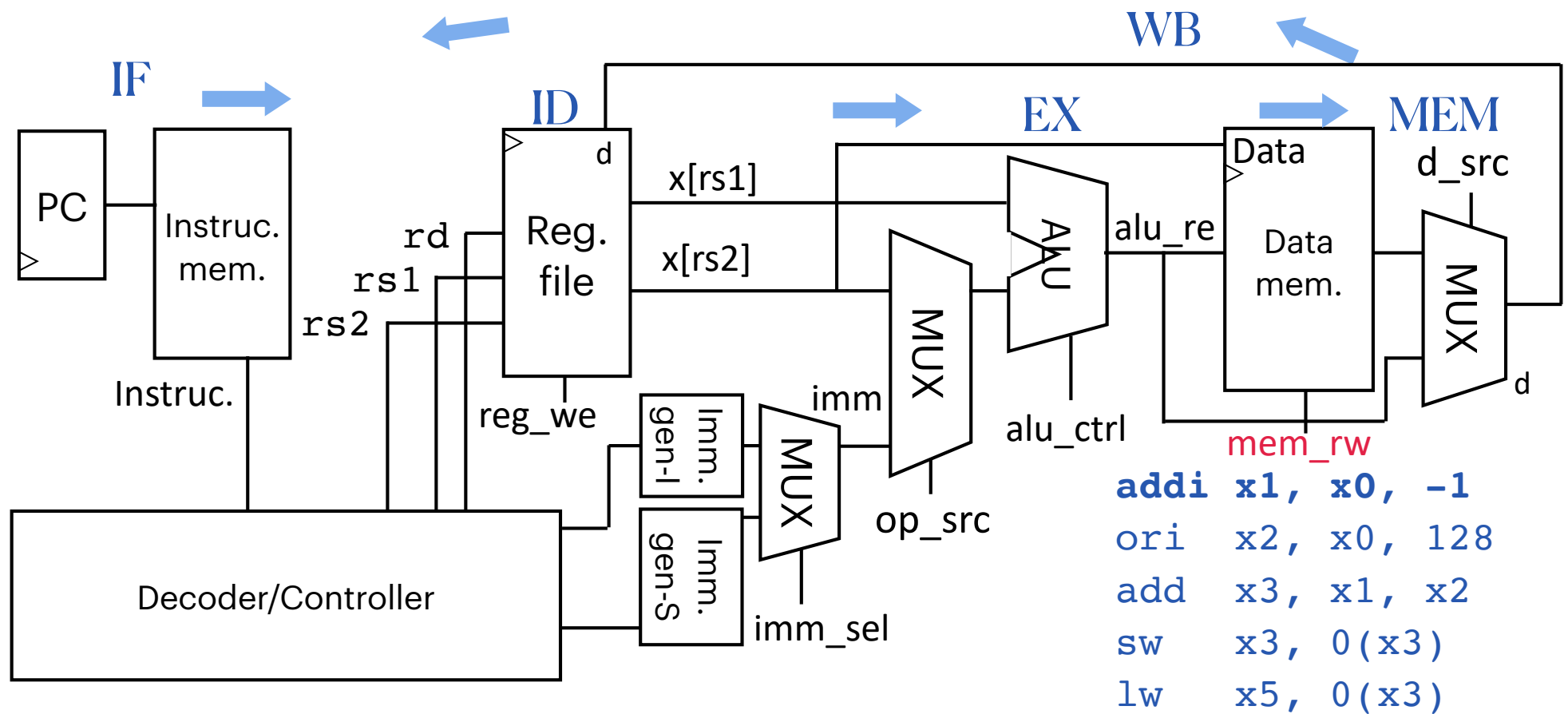


 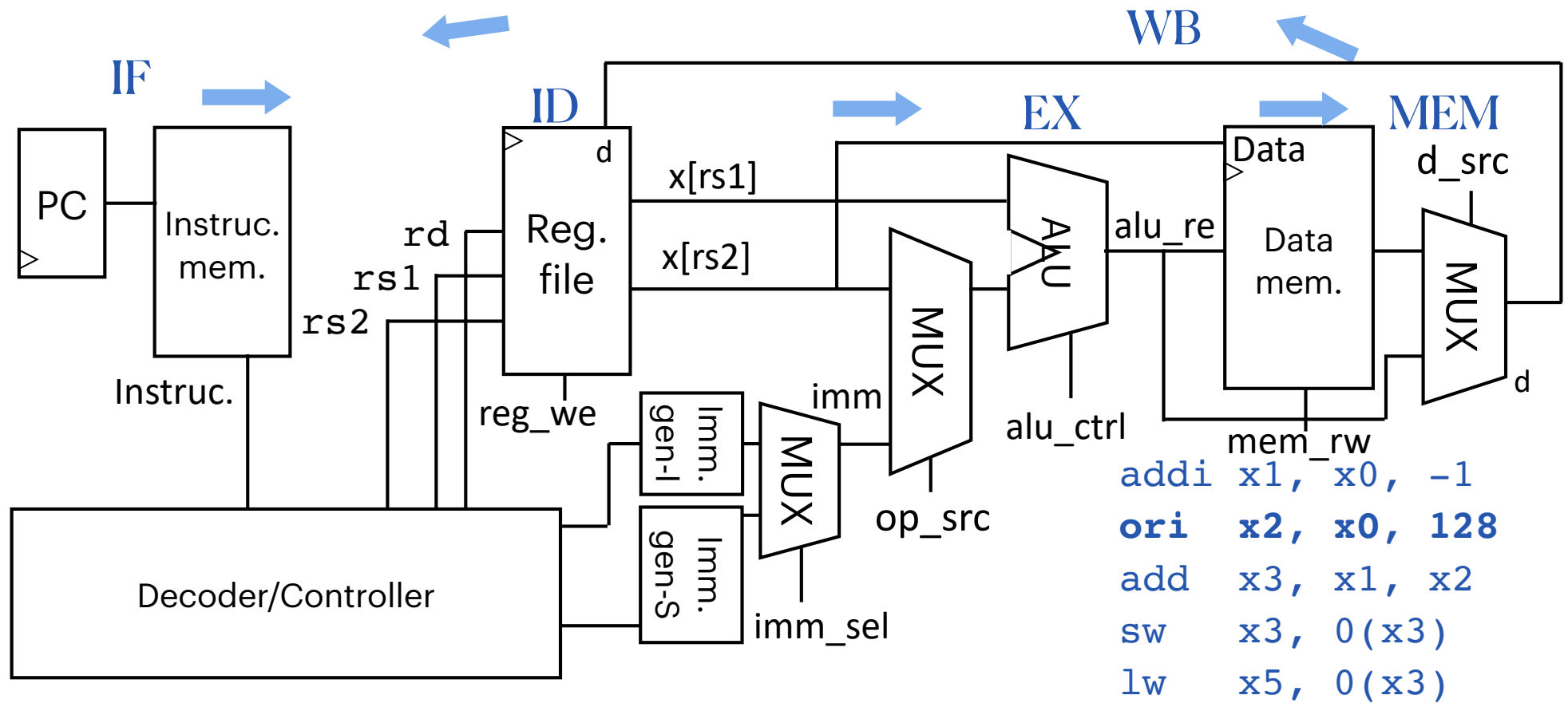

 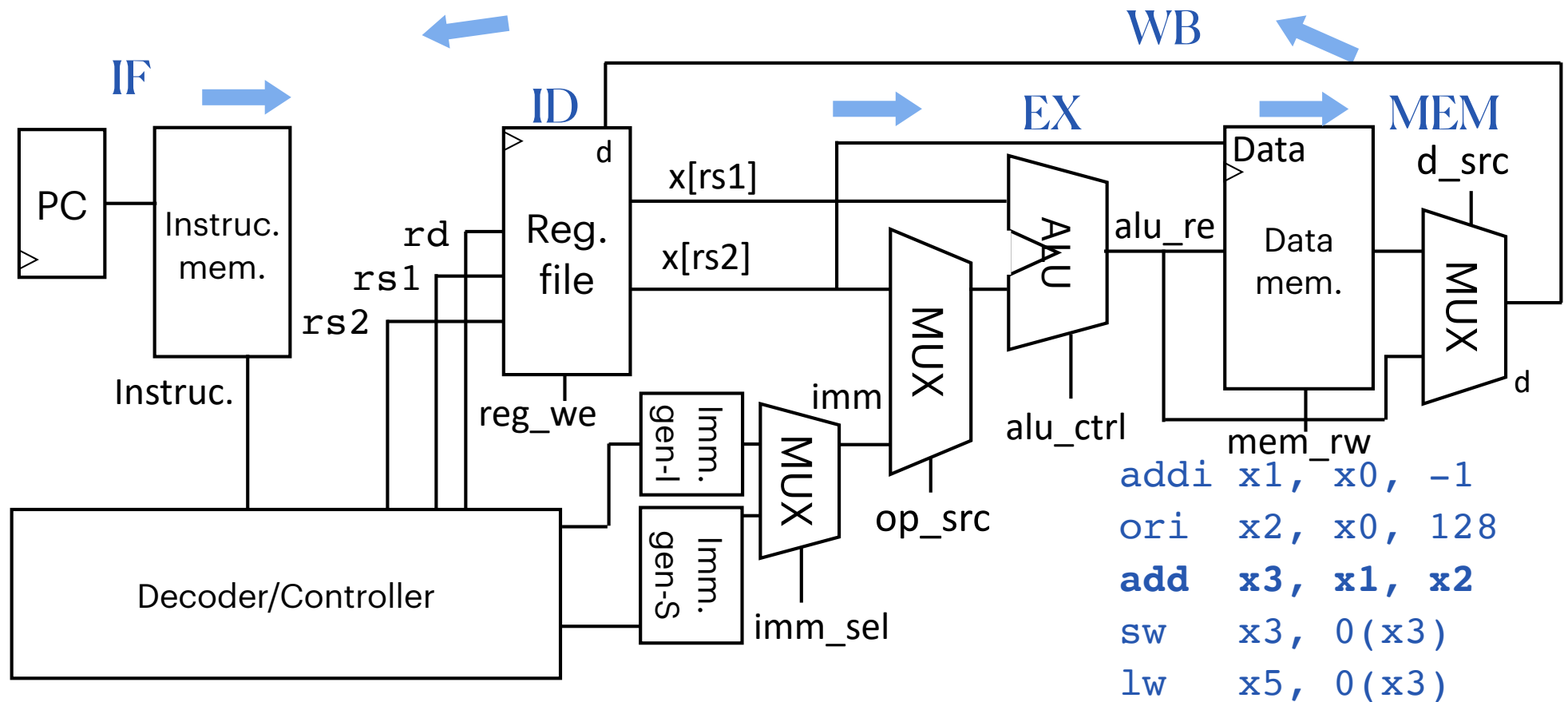


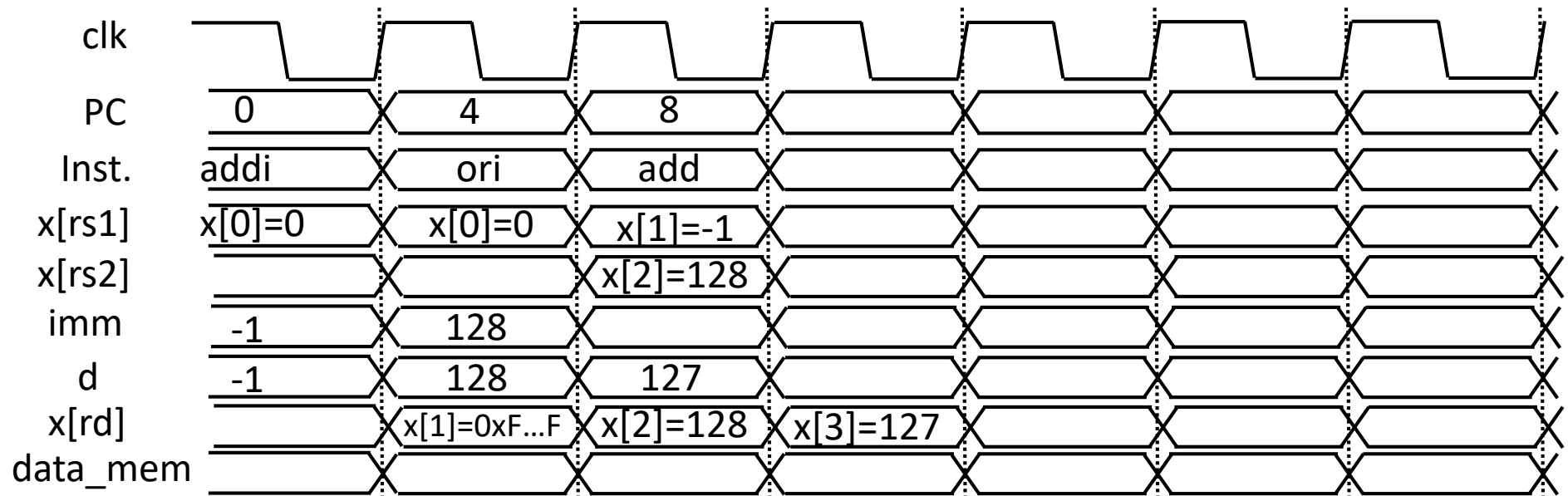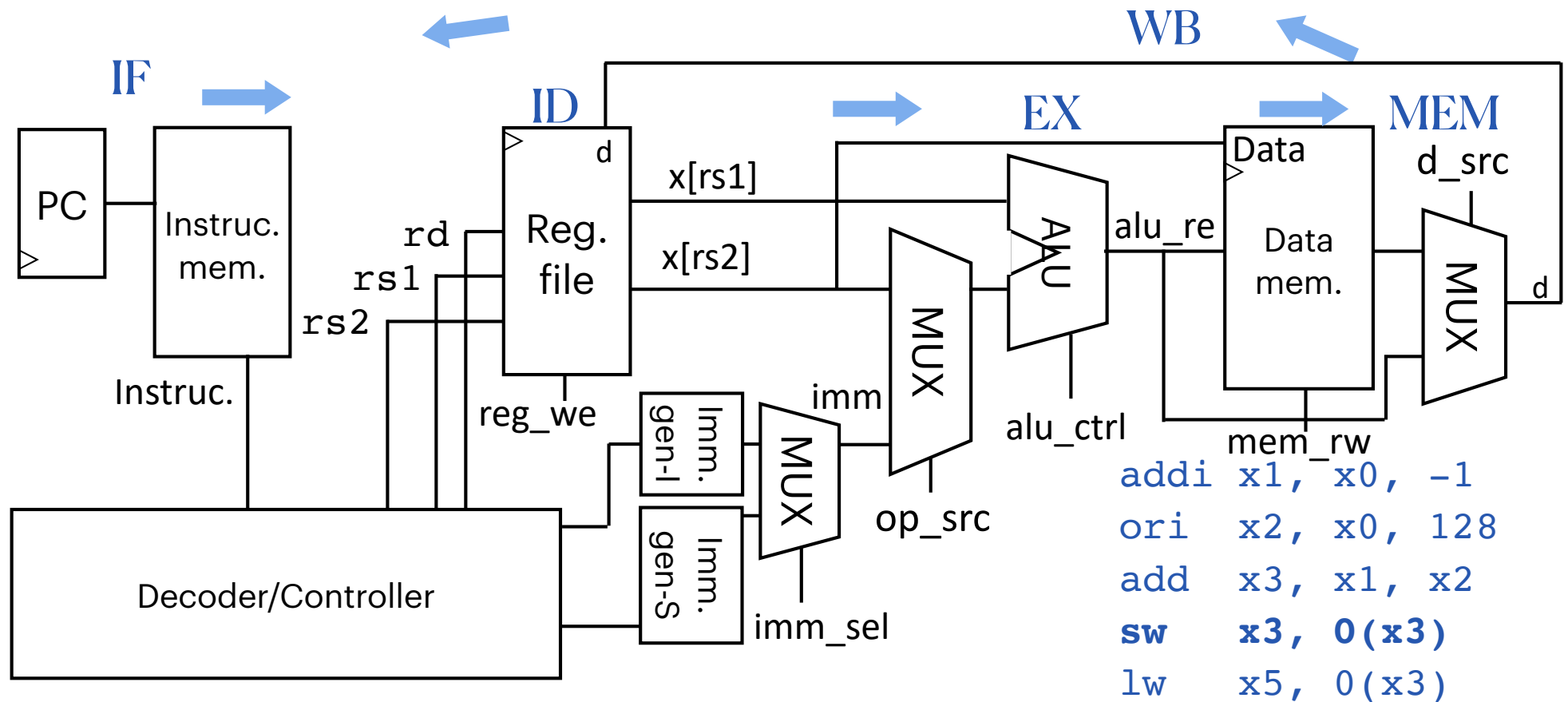

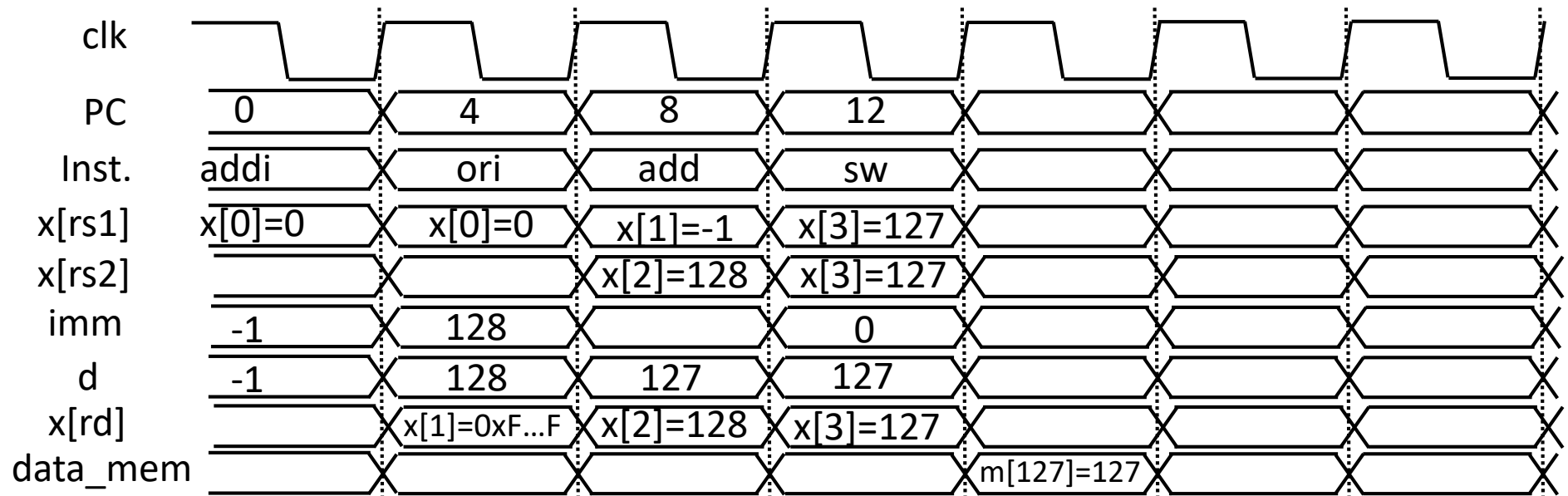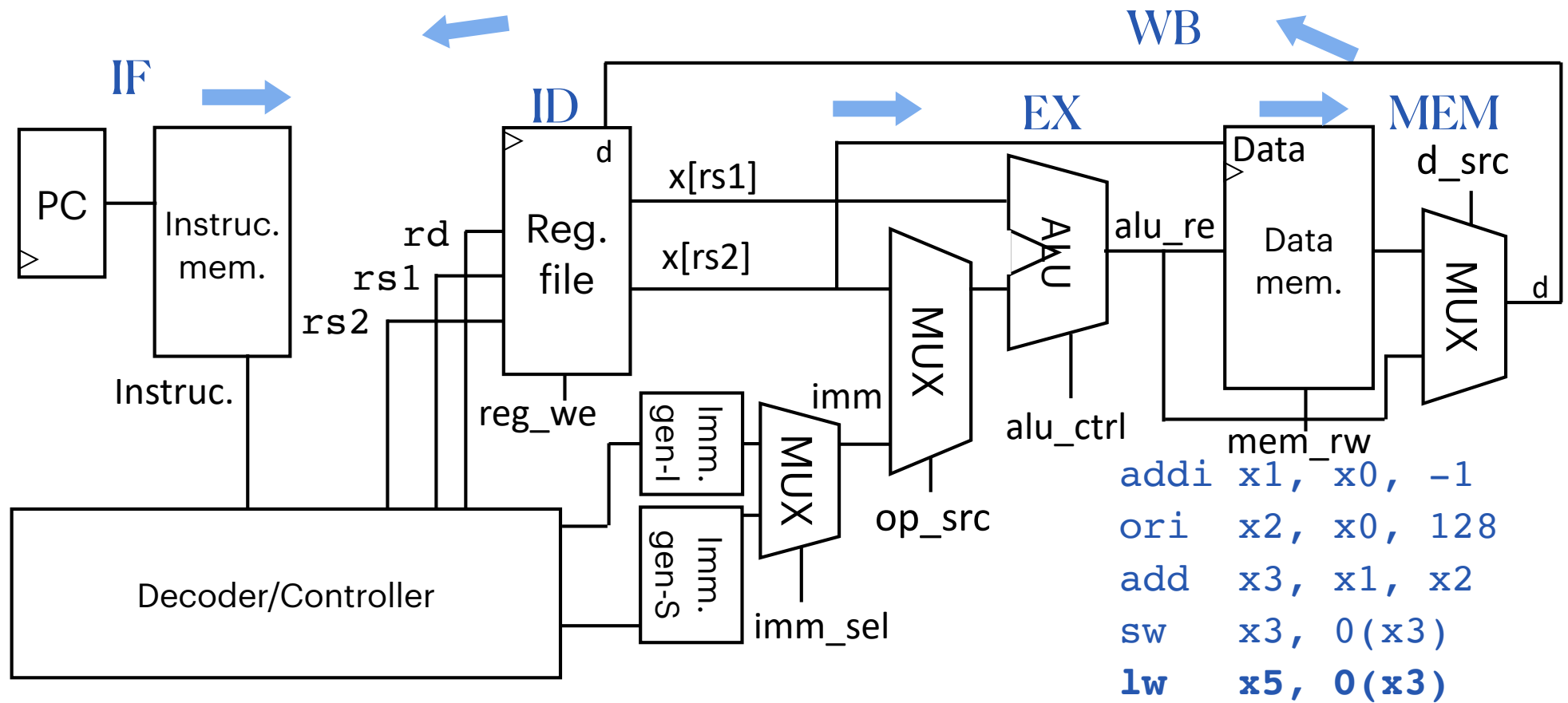


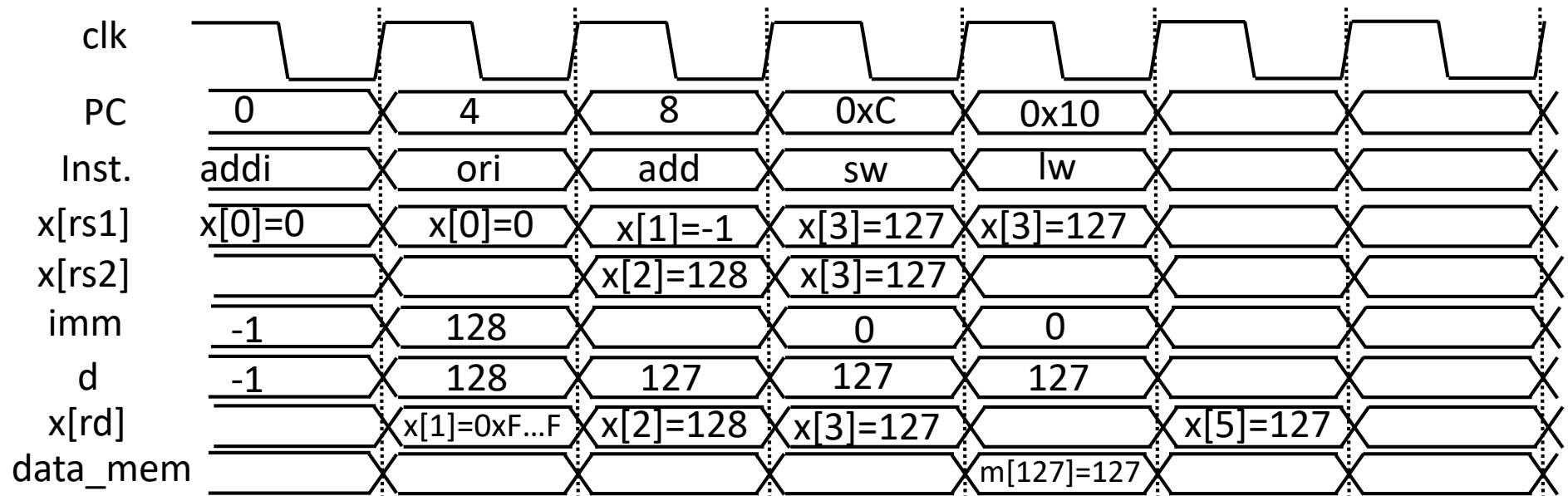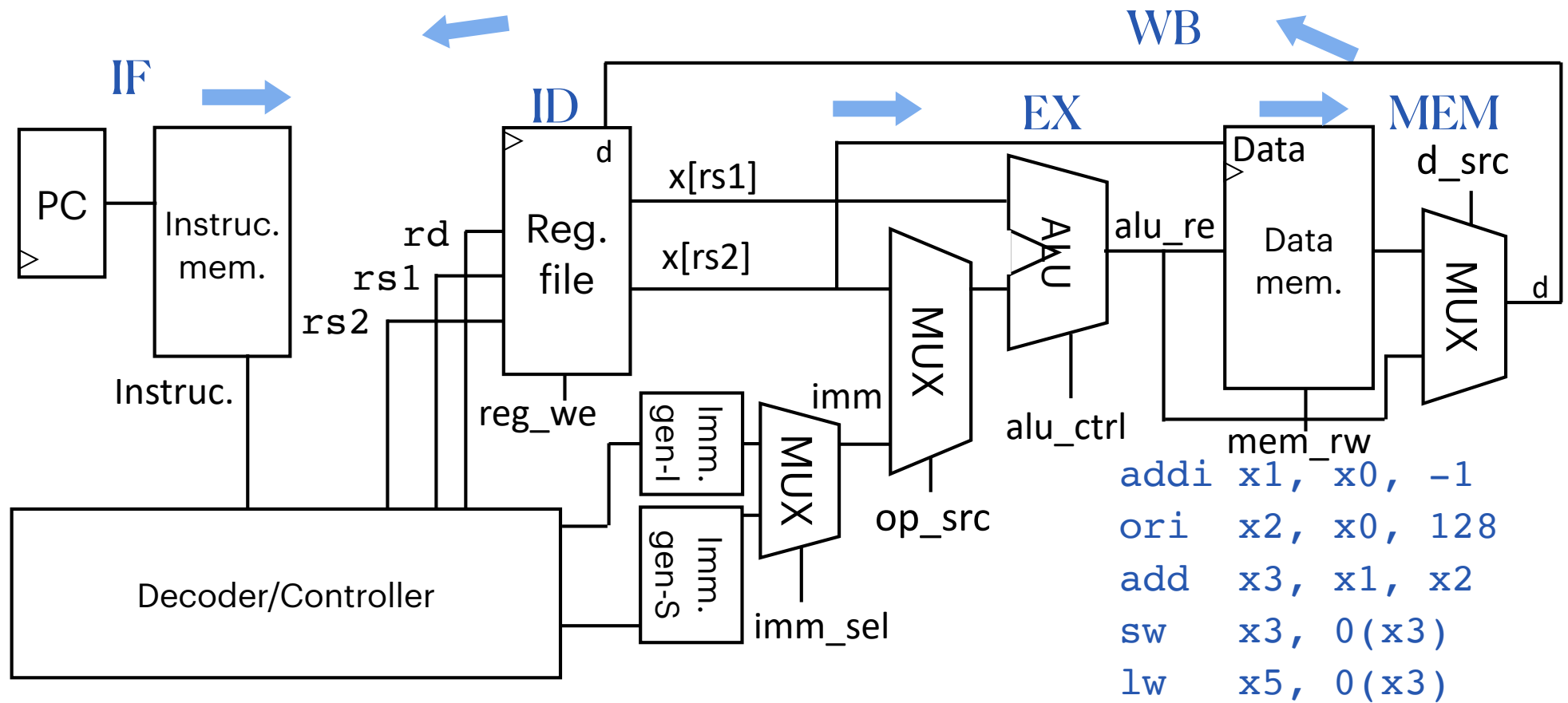

Controller as FSM

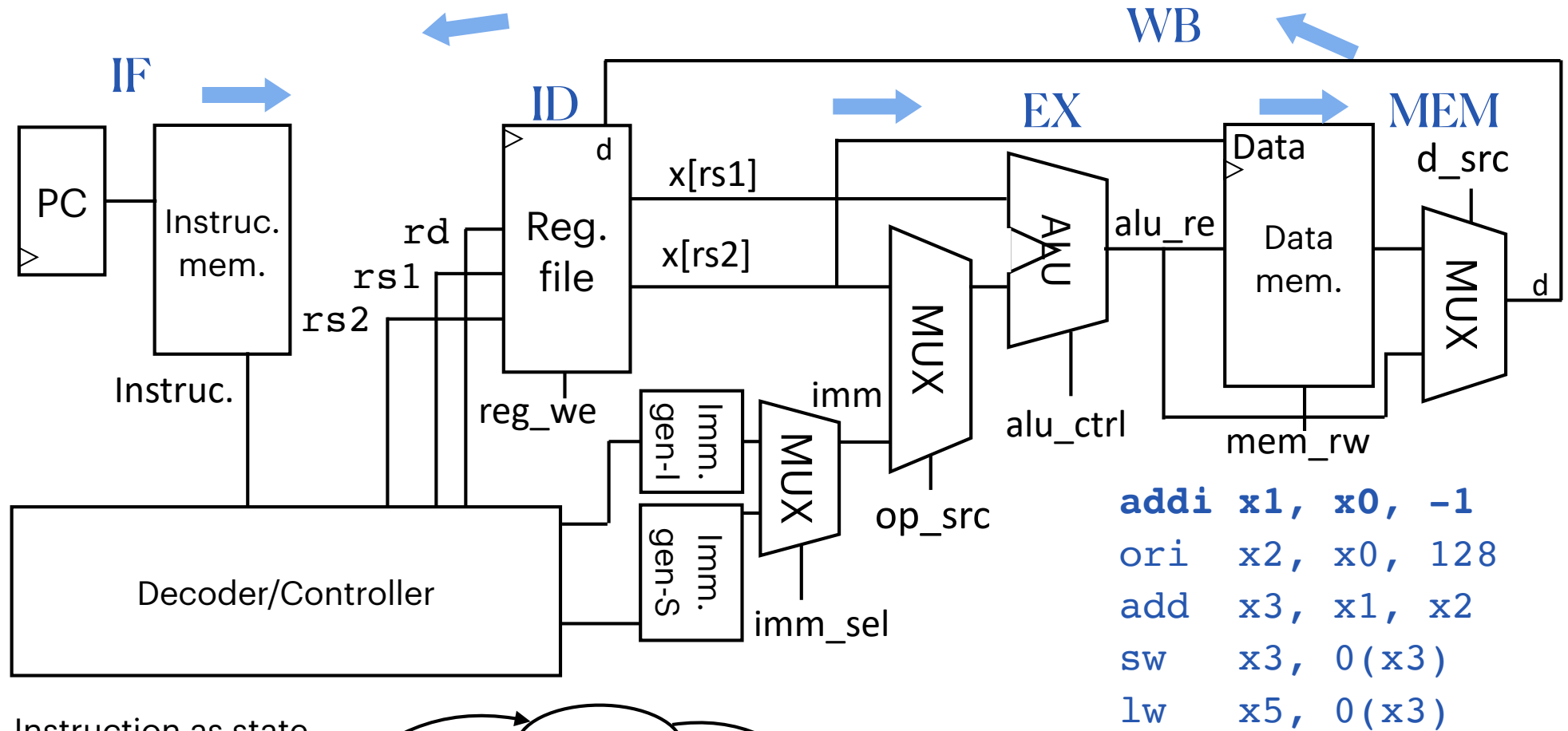


Instruction as state

 

Next state =

Output = control signals

Controller as FSM

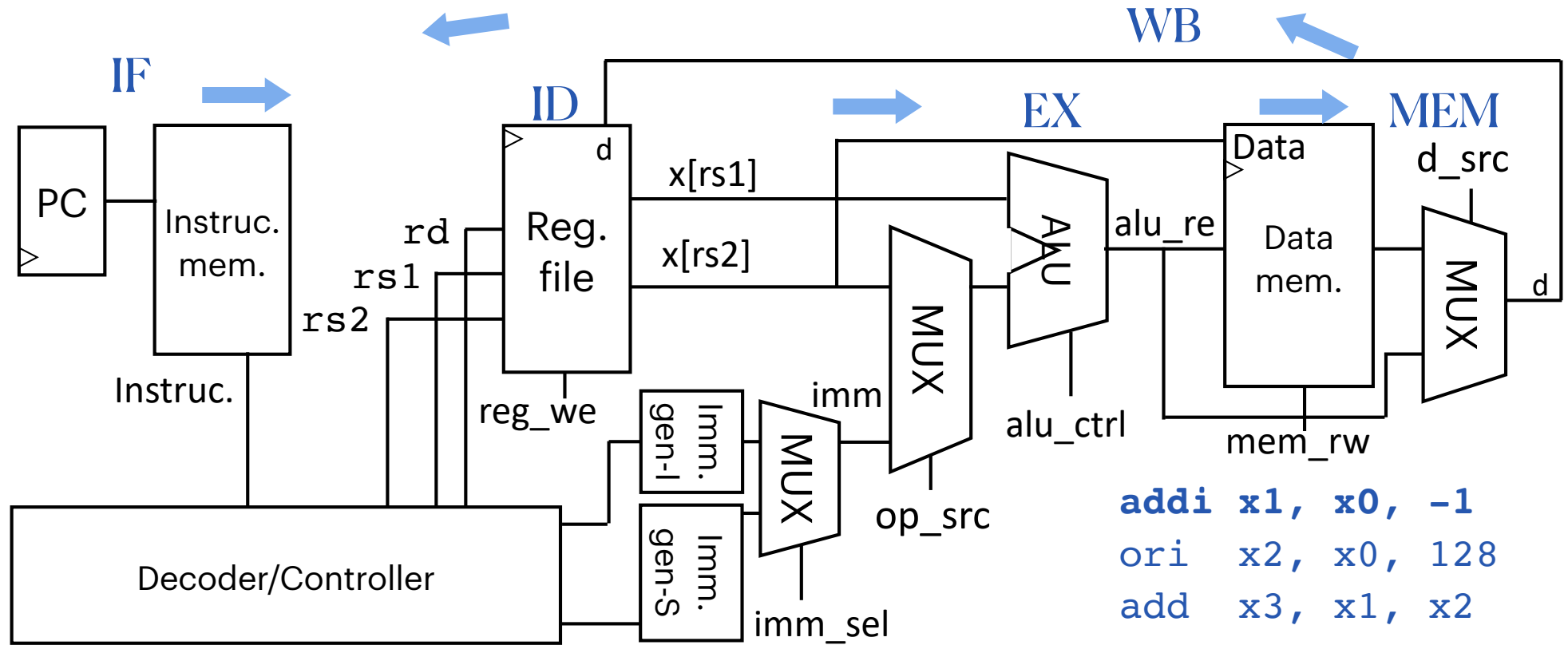


```
addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
```

Next state =

Output = control signals

	addi				
reg_we					
mem_rw					
alu_ctrl					
imm_sel					
d_src					
op_src					

Controller as FSM

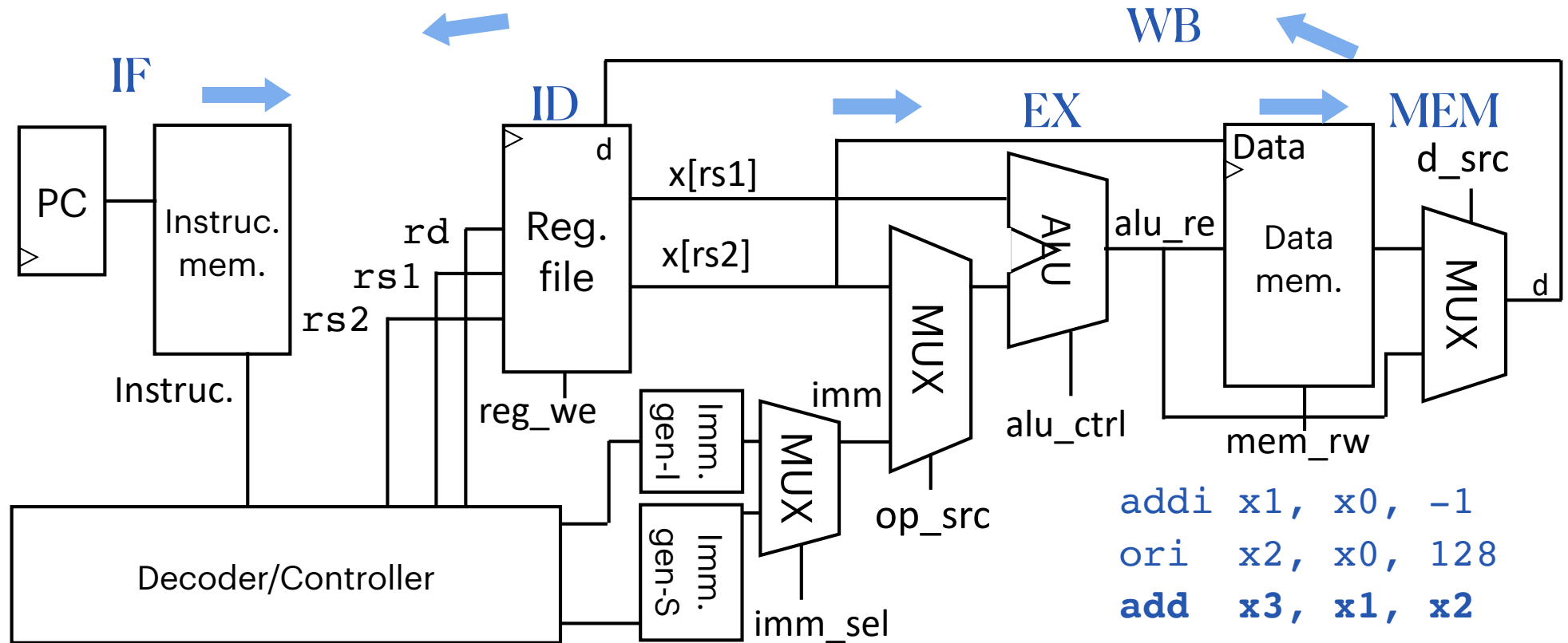

```


addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
    
```

Next state =

Output = control signals

	addi	add			
reg_we	1				
mem_rw	R				
alu_ctrl	add				
imm_sel	I				
d_src	alu				
op_src	imm				

Controller as FSM

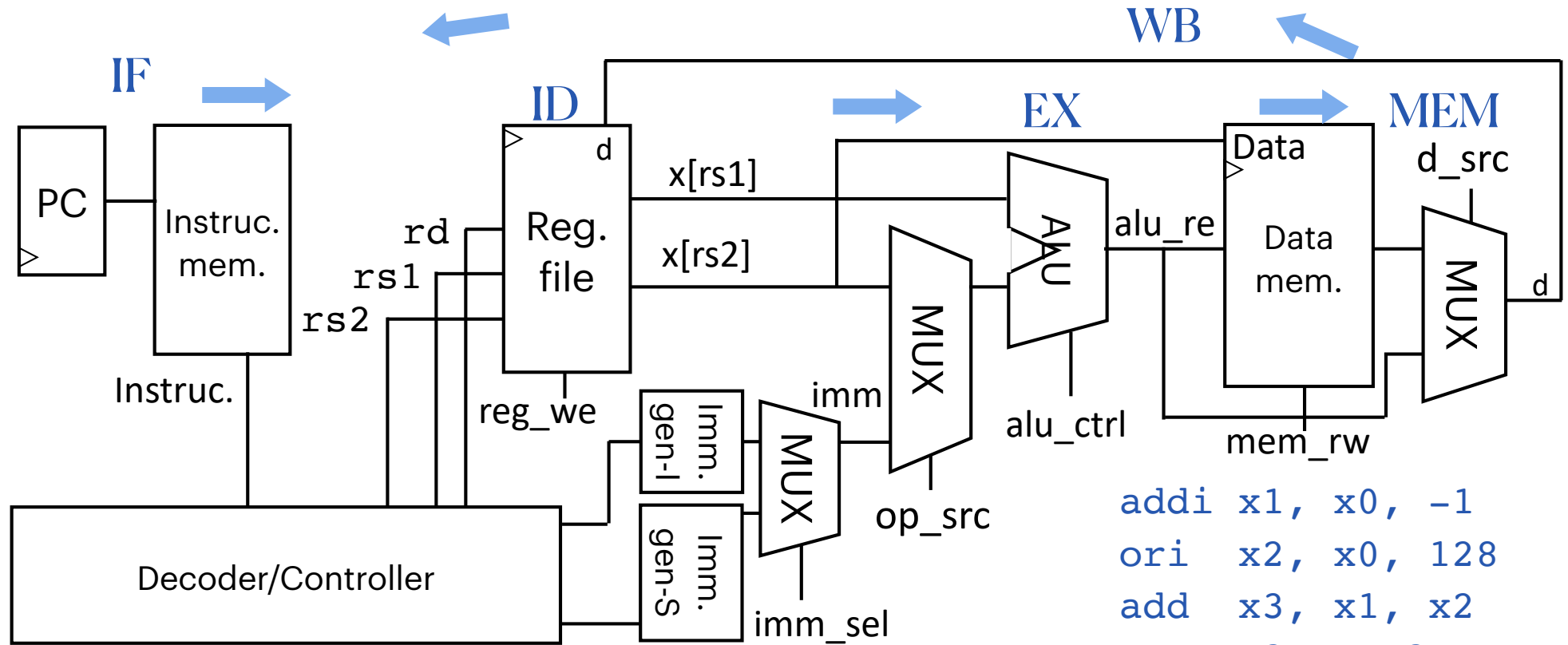

```


addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
    
```

	addi	add	sw	
reg_we	1	1		
mem_rw	R	R		
alu_ctrl	add	add		
imm_sel	I	I		
d_src	alu	alu		
op_src	imm	reg		

Next state =

Output = control signals

Controller as FSM

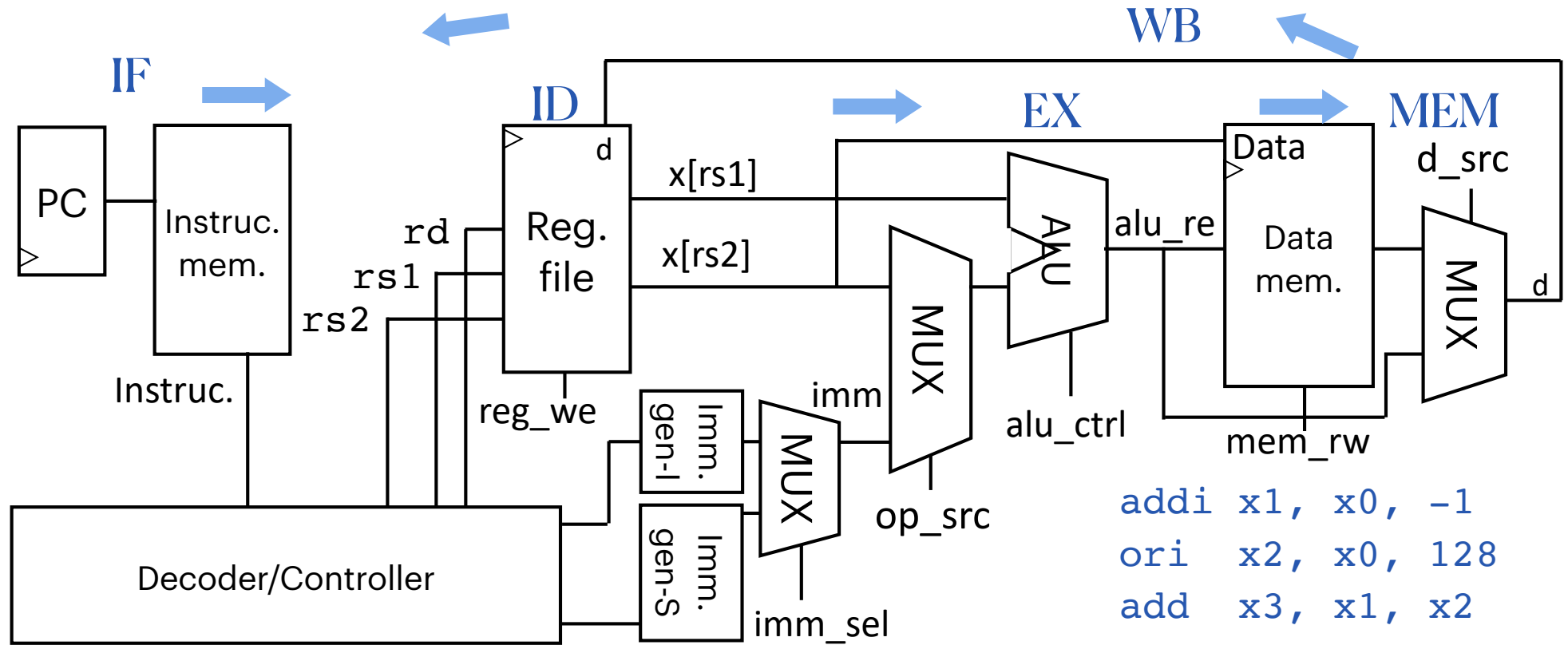


```
addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
```

	addi	add	sw	lw
reg_we	1	1	0	
mem_rw	R	R	W	
alu_ctrl	add	add	add	
imm_sel	I	I	S	
d_src	alu	alu	*	
op_src	imm	reg	imm	

Next state =

Output = control signals

Controller as FSM

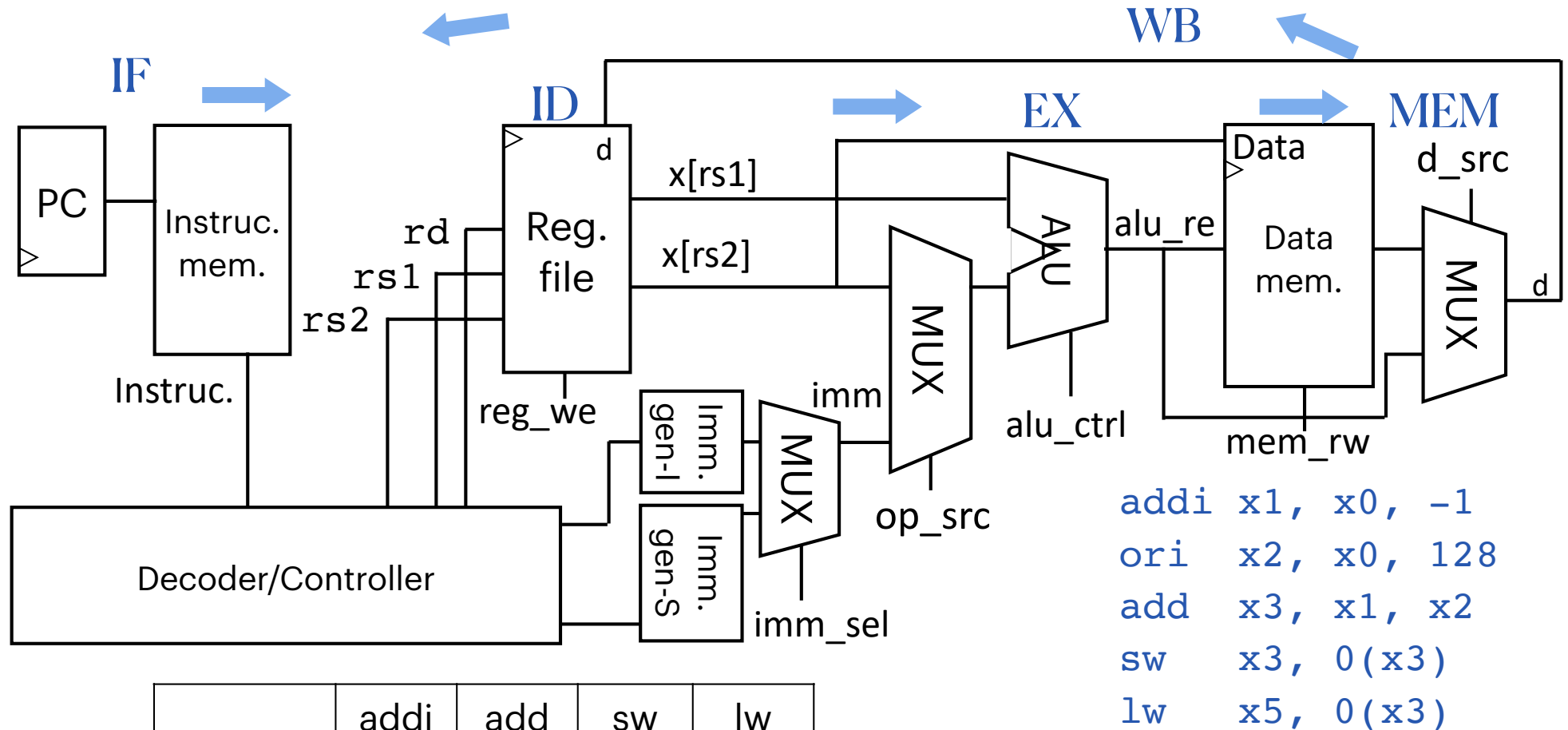

	addi	add	sw	lw
reg_we	1	1	0	1
mem_rw	R	R	W	R
alu_ctrl	add	add	add	add
imm_sel	I	I	S	I
d_src	alu	alu	*	mem
op_src	imm	reg	imm	imm



Next state =

Output = control signals



Continue with Datapath

— Decision Making Instructions



B-type Branch

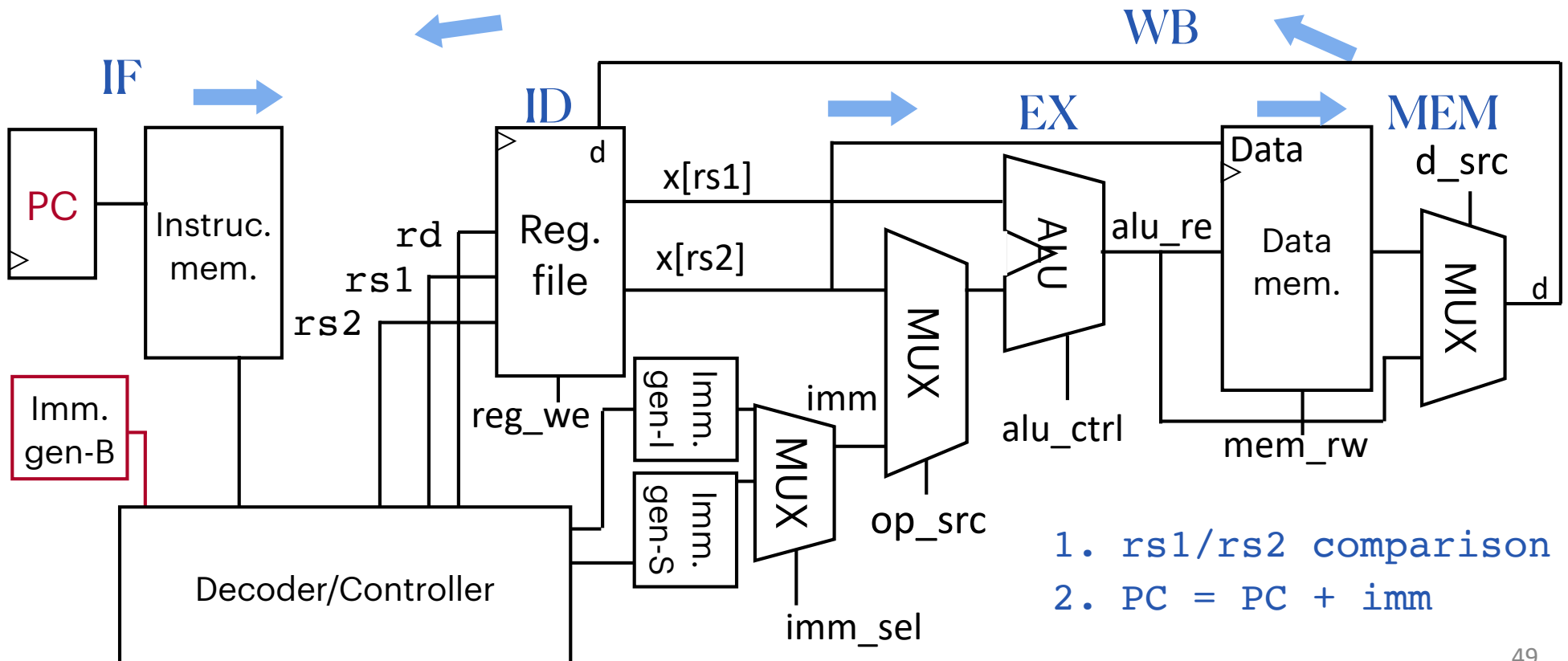 

B-type Branch

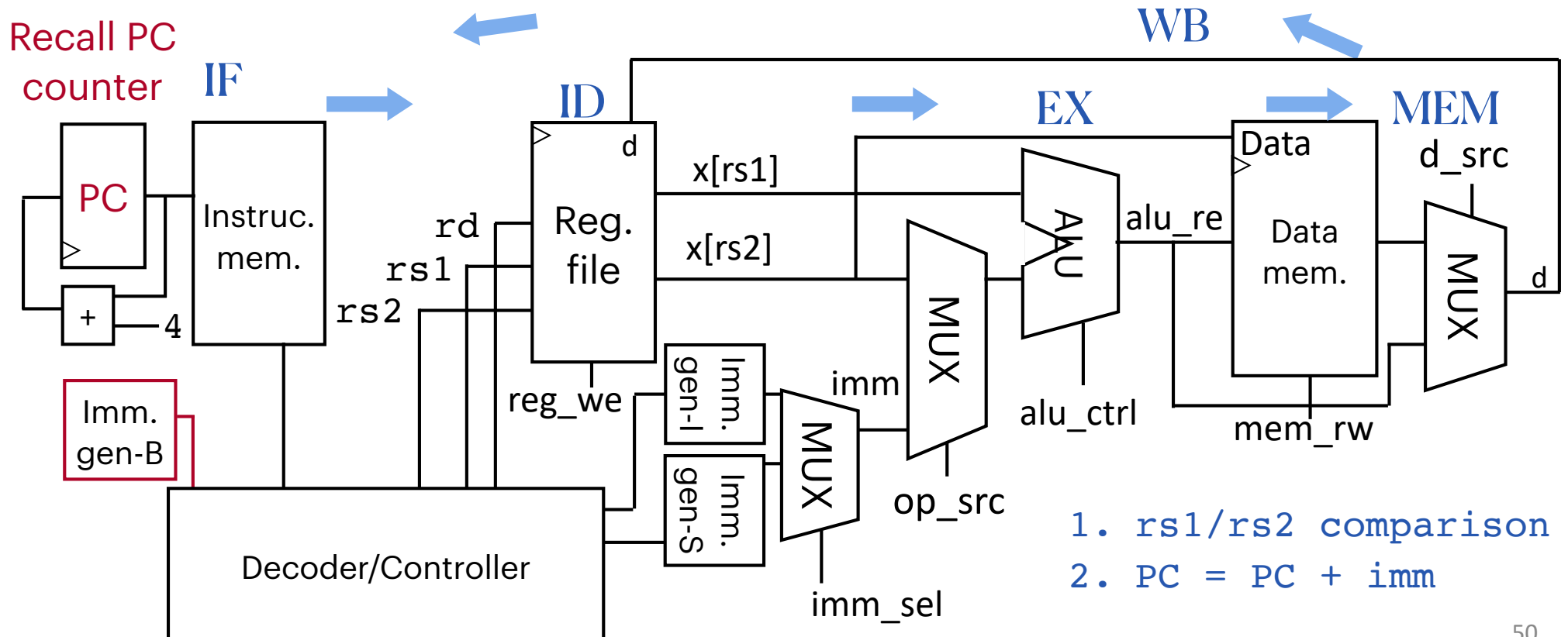 



B-type Branch

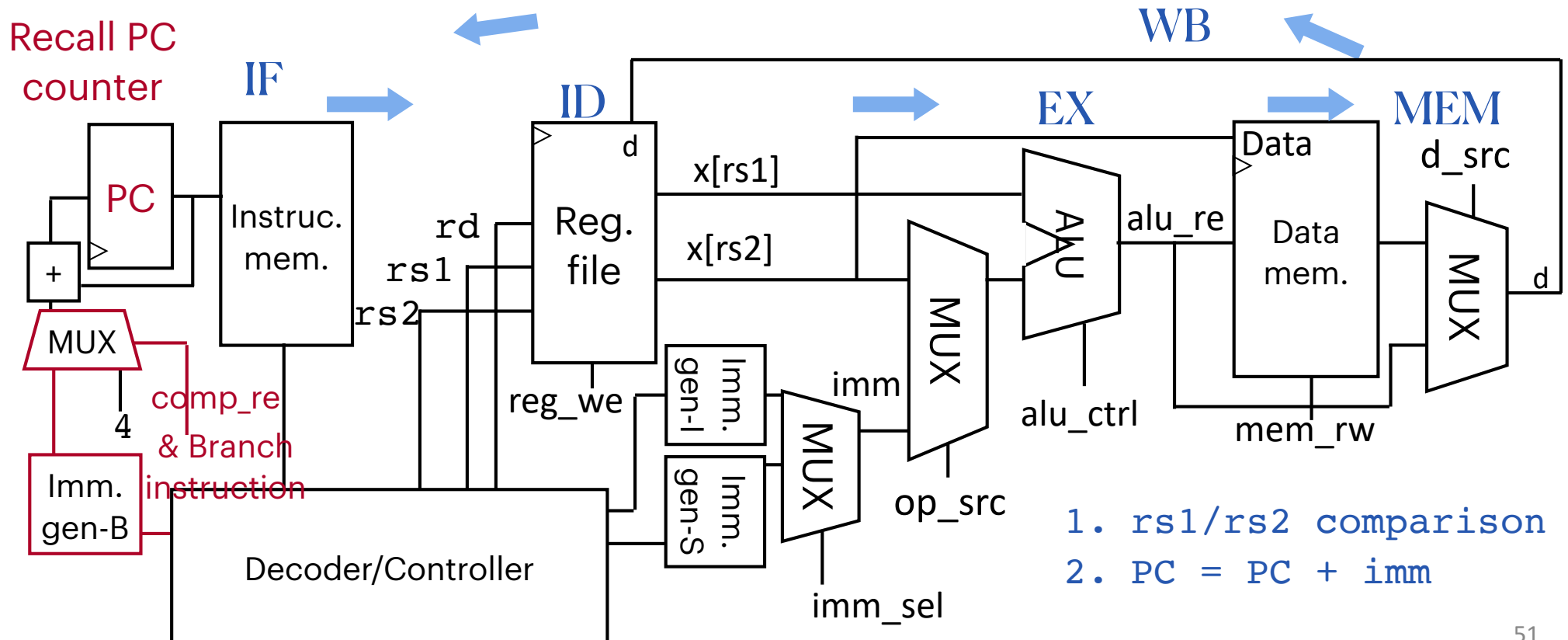
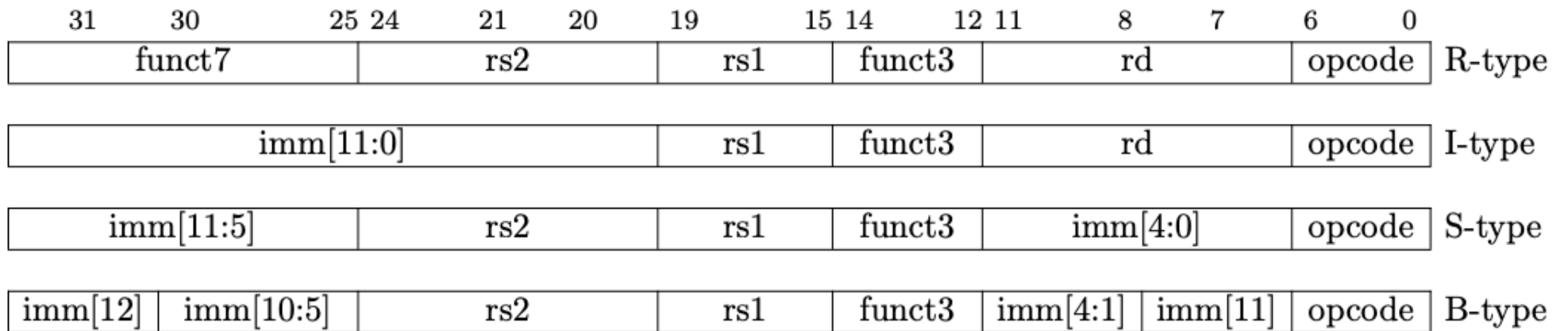



B-type Branch

31	30	25	24	21	20	19	15	14	12	11	8	7	6	0	
funct7				rs2			rs1		funct3		rd			opcode	R-type
imm[11:0]						rs1		funct3		rd			opcode	I-type	
imm[11:5]				rs2			rs1		funct3		imm[4:0]			opcode	S-type
imm[12]	imm[10:5]			rs2			rs1		funct3		imm[4:1]	imm[11]	opcode	B-type	

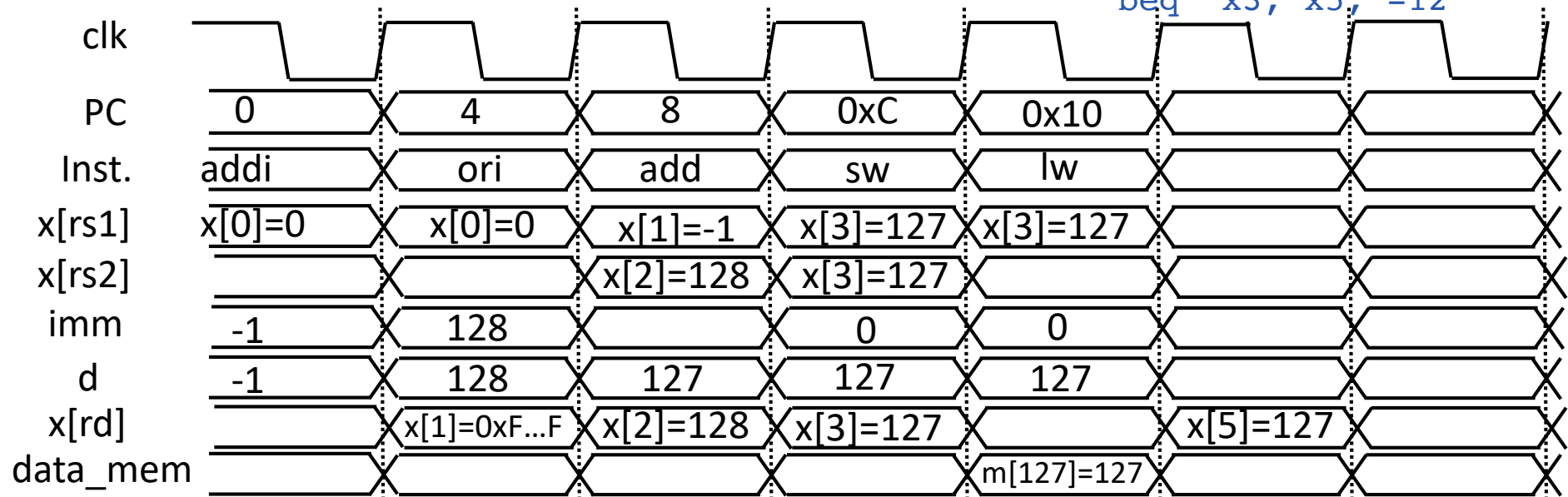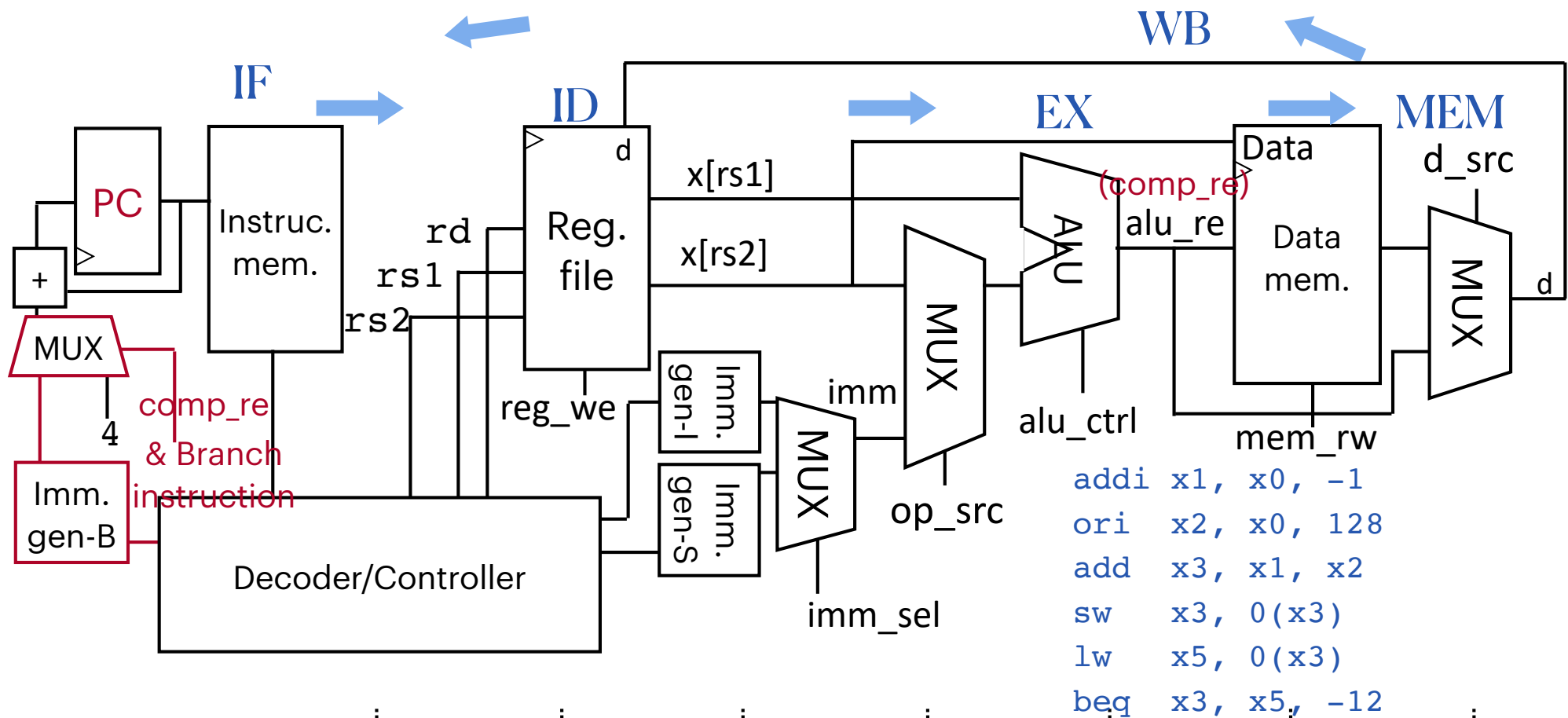- Implementation of comparison
 - Comparison \leq subtraction, can reuse the hardware of add/sub to generate comparison result



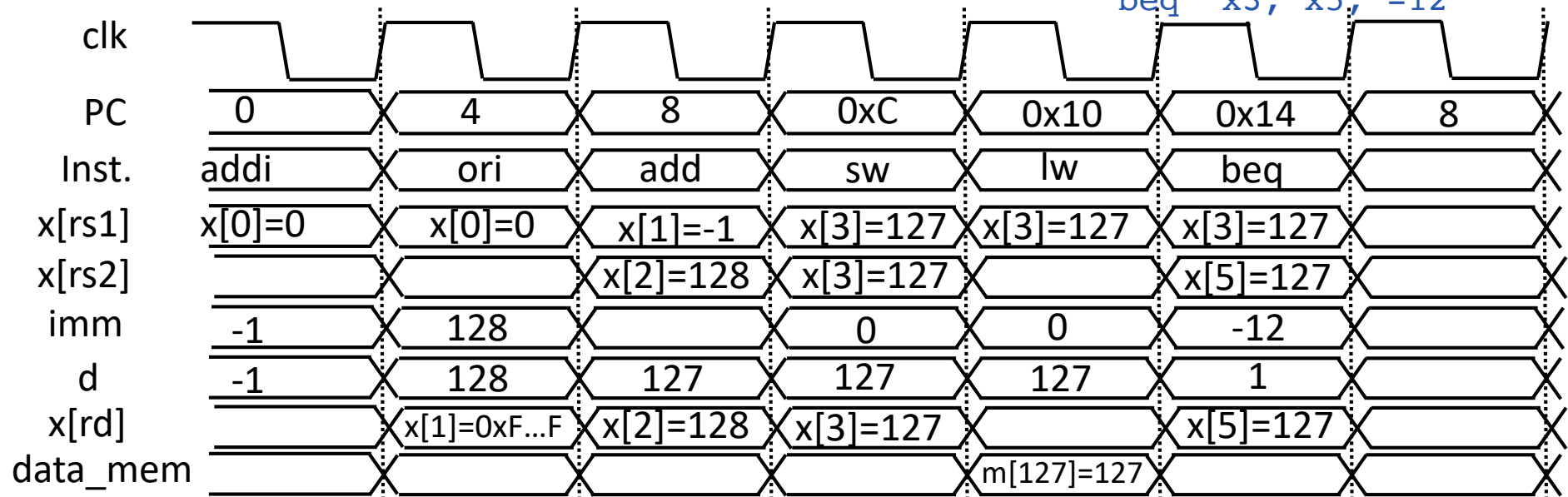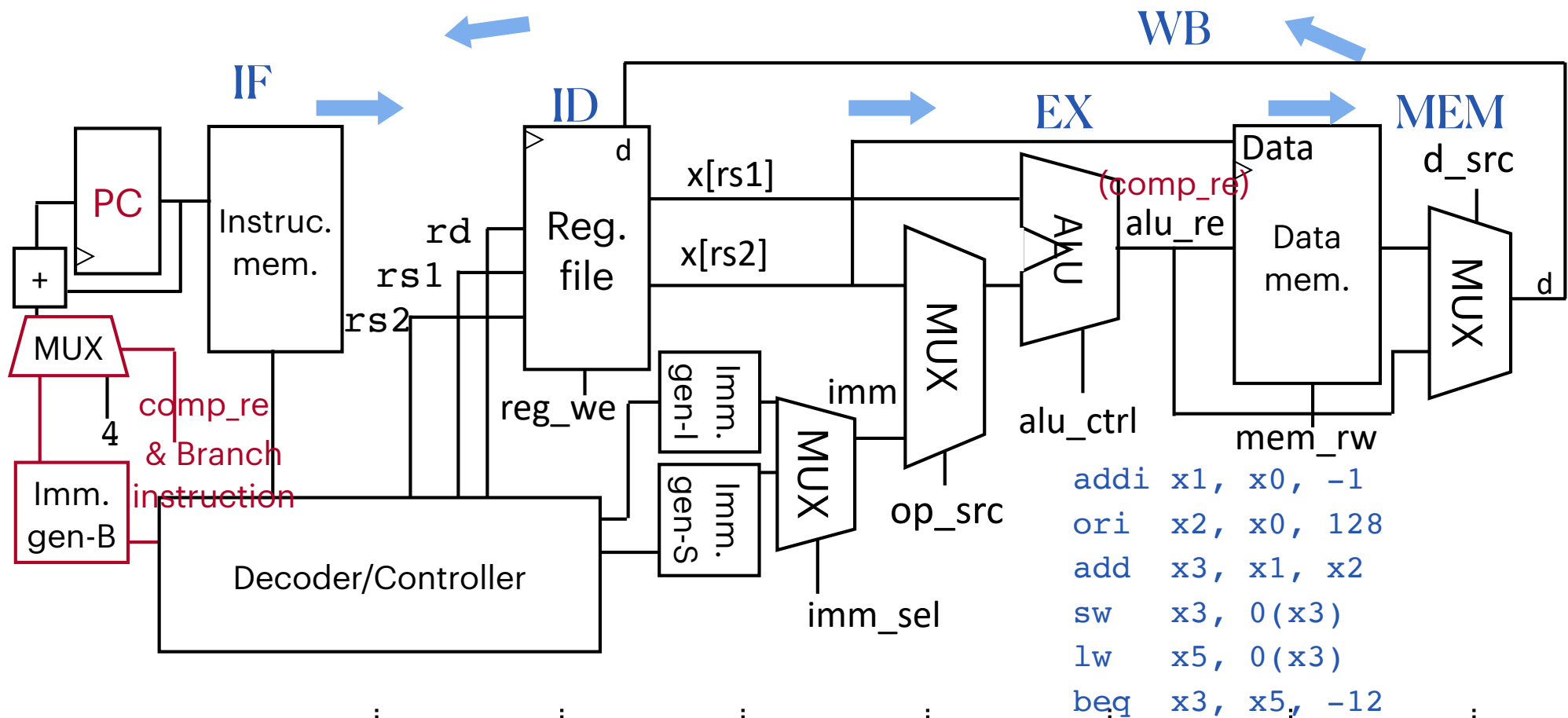

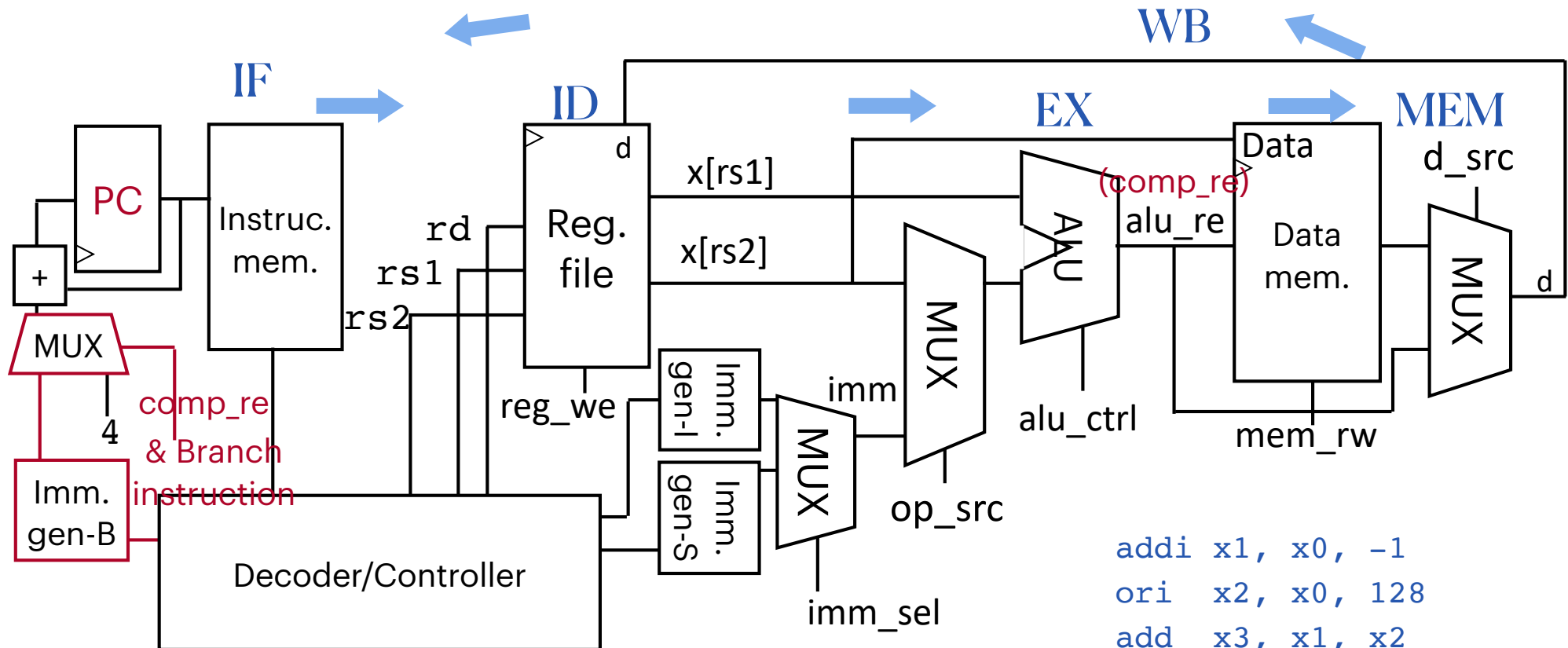


```

addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
beq  x3, x5, -12

```

	addi	add	sw	lw	beq
reg_we	1	1	0	1	
mem_rw	R	R	W	R	
alu_ctrl	add	add	add	add	
imm_sel	I	I	S	I	
d_src	alu	alu	*	mem	
op_src	imm	reg	imm	imm	
PC_mux					

Output = control signals

 

```


addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
beq  x3, x5, -12

```

	addi	add	sw	lw	beq
reg_we	1	1	0	1	0
mem_rw	R	R	W	R	R
alu_ctrl	add	add	add	add	comp
imm_sel	I	I	S	I	B
d_src	alu	alu	*	mem	alu
op_src	imm	reg	imm	imm	reg
PC_mux	+4	+4	+4	+4	comp_re & Branch instruction


Output = control signals

Another Implementation

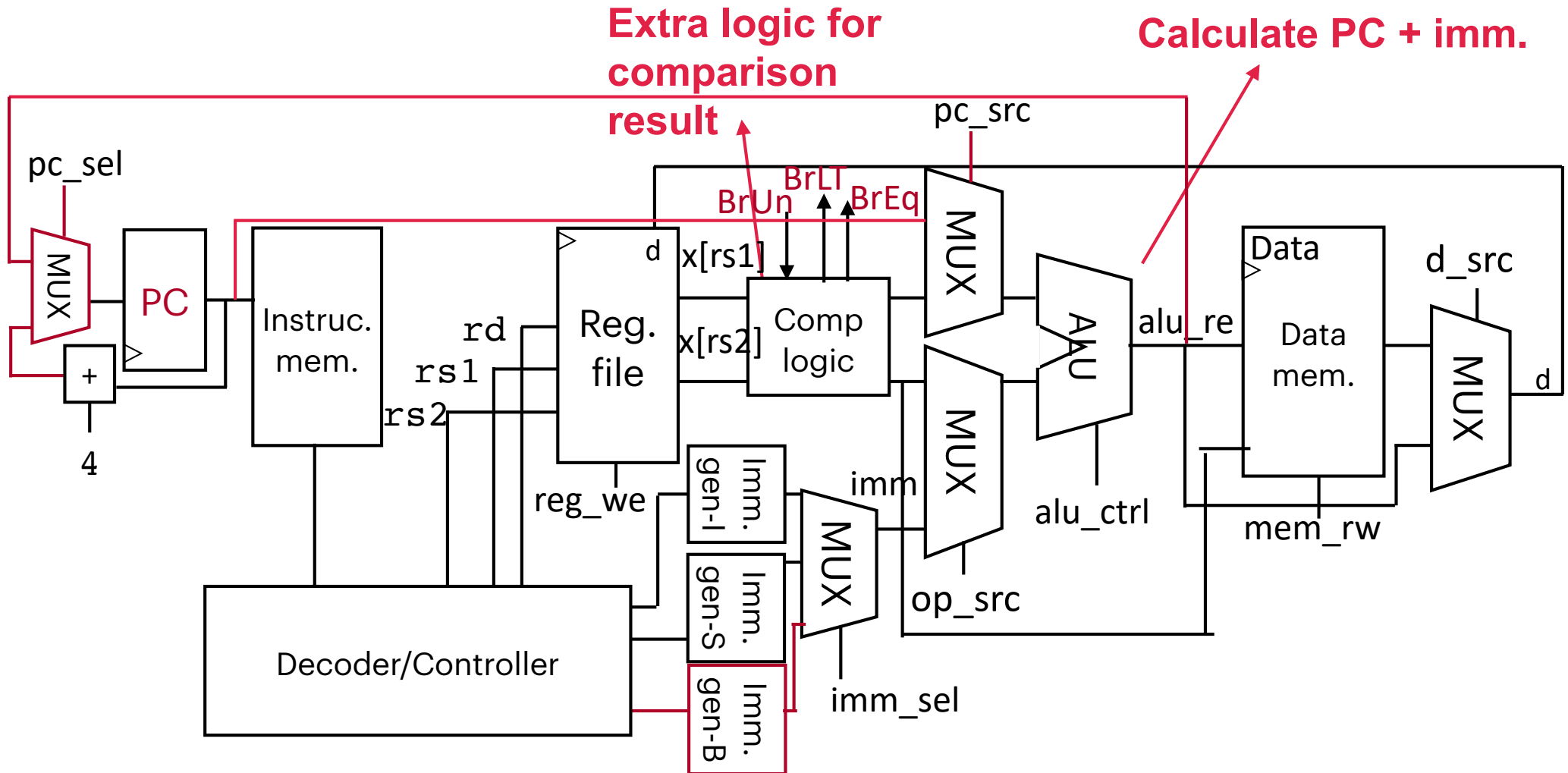



There Are a Thousand Hamlets in a Thousand People's Eyes. — Shakespeare

Compare-Logic

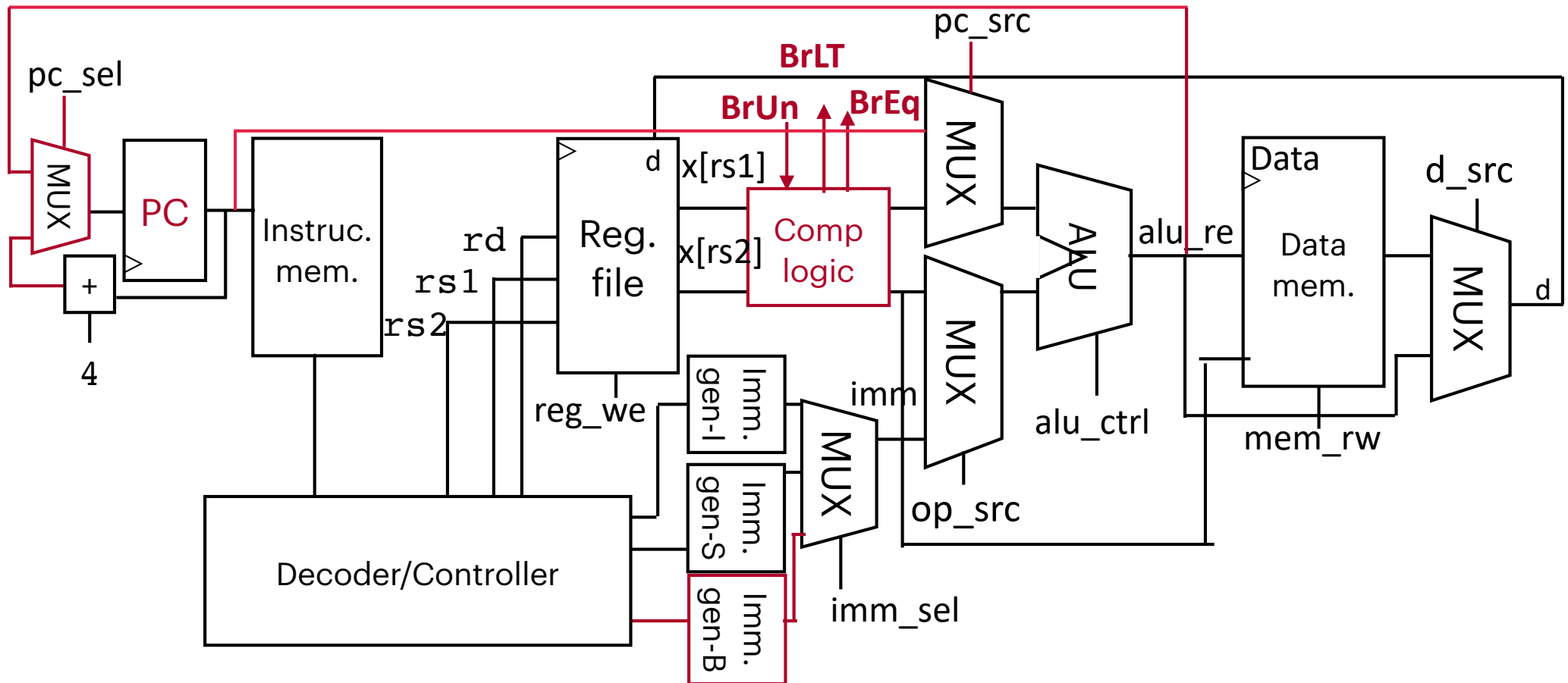

There Are a Thousand Hamlets in a Thousand People's Eyes. — Shakespeare

Consideration for IMM Generation

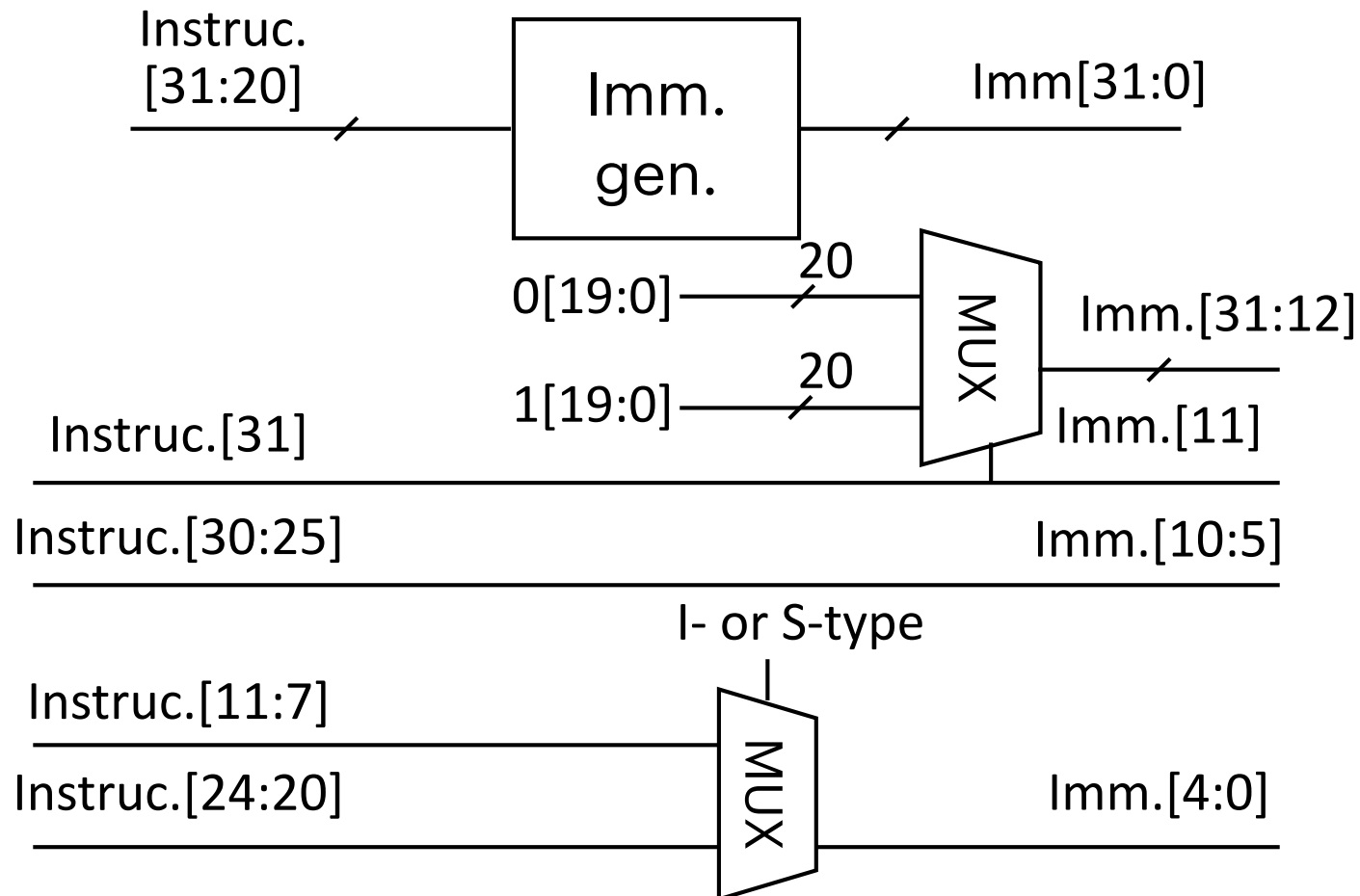 

Consideration for IMM Generation

