

Course Info

- Lab 6 next week, prepare before lab sessions! Keep an eye on piazza.
- Project 1.2 ddl March 31st. Project 2.1 released next week!
- This week discussion on ALU & FSM. Next week discussion on datapath.
- Mid-term I answer & score will be released before next week. If you have questions, feel free to ask on Piazza.

Course Info

- HW4 will be released, keep an eye on piazza. Submit your paper homework to the picture below (SIST 3-322). There will be a box. Put into the box. Remember to add your name. You have only one chance to submit and cannot be withdrawn.





信息科学与技术学院

School of Information Science and Technology

CS 110

Computer Architecture

Datapath & Controller

Instructors:

Siting Liu & Chundong Wang


Course website: [https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/
Spring-2023/index.html](https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2023/index.html)

School of Information Science and Technology (SIST)


ShanghaiTech University

2023/3/5

Controller as FSM

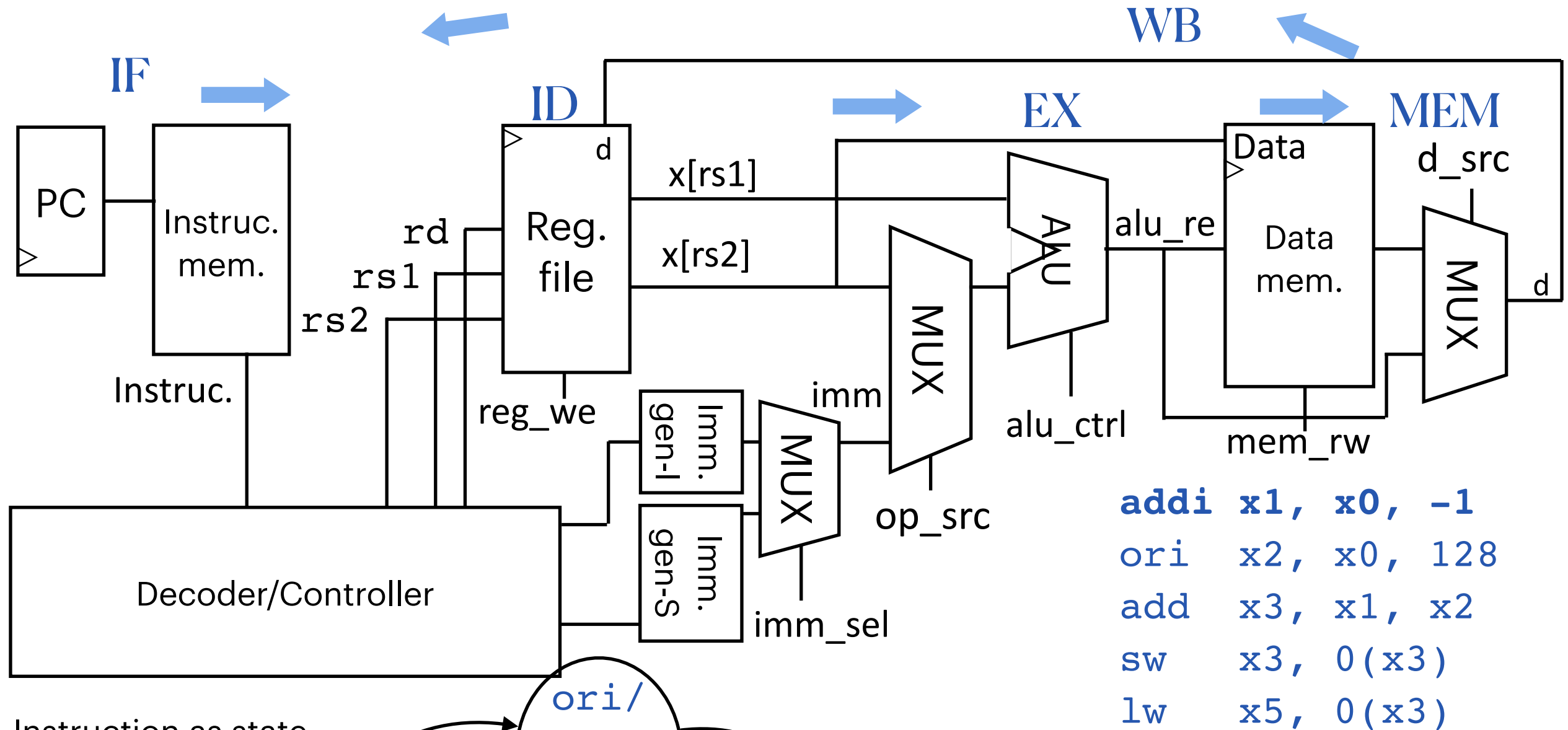


Instruction as state

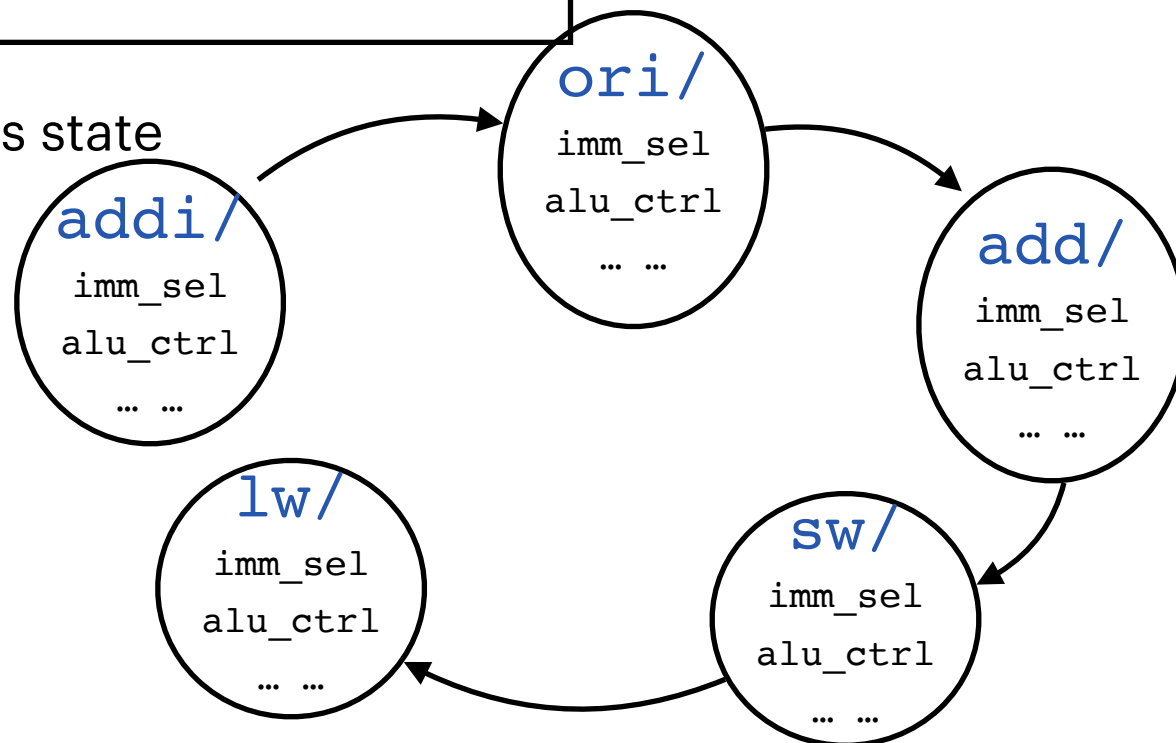

Next state = instruction will be executed

Output = control signals

Cur. state = instruction being executed

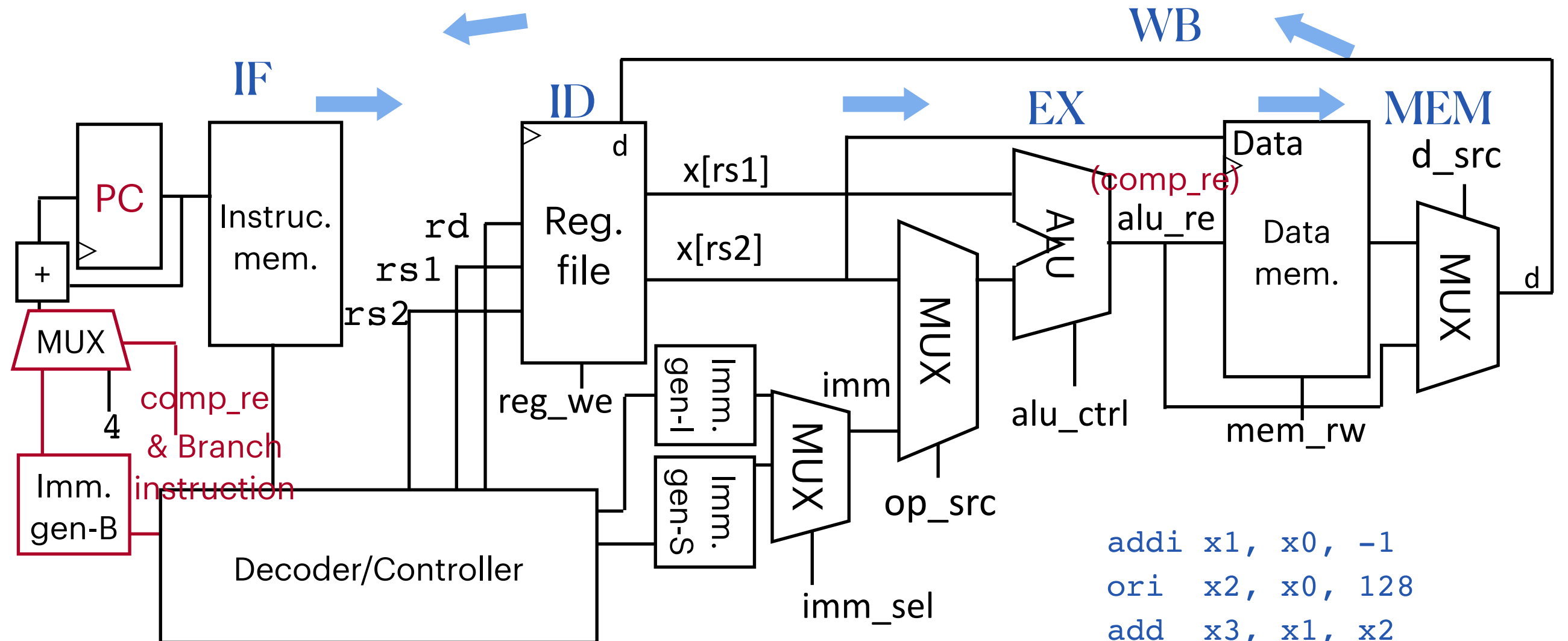



```

addi x1, x0, -1
ori  x2, x0, 128
add  x3, x1, x2
sw   x3, 0(x3)
lw   x5, 0(x3)
beq  x3, x5, -12


```

Output = control signals

	addi	add	sw	lw	beq
reg_we	1	1	0	1	0
mem_rw	R	R	W	R	R
alu_ctrl	add	add	add	add	comp
imm_sel	I	*	S	I	B*
d_src	alu	alu	*	mem	alu*
op_src	imm	reg	imm	imm	reg
PC_mux	+4	+4	+4	+4	comp_re & Branch instruction

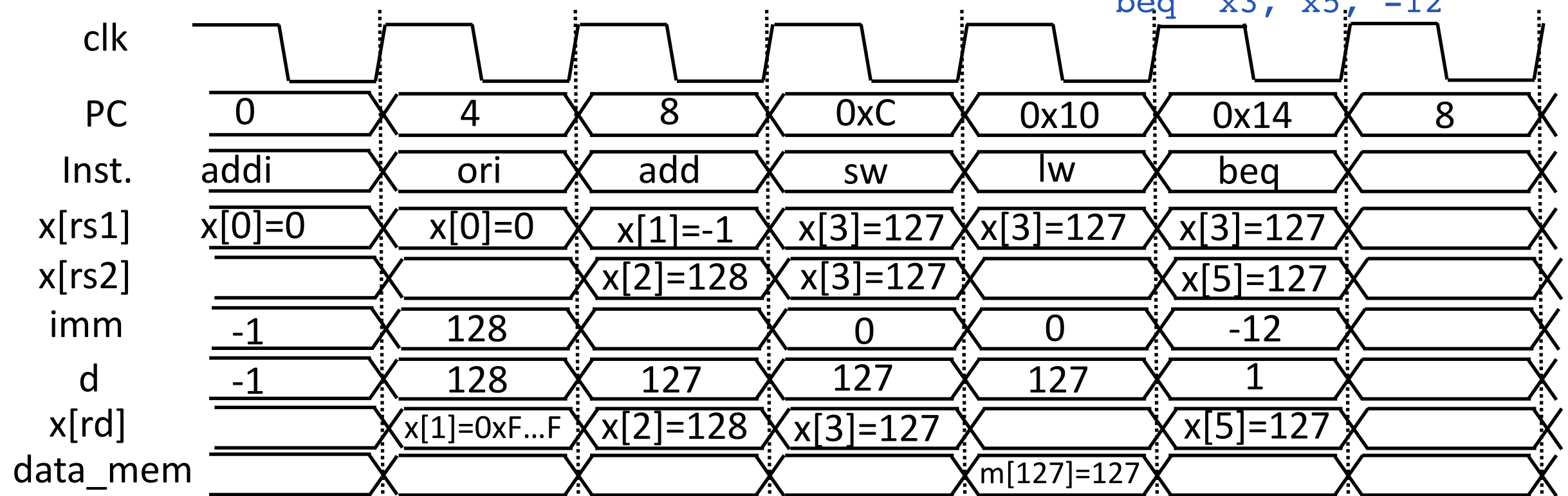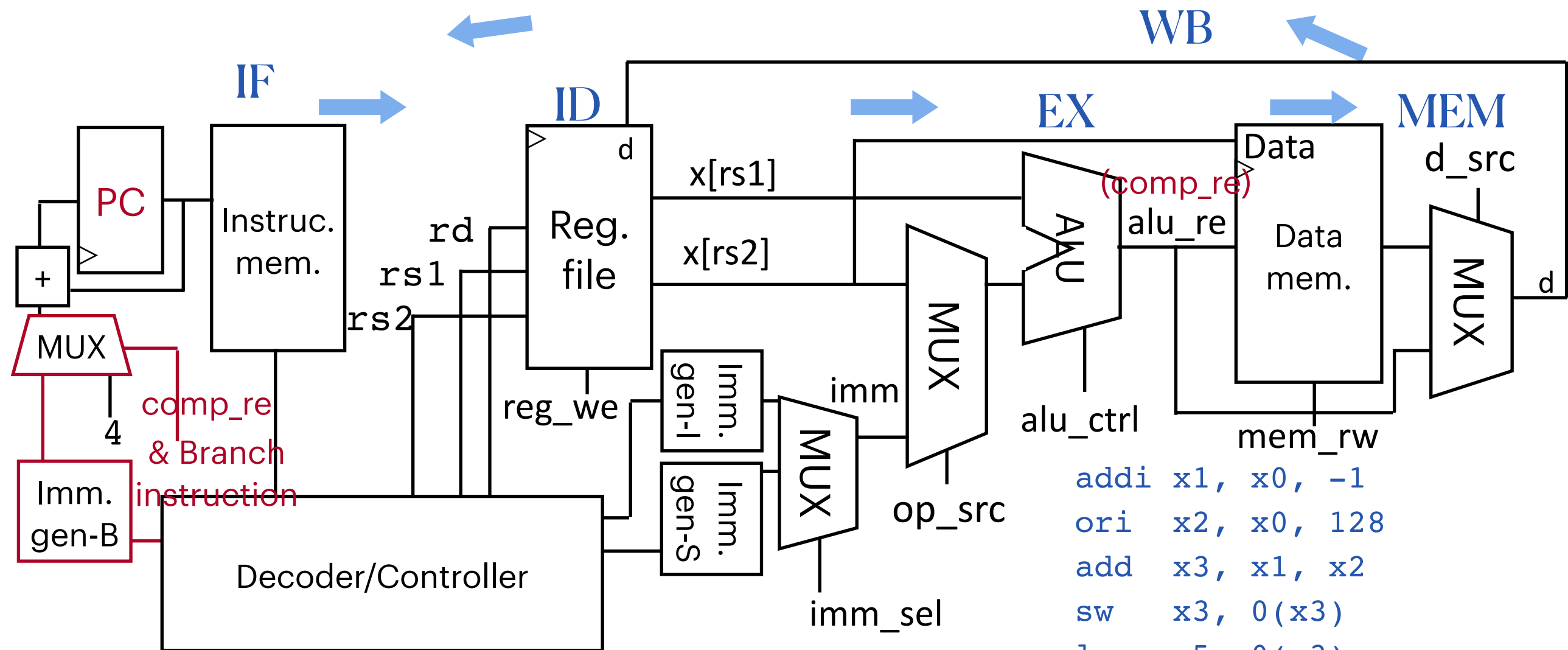


Another Implementation

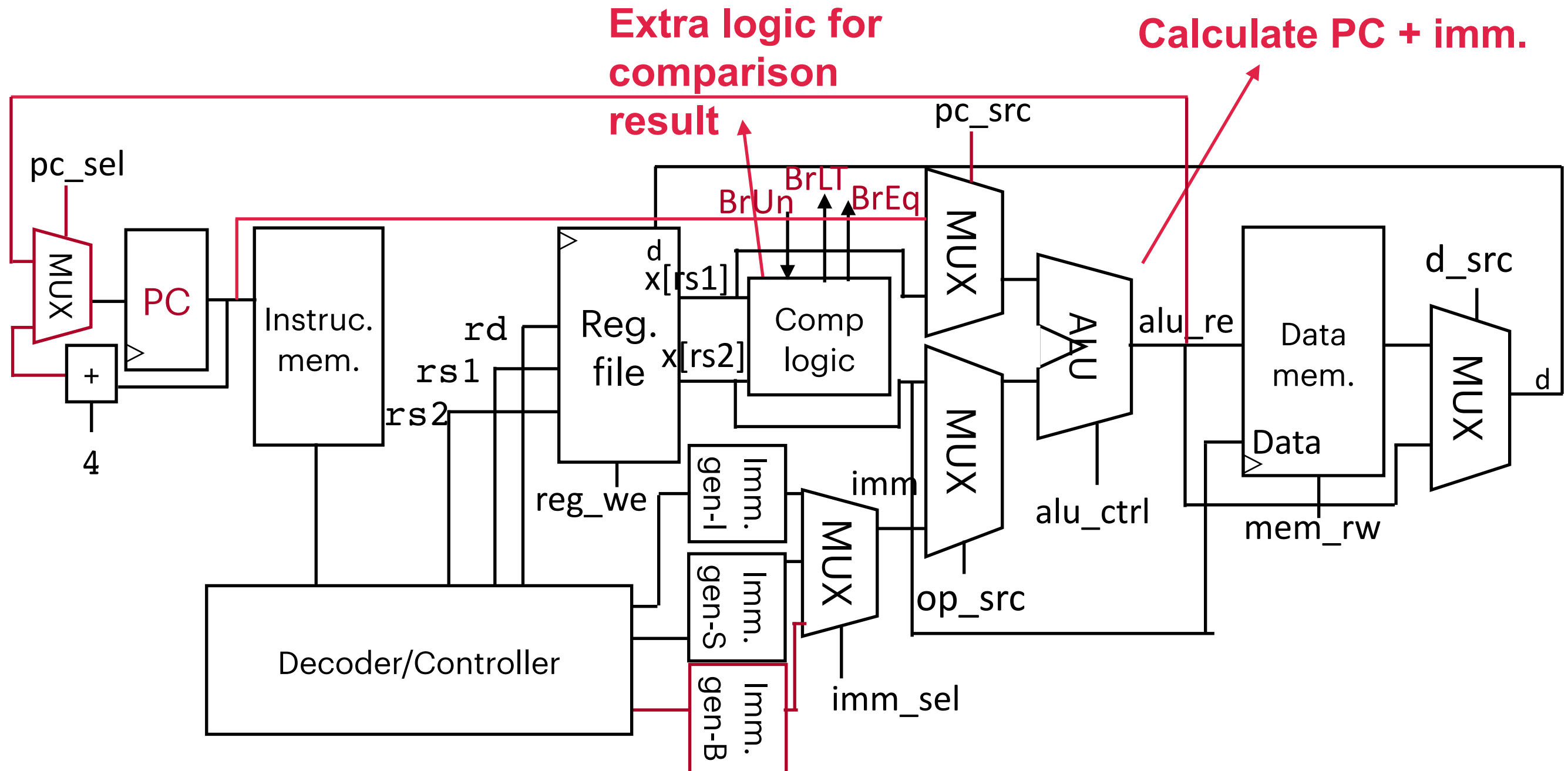


There Are a Thousand Hamlets in a Thousand People's Eyes. — Shakespeare

Compare Logic

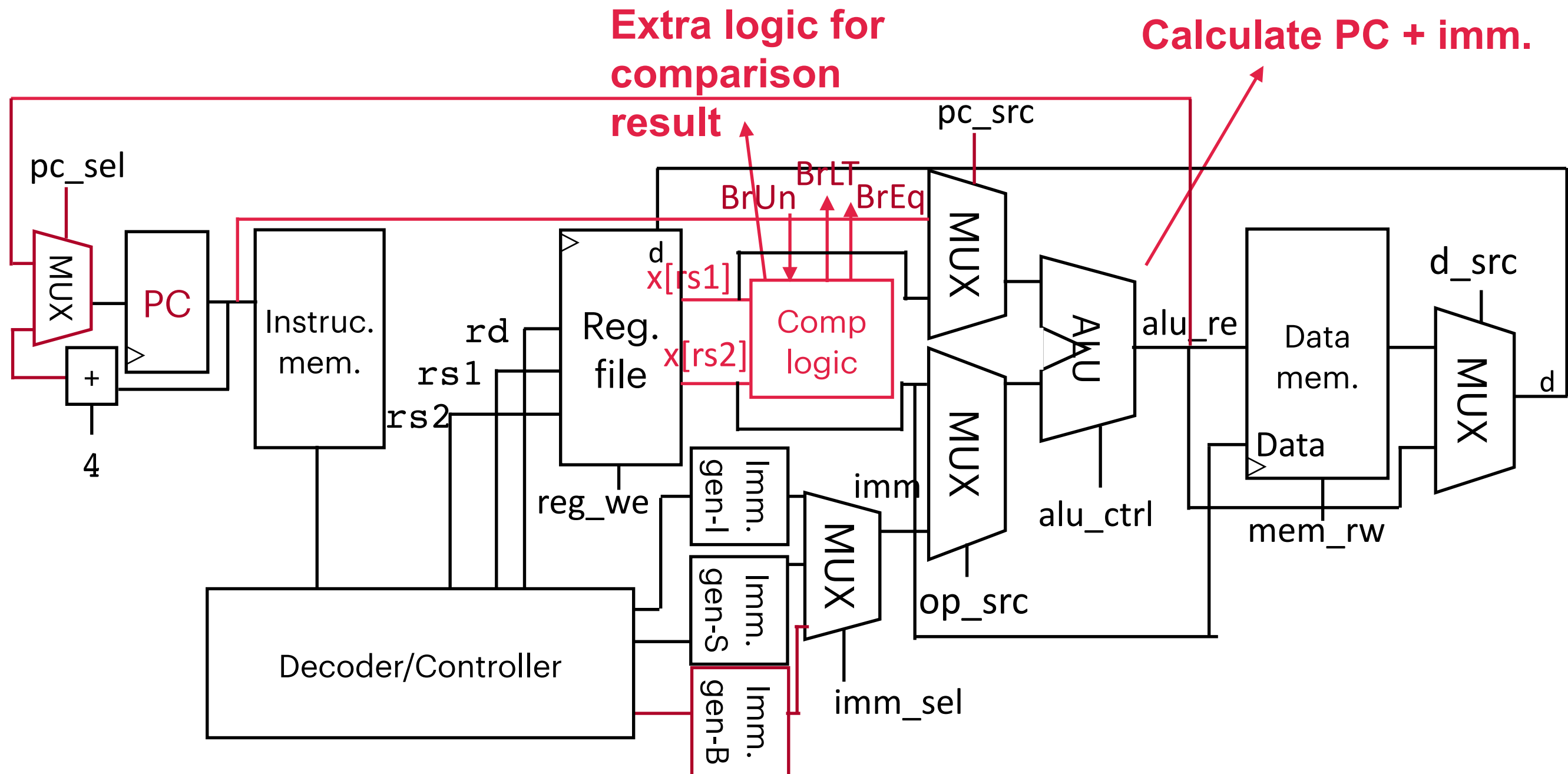

BrUn: control signal (input), whether it is a unsigned or signed comparison;
 BrLT: 1 if less than, otherwise 0; output signal to the decoder/controller;
 BrEq: 1 if equal, otherwise 0; output signal to the decoder/controller;

Compare Logic

 



$BrUn$: control signal (input), whether it is a unsigned or signed comparison;

$BrLT$: 1 if less than, otherwise 0; output signal


$BrEq$: 1 if equal, otherwise 0; output signal

	$BrLT$	$BrEq$
BEQ	0	1
BNE	0/1	0
BLT	1	0
BGE	0	0/1


Consideration for IMM Generation

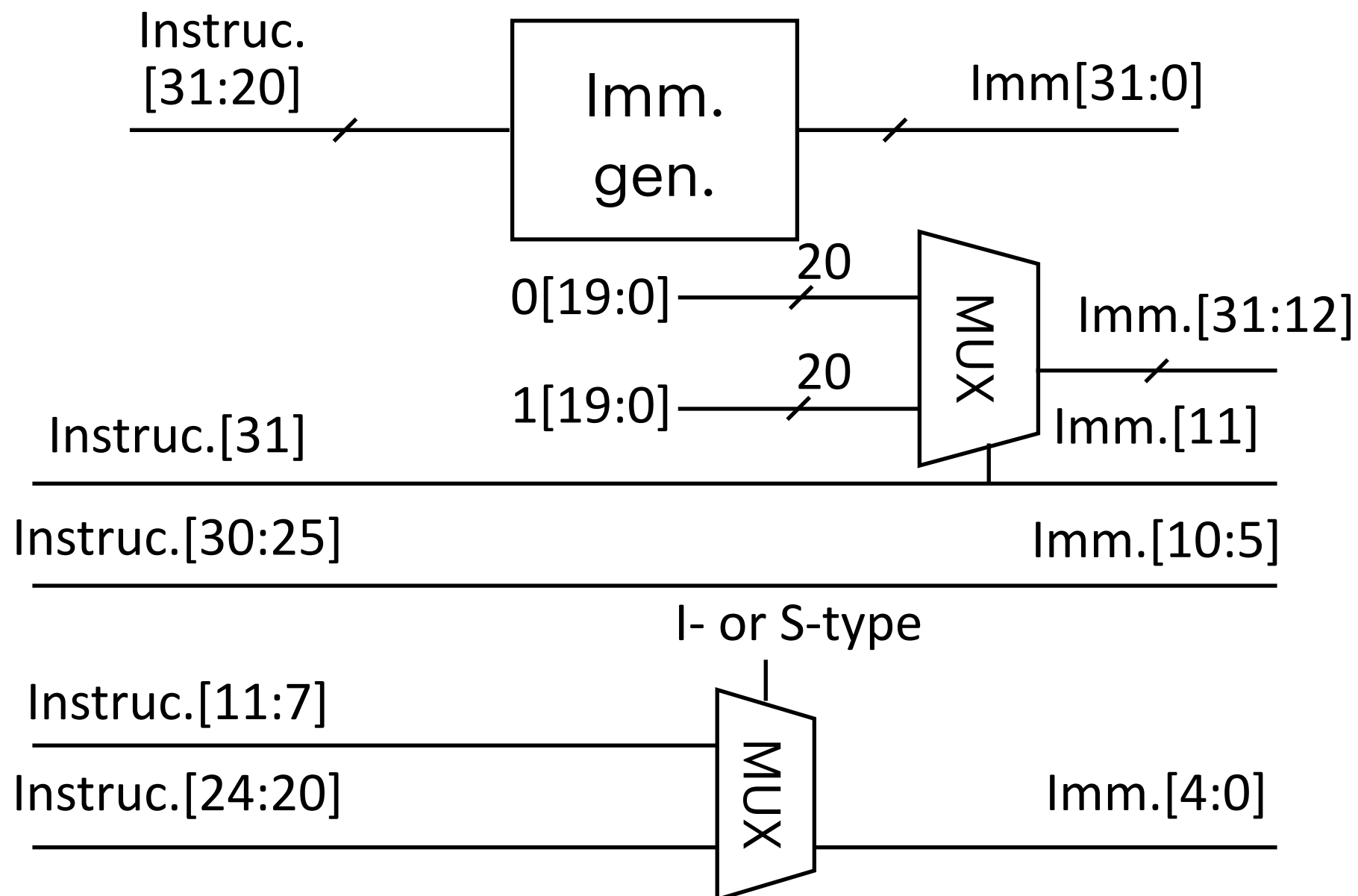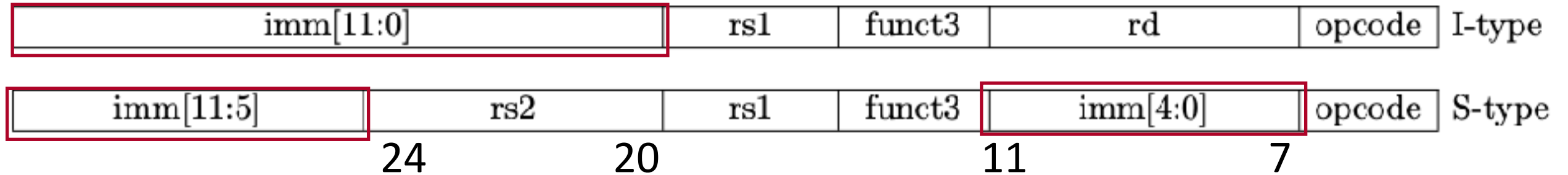

Consideration for IMM Generation

 



Up to Now

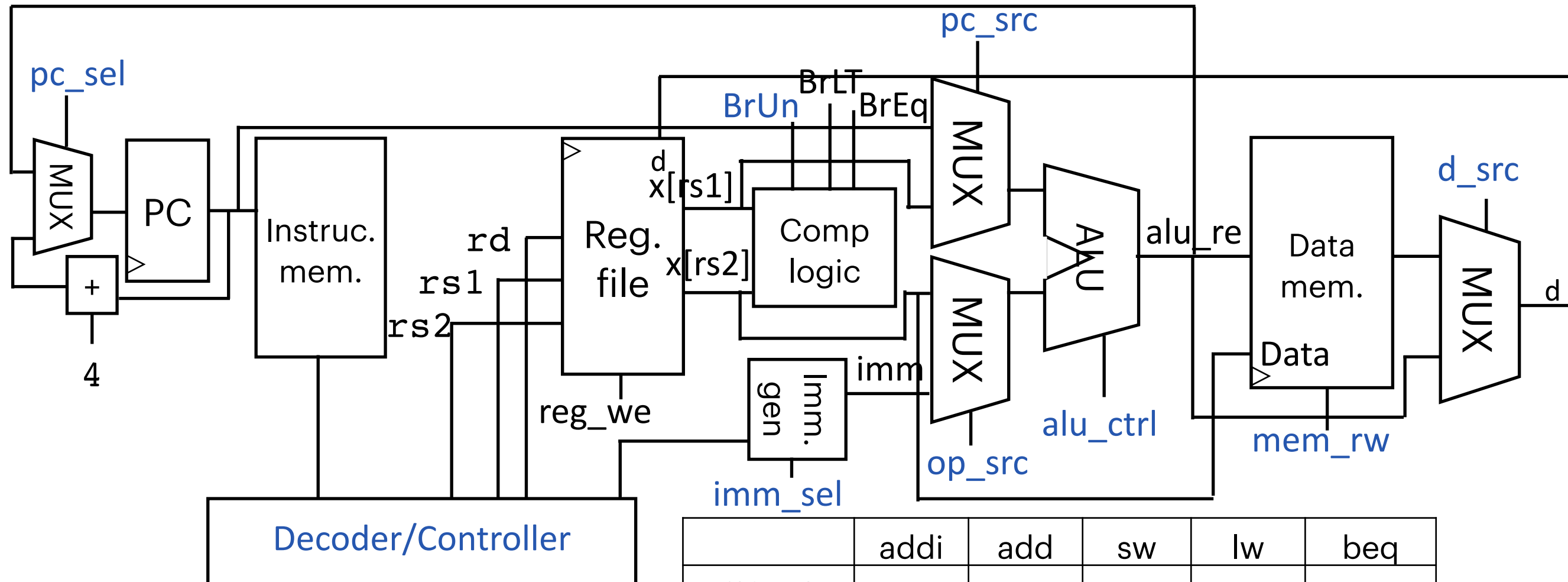


Control signals generated by
decoder/controller,
according to the instruction

	addi	add	sw	lw	beq
reg_we	1	1	0	1	0
mem_rw	R	R	W	R	R
alu_ctrl	add	add	add	add	add
imm_sel	I	*	S	I	B
d_src	alu	alu	*	mem	*
op_src	imm	reg	imm	imm	imm
pc_sel	+4	+4	+4	+4	Comp.
pc_src	reg	reg	reg	reg	pc
BrUn	*	*	*	*	w/w/o u

Add JALR

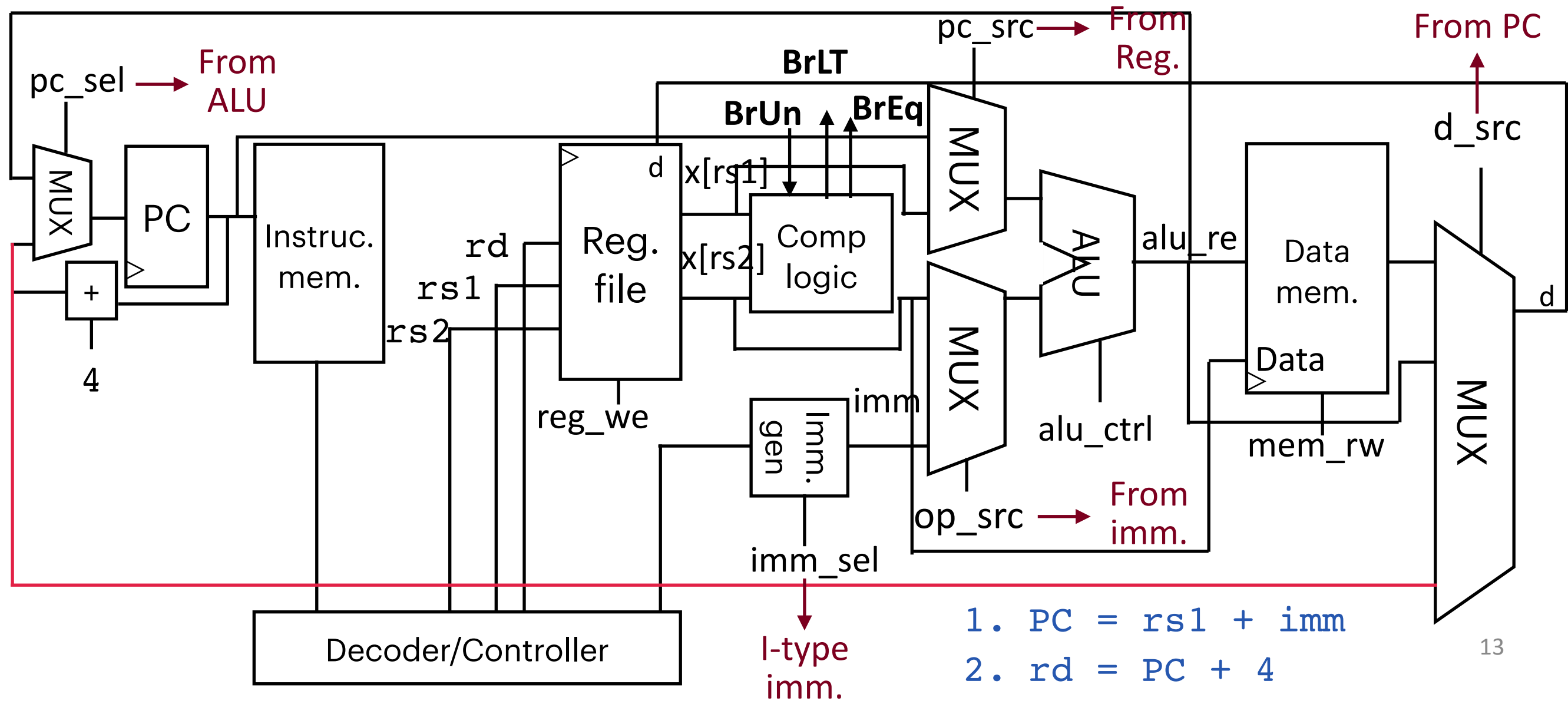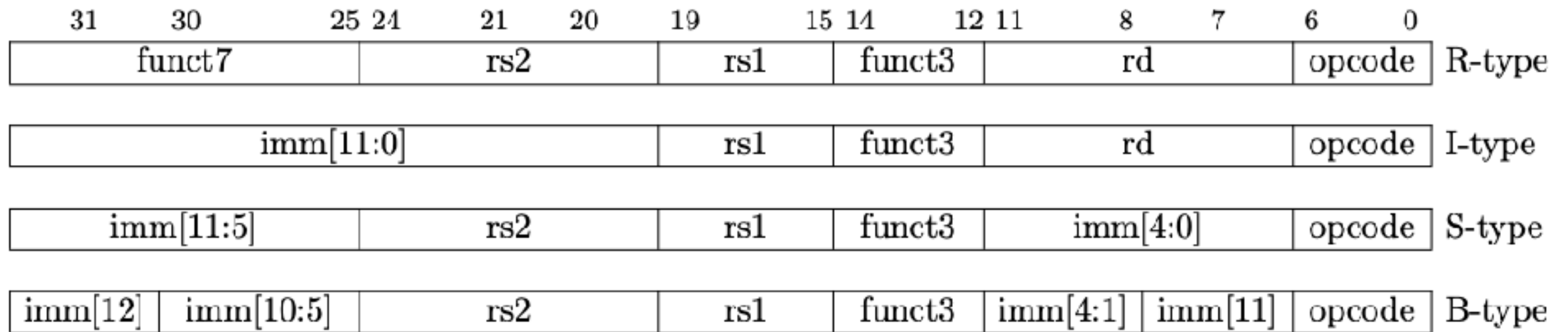


Add JALR

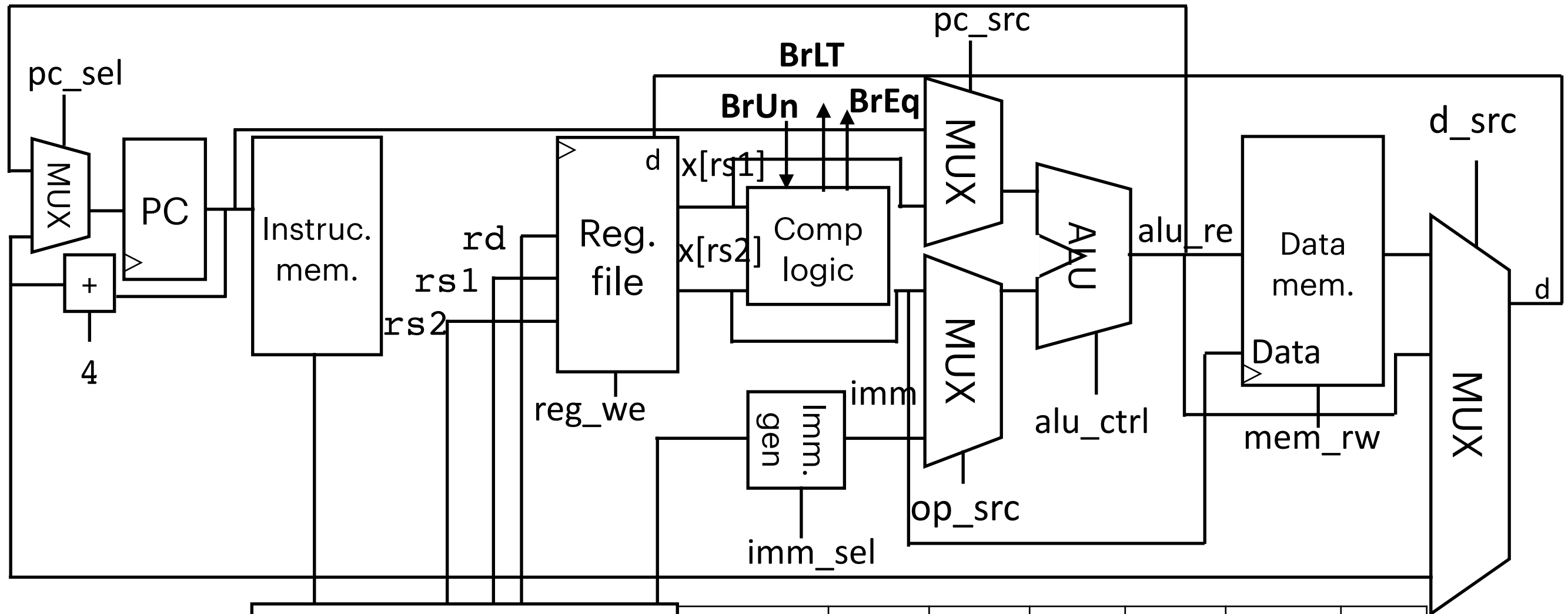

Decoder/Controller

	addi	add	sw	lw	beq	jlr
reg_we	1	1	0	1	0	
mem_rw	R	R	W	R	R	
alu_ctrl	add	add	add	add	add	
imm_sel	I	*	S	I	B	
d_src	alu	alu	*	mem	*	
op_src	imm	reg	imm	imm	imm	
pc_sel	+4	+4	+4	+4	Comp.	
pc_src						

Add JALR

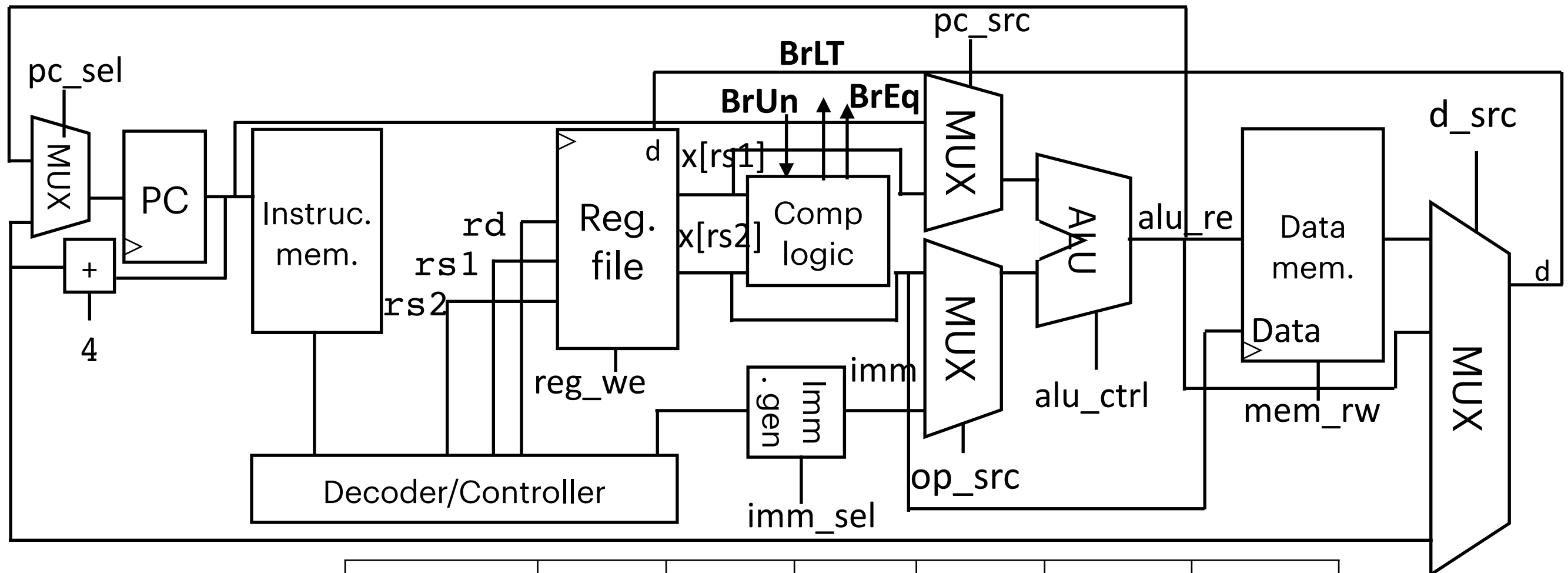


	addi	add	sw	lw	beq	jalr
reg_we	1	1	0	1	0	
mem_rw	R	R	W	R	R	
alu_ctrl	add	add	add	add	add	
imm_sel	I	*	S	I	B	
d_src	alu	alu	*	mem	*	
op_src	imm	reg	imm	imm	imm	
pc_sel	+4	+4	+4	+4	Comp.	
pc_src	reg	reg	reg	reg	pc	
BrUn	*	*	*	*	w/w/o u	

Add JAL

$$1. PC = PC + imm$$

$$2. rd = PC + 4$$


imm[11:0]			rs1	funct3	rd		opcode	I-type		
imm[11:5]		rs2		rs1	funct3	imm[4:0]		opcode	S-type	
imm[12]	imm[10:5]		rs2		rs1	funct3	imm[4:1]	imm[11]	opcode	B-type
imm[31:12]						rd		opcode	U-type	
imm[20]	imm[10:1]		imm[11]	imm[19:12]		rd		opcode	J-type	

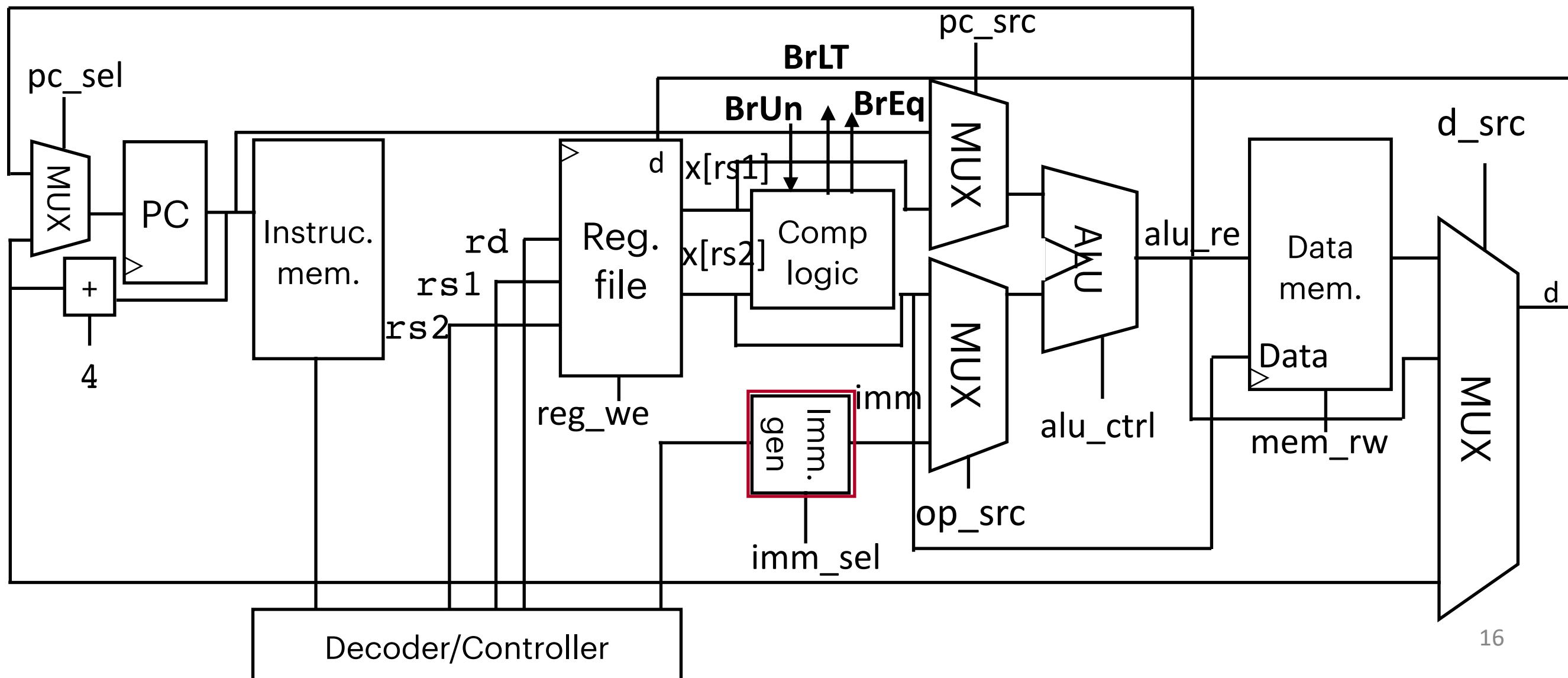

Add JAL

$$1. PC = PC + imm$$


$$2. rd = PC + 4$$

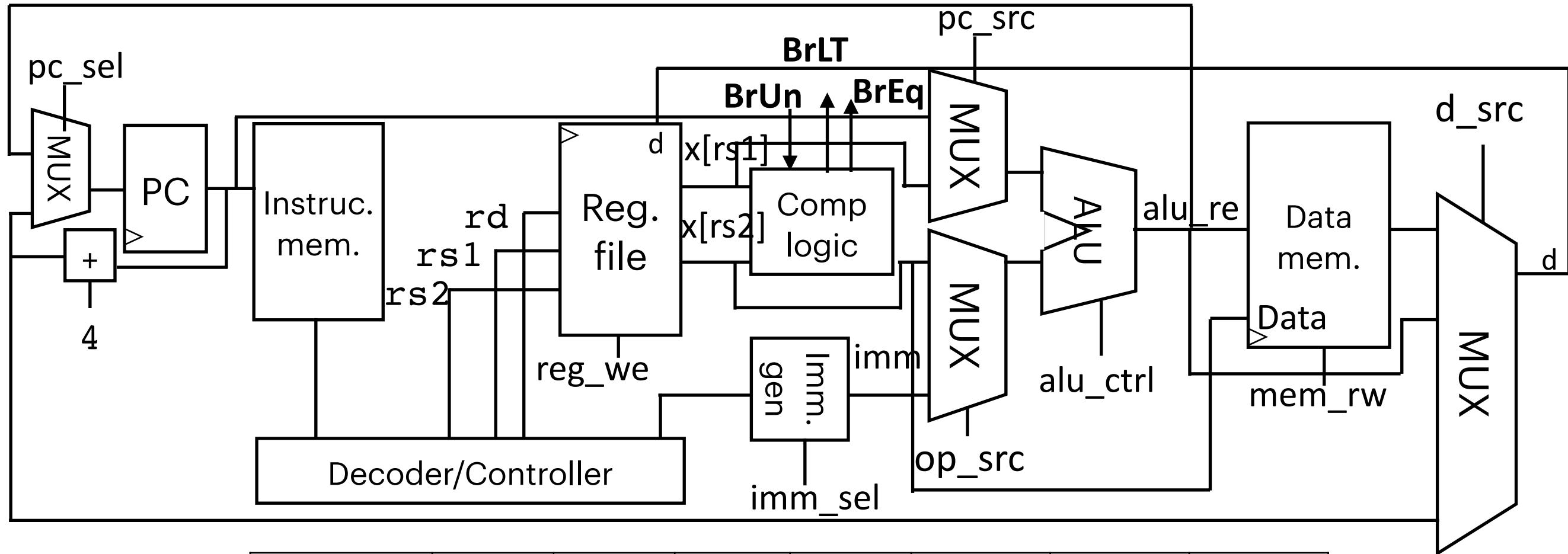

	addi	add	sw	lw	beq	jalr	jal
reg_we	1	1	0	1	0	1	
mem_rw	R	R	W	R	R	R	
alu_ctrl	add	add	add	add	add	add	
imm_sel	I	*	S	I	B	I	
d_src	alu	alu	*	mem	*	pc	
op_src	imm	reg	imm	imm	imm	imm	
pc_sel	+4	+4	+4	+4	Comp.	alu_re	
pc_src	reg	reg	reg	reg	pc	reg	
BrUn	*	*	*	*	w/w/o u	*	


Add U-type: LUI

imm[31:12]				rd	opcode	U-type
imm[20]	imm[10:1]	imm[11]	imm[19:12]	rd	opcode	J-type

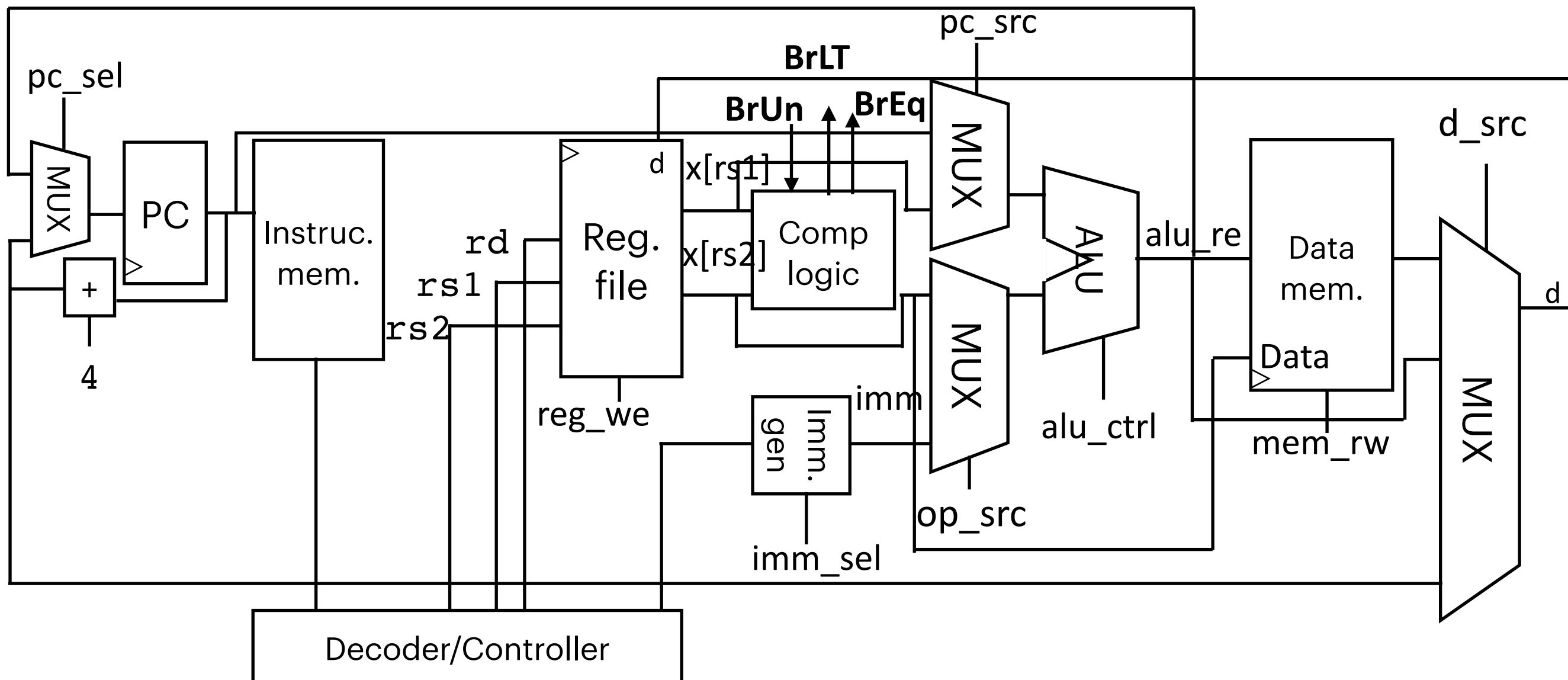


Add U-type: AUIPC

imm[31:12]				rd	opcode	U-type
imm[20]	imm[10:1]	imm[11]	imm[19:12]	rd	opcode	J-type

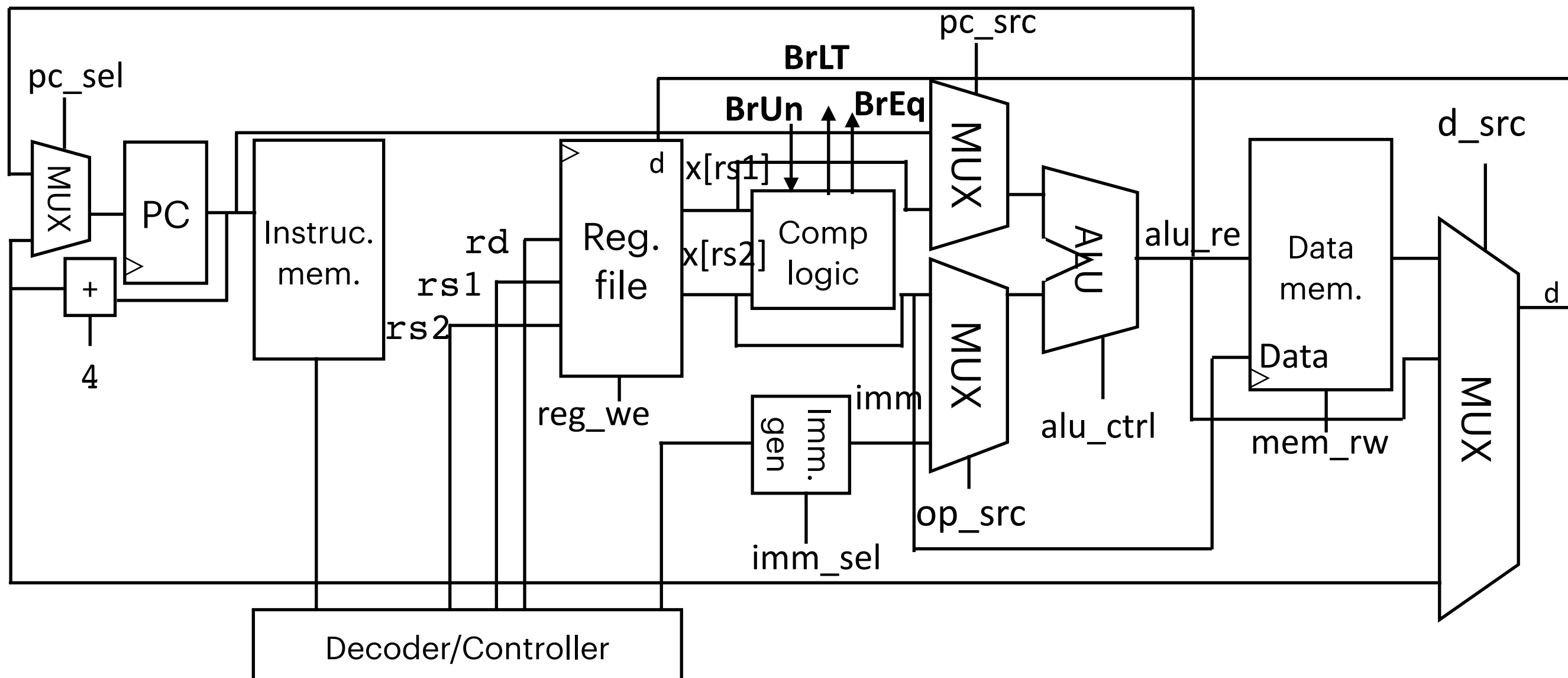

Timing Analysis

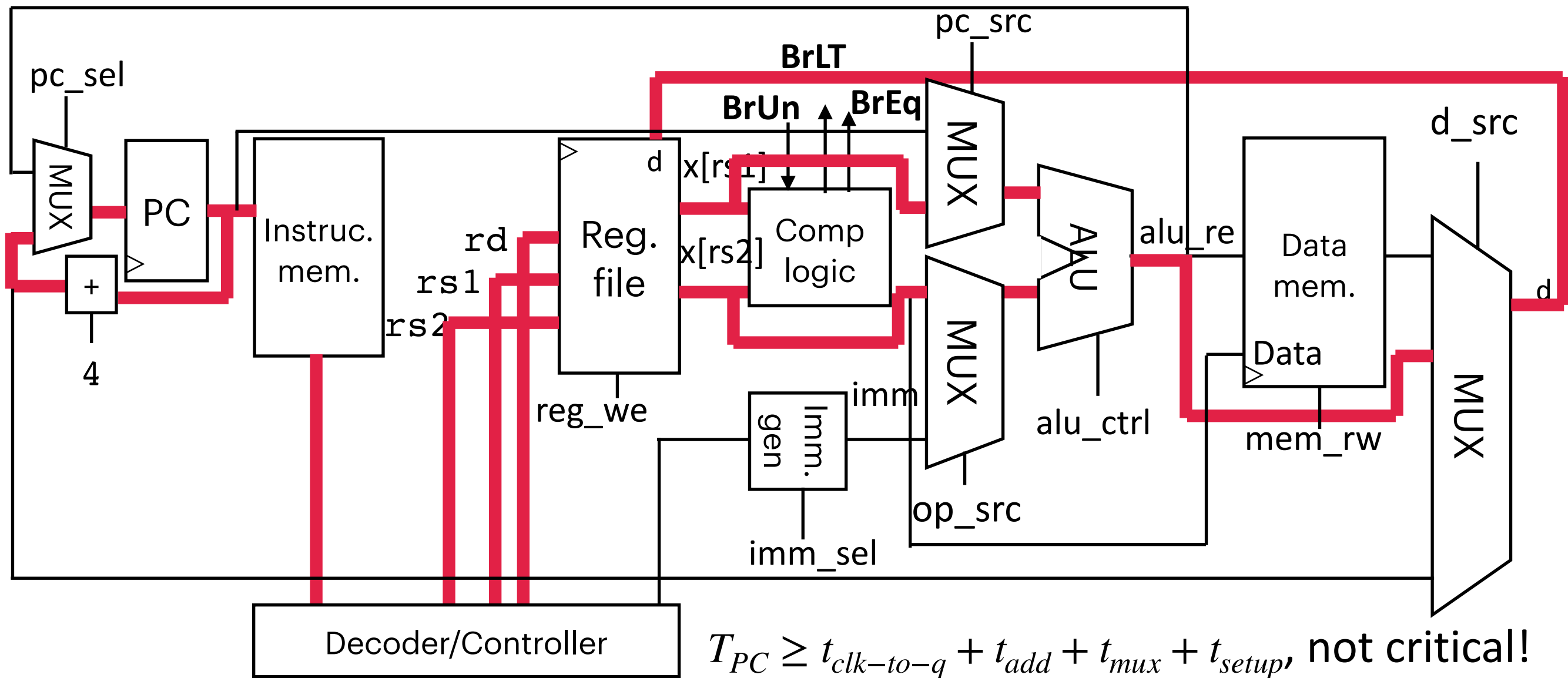
- What is the minimum clock cycle/max frequency of the CPU?



R-type: $T \geq t_{clk-to-q} + t_{imem} + t_{dec} + t_{reg} + t_{mux} + t_{alu} + t_{mux} + t_{setup}$ 20

Timing Analysis

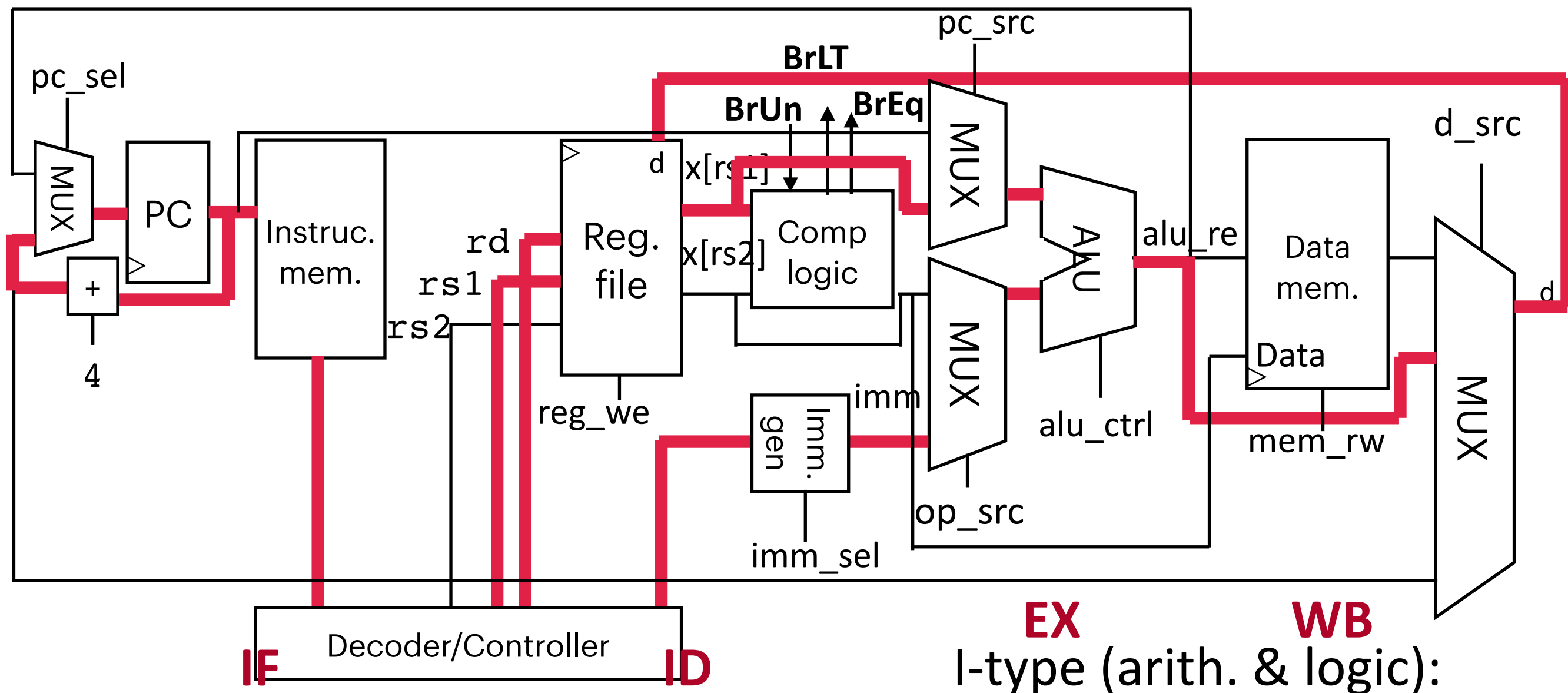
- What is the minimum clock cycle/max frequency of the CPU?



$$T \geq t_{clk-to-q} + t_{imem} + t_{dec} + \max(t_{reg}, t_{imm}) + t_{mux} + t_{alu} + t_{mux} + t_{setup}$$

Timing Analysis

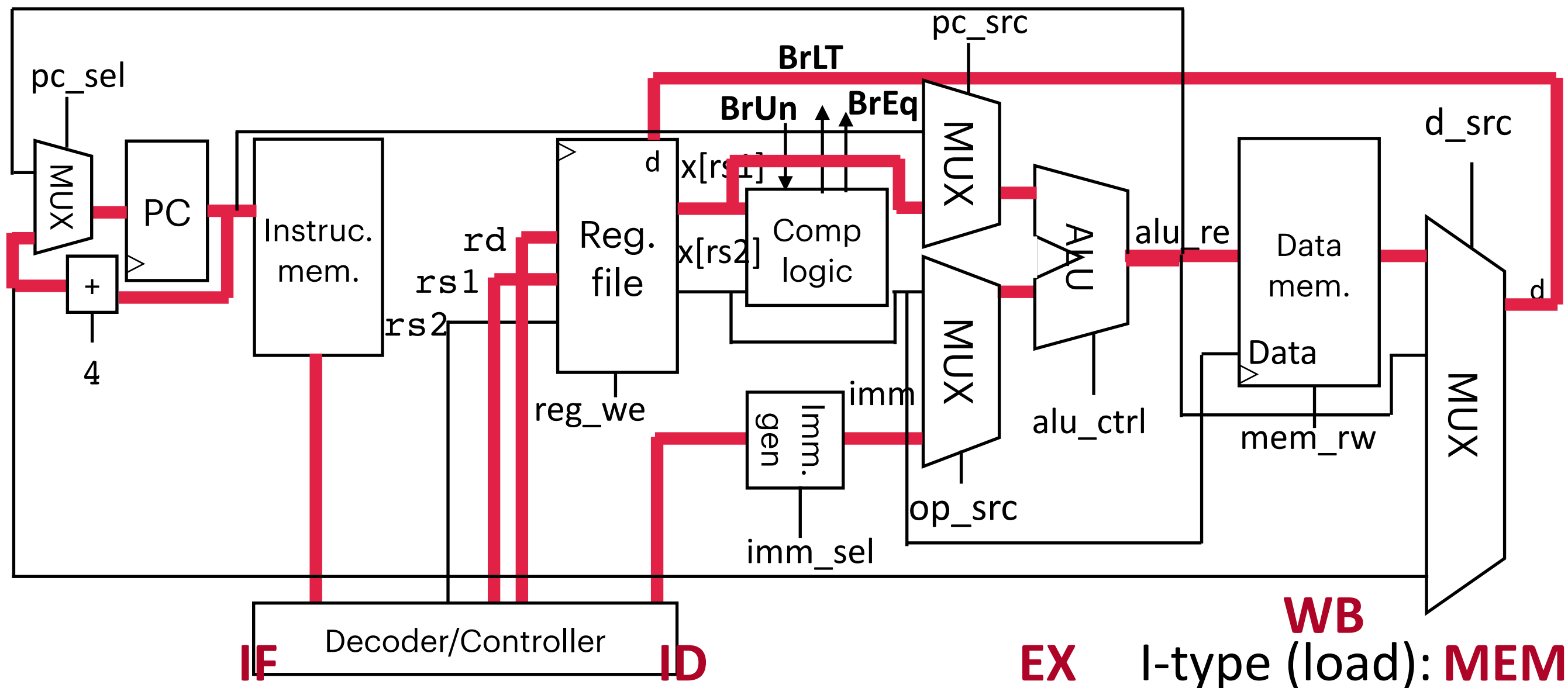
- What is the minimum clock cycle/max frequency of the CPU?



$$T \geq t_{clk-to-q} + t_{imem} + t_{dec} + \max(t_{reg}, t_{imm}) + t_{mux} + t_{alu} + t_{mux} + t_{setup} + t_{dmem}$$

Timing Analysis

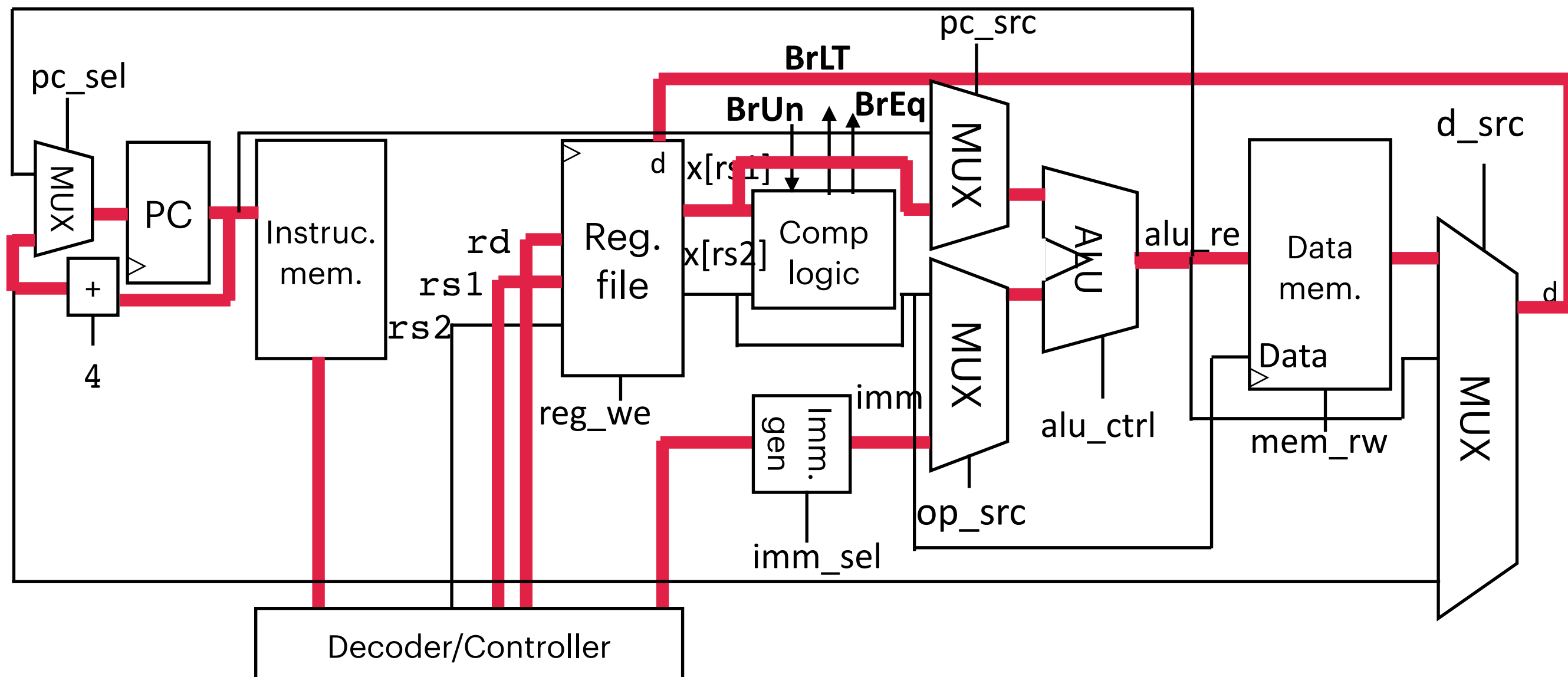
- What is the minimum clock cycle/max frequency of the CPU?



I-type (load): $T \geq t_{IF} + t_{ID} + t_{EXE} + t_{MEM} + t_{WB}$

Timing Analysis


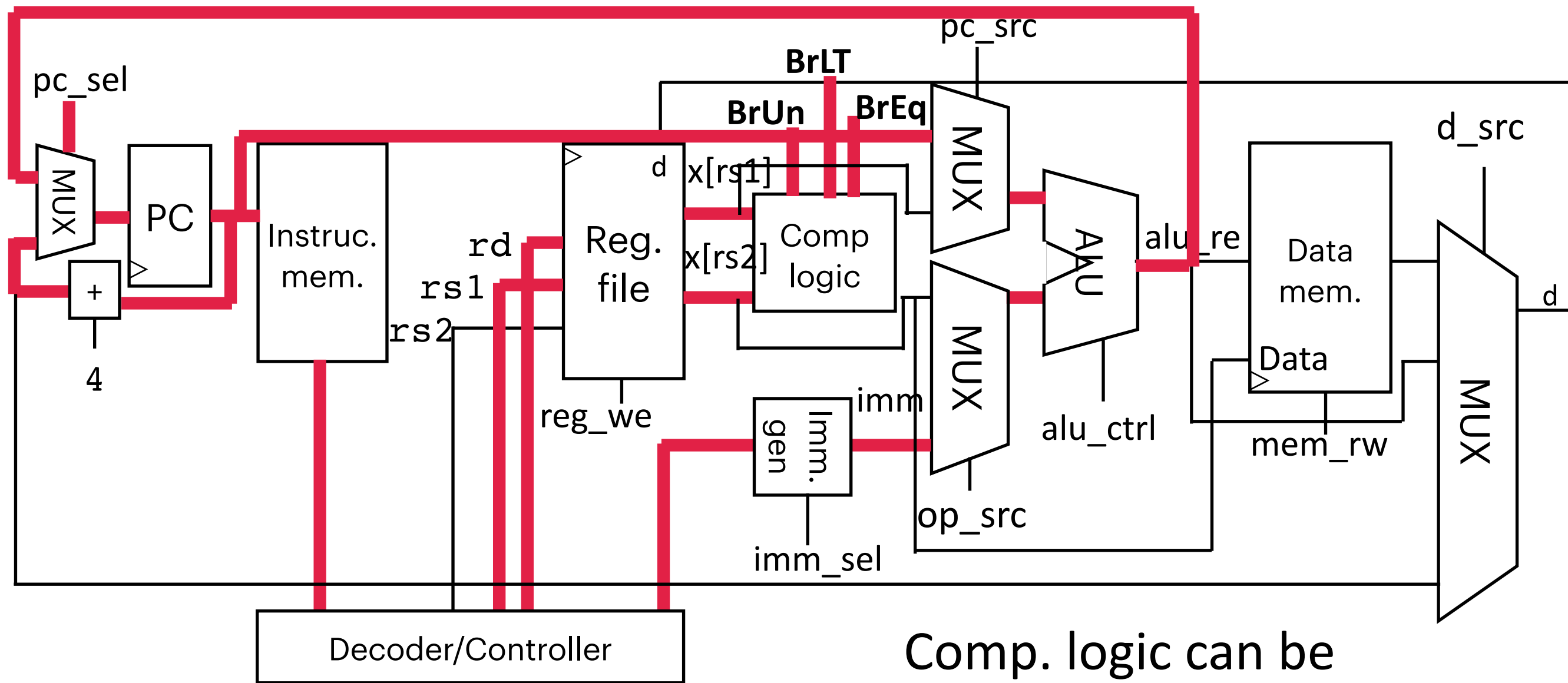
- What is the minimum clock cycle/max frequency of the CPU?



B-type: $T \geq t_{IF} + t_{ID} + t_{EXE}$


Comp. logic can be considered as part of *ID*

Timing Diagram (Consider delays)

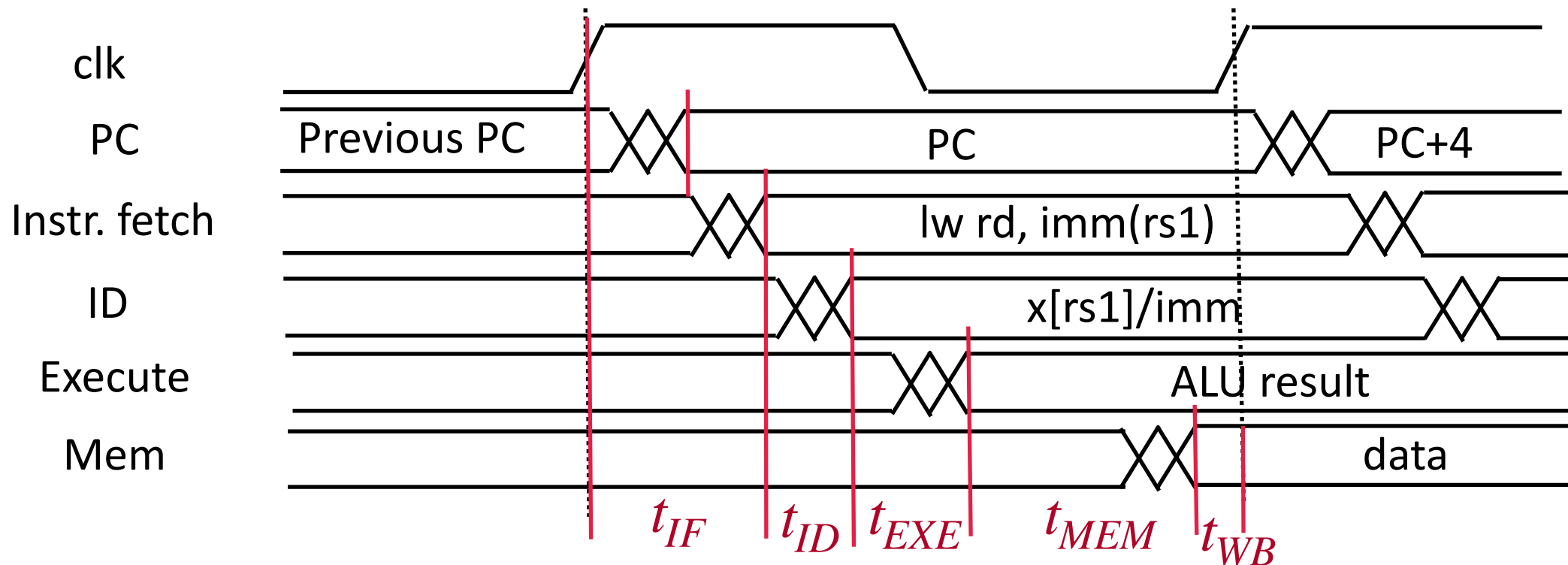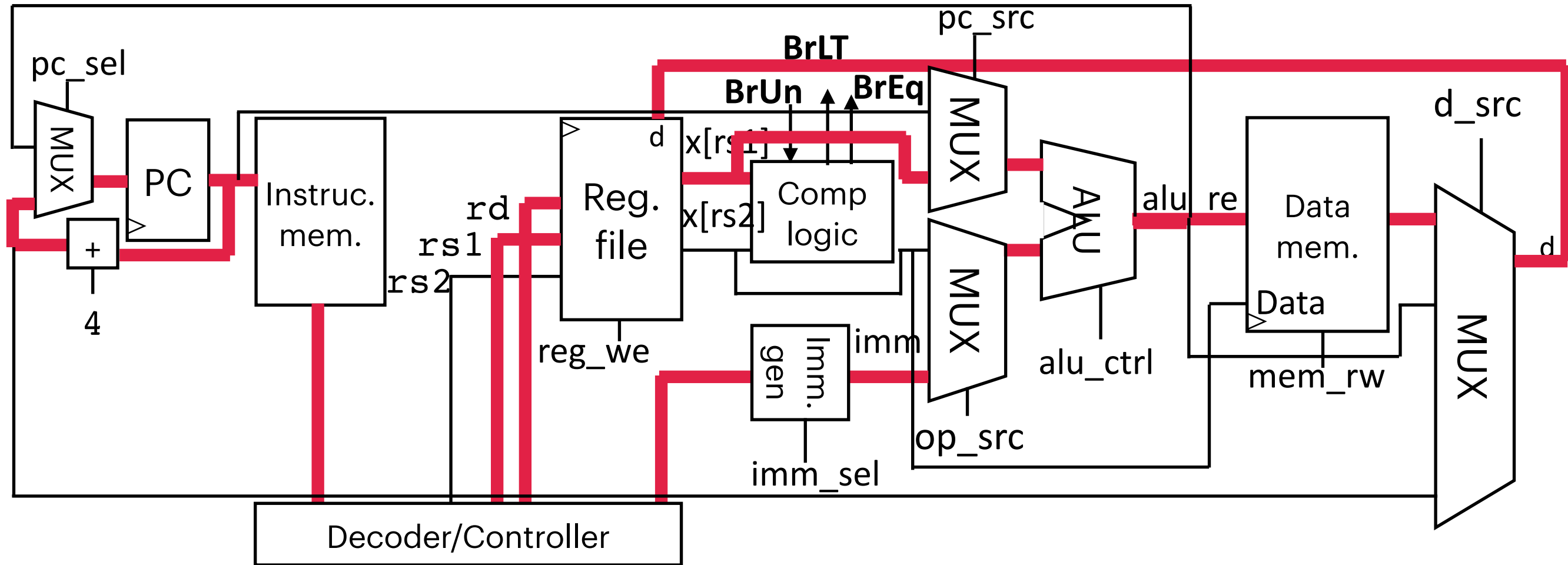


Timing Diagram (Consider delays)


Instru.	IF = 300 ps	ID = 100 ps	EX = 200 ps	MEM = 300 ps	WB = 100 ps	Total
add	X	X	X		X	700 ps
beq	X	X	X			600 ps
jal	X	X	X		X	700 ps
lw	X	X	X	X	X	1000 ps
sw	X	X	X	X		900 ps

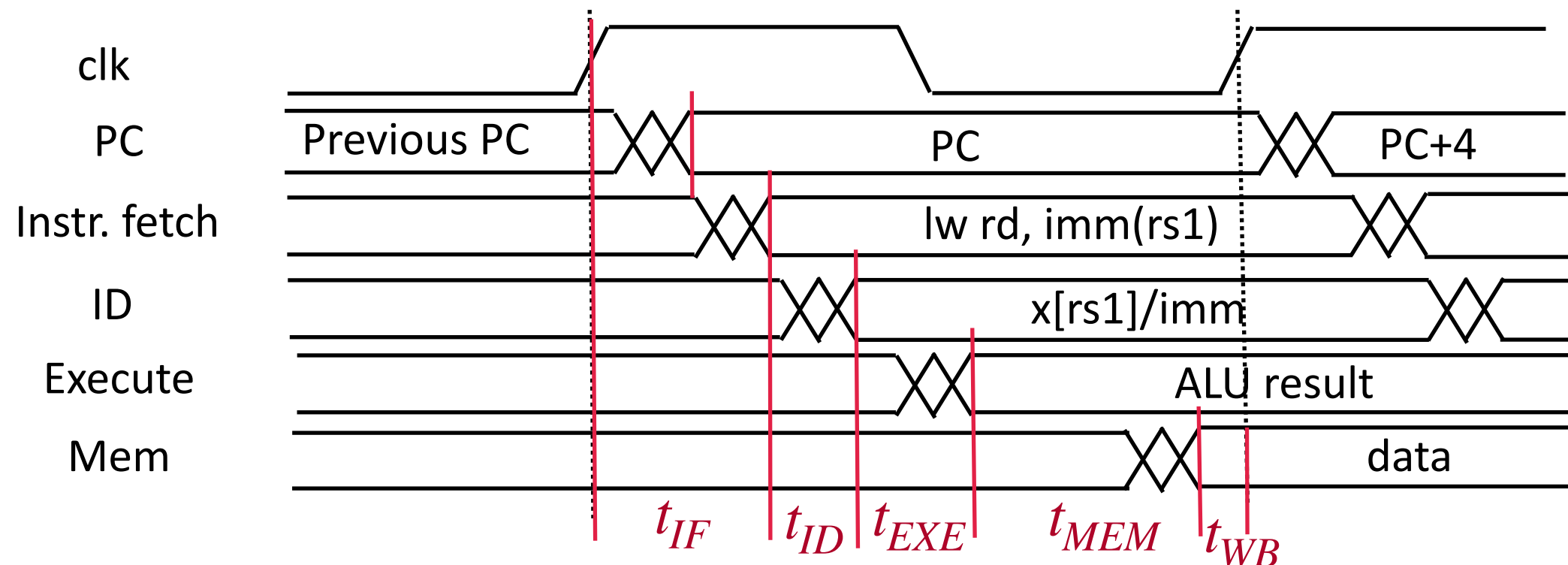

Up to Now

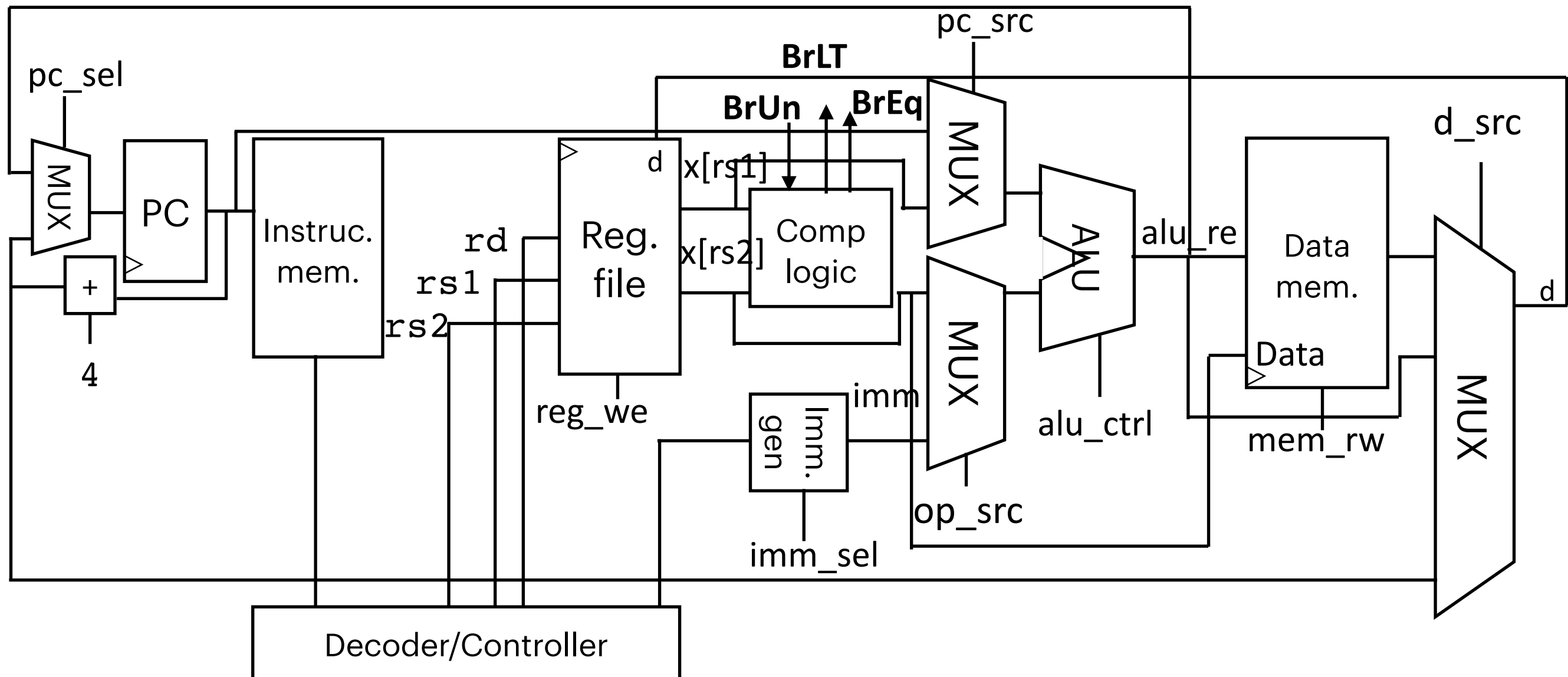

Controller: Two Implementations

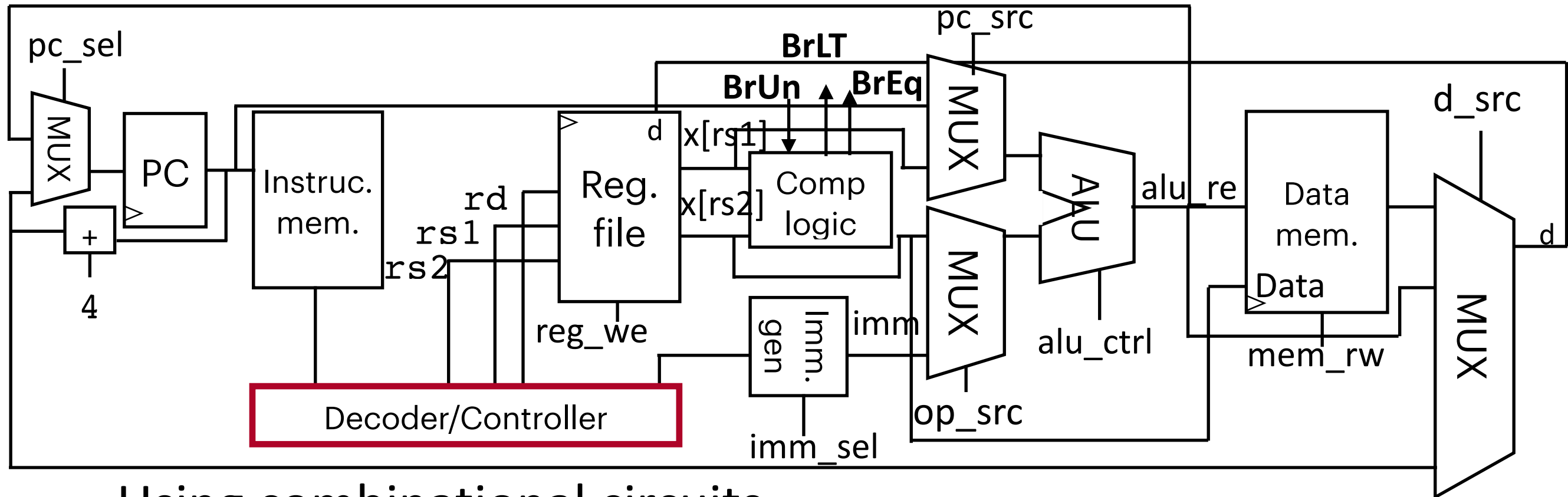

- Using combinational circuits

	addi	add	sw	lw	beq	jalr	jal
reg_we	1	1	0	1	0	1	1
mem_rw	R	R	W	R	R	R	R
alu_ctrl	add	add	add	add	add	add	add
imm_sel	I	*	S	I	B	I	J
d_src	alu	alu	*	mem	*	pc	pc
op_src	imm	reg	imm	imm	imm	imm	imm
pc_sel	+4	+4	+4	+4	Comp.	alu_re	alu_re
pc_src	reg	reg	reg	reg	pc	reg	pc
BrUn	*	*	*	*	w/w/o u	*	*

Combinational Control Logic

imm[31:12]				rd	011011	LUI
imm[31:12]				rd	001011	AUIPC
imm[20:10:11:19:12]				rd	110111	JAL
imm[11:0]				rd	110011	JALR
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	110001	BEQ
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	110001	BNE
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	110001	BLT
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	110001	BGE
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	110001	BLTU
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	110001	BGEU
imm[11:0]				rd	000001	LB
imm[11:0]				rd	000001	LH
imm[11:0]				rd	000001	LW
imm[11:0]				rd	000001	LBU
imm[11:0]				rd	000001	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	010001	SB
imm[11:5]	rs2	rs1	001	imm[4:0]	010001	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	010001	SW
imm[11:0]				rd	001001	ADDI
imm[11:0]				rd	001001	SLTI
imm[11:0]				rd	001001	SLTIU
imm[11:0]				rd	001001	XORI
imm[11:0]				rd	001001	ORI
imm[11:0]				rd	001001	ANDI

i[30]

i[14:12]

i[6:2]

00	00000		shamt	rs1	001	rd	0010011	SLLI
00	00000		shamt	rs1	101	rd	0010011	SRLI
01	00000		shamt	rs1	101	rd	0010011	SRAI
00	00000		rs2	rs1	000	rd	0110011	ADD
01	00000		rs2	rs1	000	rd	0110011	SUB
00	00000		rs2	rs1	001	rd	0110011	SLL
00	00000		rs2	rs1	010	rd	0110011	SLT
00	00000		rs2	rs1	011	rd	0110011	SLTU
00	00000		rs2	rs1	100	rd	0110011	XOR
00	00000		rs2	rs1	101	rd	0110011	SRL
01	00000		rs2	rs1	101	rd	0110011	SRA
00	00000		rs2	rs1	110	rd	0110011	OR
00	00000		rs2	rs1	111	rd	0110011	AND
0000	pred	succ	00000	000	00000	0001111	FENCE	
0000	0000	0000	00000	001	00000	0001111	FENCE.I	
000000000000			00000	000	00000	1110011	ECALL	
000000000001			00000	000	00000	1110011	EBREAK	
CSR			rs1	001	rd	1110011	CSR.W	
CSR			rs1	010	rd	1110011	CSR.RS	
CSR			rs1	011	rd	1110011	CSR.RC	
CSR			zimm	101	rd	1110011	CSR.WI	
CSR			zimm	110	rd	1110011	CSR.RSI	
CSR			zimm	111	rd	1110011	CSR.RCI	

Not in CS110

- Simplest example: BrUn

inst[14:12]				inst[6:2] = Branch		
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	110001	BEQ
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	110001	BNE
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	110001	BLT
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	110001	BGE
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	110001	BLTU
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	110001	BGEU

- How to decode/control whether BrUn is 1? BrUn = Inst [13] & Branch instruction
- Branch?


Using Types of Instructions

	addi	add	sw	lw	beq	jalr	jal
reg_we	1	1	0	1	0	1	1
mem_rw	R	R	W	R	R	R	R
alu_ctrl	add	add	add	add	add	add	add
imm_sel	I	*	S	I	B	I	J
d_src	alu	alu	*	mem	*	pc	pc
op_src	imm	reg	imm	imm	imm	imm	imm
pc_sel	+4	+4	+4	+4	Comp.	alu_re	alu_re
pc_src	reg	reg	reg	reg	pc	reg	pc
BrUn	*	*	*	*	w/w/o u	*	*

- Example:
 - mem_rw, 1 when “W”; 0 when “R”
 - Only “W” when S-type store

$$\text{mem_rw} = \text{SW} + \text{SH} + \text{SB}$$

Recall: S-Format Store Instructions

 

Assembly: `sw/sh/sb rs2, imm(rs1)`

imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	SB
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW

$$SB = \overline{i[14]} \overline{i[13]} \overline{i[12]} \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]}$$

$$SH = \overline{i[14]} \overline{i[13]} i[12] \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]}$$

$$SW = \overline{i[14]} i[13] \overline{i[12]} \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]}$$

Combinational Control Logic (Don't-care values)

	addi	add	sw	lw	beq	jalr	jal
reg_we	1	1	0	1	0	1	1
mem_rw	R	R	W	R	R	R	R
alu_ctrl	add	add	add	add	add	add	add
imm_sel	I	*	S	I	B	I	J
d_src	alu	alu	*	mem	*	pc	pc
op_src	imm	reg	imm	imm	imm	imm	imm
pc_sel	+4	+4	+4	+4	Comp.	alu_re	alu_re
pc_src	reg	reg	reg	reg	pc	reg	pc
BrUn	*	*	*	*	w/w/o u	*	*

Combinational Control Logic (Don't-care values)

- imm_sel as an example

0000000	rs2	rs1	000	rd	0110011	ADD
imm		rs1	000	rd	0010011	ADDI
imm		rs1	010	rd	0000011	LW
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW
imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
imm[20 10:1 11 19:12]				rd	1101111	JAL
imm		rs1	000	rd	1100111	JALR

- Assume (should be 3-bit, because we still have U-type imm.)

	addi	add	sw	lw	beq	jalr	jal
imm_sel	I	*	S	I	B	I	J
	00	—	01	00	10	00	11

Combinational Control Logic (Don't-care values)

- imm_sel as an example

000	01100
000	00100
010	00000
010	01000
000	11000
*	11011
000	11001

Funct3 (instru[14:12]) instru[6:2]

	imm_sel
ADD	*
ADDI	00
LW	00
SW	01
BEQ	10
JAL	11
JALR	00

Can be
00, 01,
10, 11

$$\begin{aligned}
 \text{imm_sel}[1] = & i[6] i[5] \overline{i[4]} i[3] i[2] + i[6] i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]} i[14] i[13] i[12] \\
 & + \overline{i[6]} i[5] i[4] \overline{i[3]} \overline{i[2]} i[14] i[13] i[12]
 \end{aligned}$$

ROM-based Implementation

imm[31:12]				rd	011011	LUI
imm[31:12]				rd	001011	AUIPC
imm[20:10:11:19:12]				rd	110111	JAL
imm[11:0]				rd	110011	JALR
imm[12:10:5]	rs2	rs1	000	imm[4:1:11]	110001	BEQ
imm[12:10:5]	rs2	rs1	001	imm[4:1:11]	110001	BNE
imm[12:10:5]	rs2	rs1	100	imm[4:1:11]	110001	BLT
imm[12:10:5]	rs2	rs1	101	imm[4:1:11]	110001	BGE
imm[12:10:5]	rs2	rs1	110	imm[4:1:11]	110001	BLTU
imm[12:10:5]	rs2	rs1	111	imm[4:1:11]	110001	BGEU
imm[11:0]				rd	000001	LB
imm[11:0]				rd	000001	LH
imm[11:0]				rd	000001	LW
imm[11:0]				rd	000001	LBU
imm[11:0]				rd	000001	LHU
imm[11:5]	rs2	rs1	000	imm[4:0]	010001	SB
imm[11:5]	rs2	rs1	001	imm[4:0]	010001	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	010001	SW
imm[11:0]				rd	001001	ADDI
imm[11:0]				rd	001001	SLTI
imm[11:0]				rd	001001	SLTIU
imm[11:0]				rd	001001	XORI
imm[11:0]				rd	001001	ORI
imm[11:0]				rd	001001	ANDI

00000000	shamt	rs1	001	rd	001001	SLLI
00000000	shamt	rs1	101	rd	001001	SRLI
01000000	shamt	rs1	101	rd	001001	SRAI
00000000	rs2	rs1	000	rd	011001	ADD
01000000	rs2	rs1	000	rd	011001	SUB
00000000	rs2	rs1	001	rd	011001	SLL
00000000	rs2	rs1	010	rd	011001	SLT
00000000	rs2	rs1	011	rd	011001	SLTU
00000000	rs2	rs1	100	rd	011001	XOR
00000000	rs2	rs1	101	rd	011001	SRL
01000000	rs2	rs1	101	rd	011001	SRA
00000000	rs2	rs1	110	rd	011001	OR
00000000	rs2	rs1	111	rd	011001	AND


0000	pred	succ	00000	000	00000	0001111	FENCE
0000	0000	0000	00000	001	00000	0001111	FENCE.I
00000000000000			00000	000	00000	1110011	ECALL
00000000000001			00000	000	00000	1110011	EBREAK
CSR			rs1	001	rd	1110011	CSR.W
CSR			rs1	010	rd	1110011	CSR.RS
CSR			rs1	011	rd	1110011	CSR.RC
CSR			zimm	101	rd	1110011	CSR.WI
CSR			zimm	110	rd	1110011	CSR.RSI
CSR			zimm	111	rd	1110011	CSR.RCI

Not in CS110


Not in CS110

- Read-only memory (ROM)
 - Similar to RAM, given address, the contents are accessed
 - Use 11 bits as address
 - Can be reprogrammed by replacing the stored value (add instructions)

Control Block Design

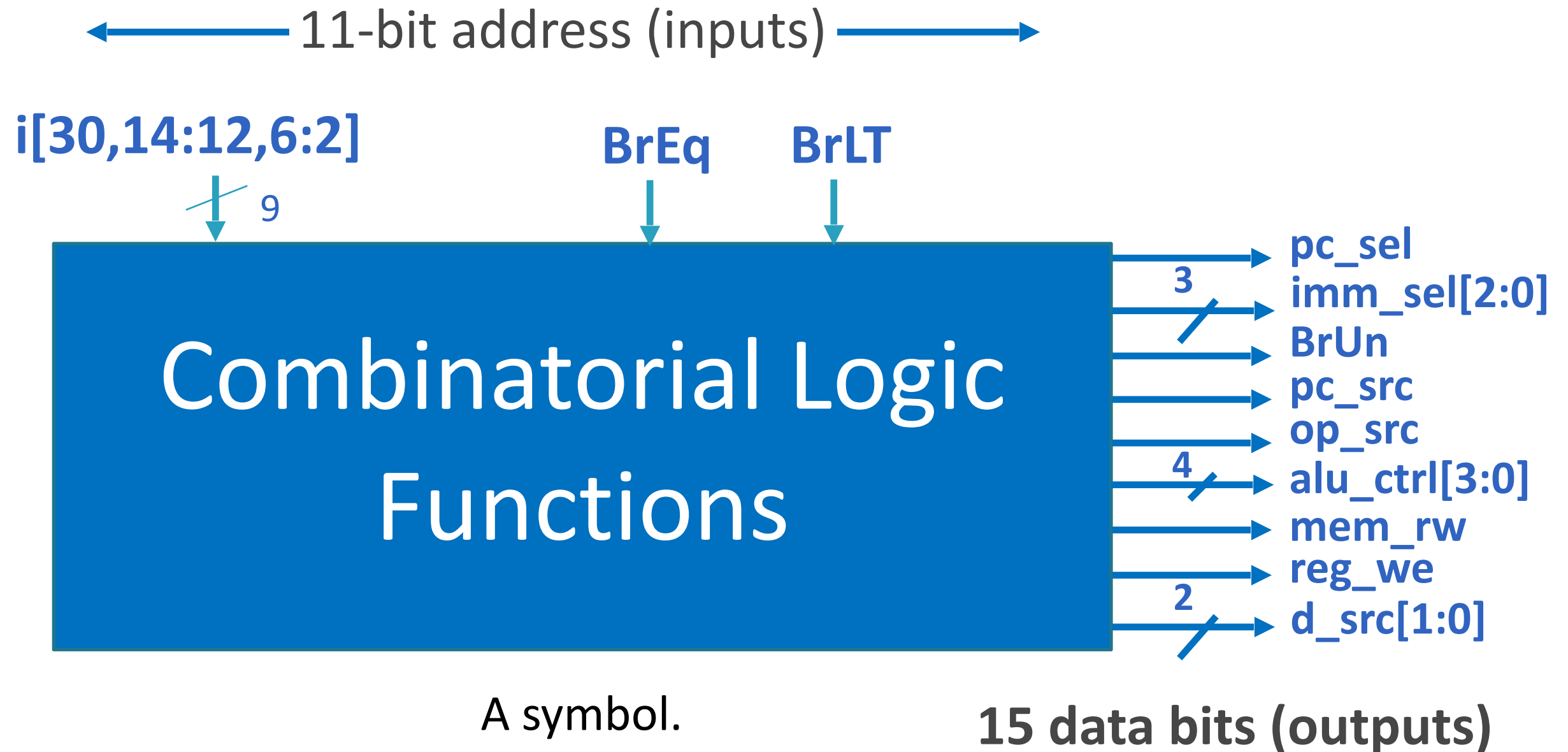

ROM Controller Implementation

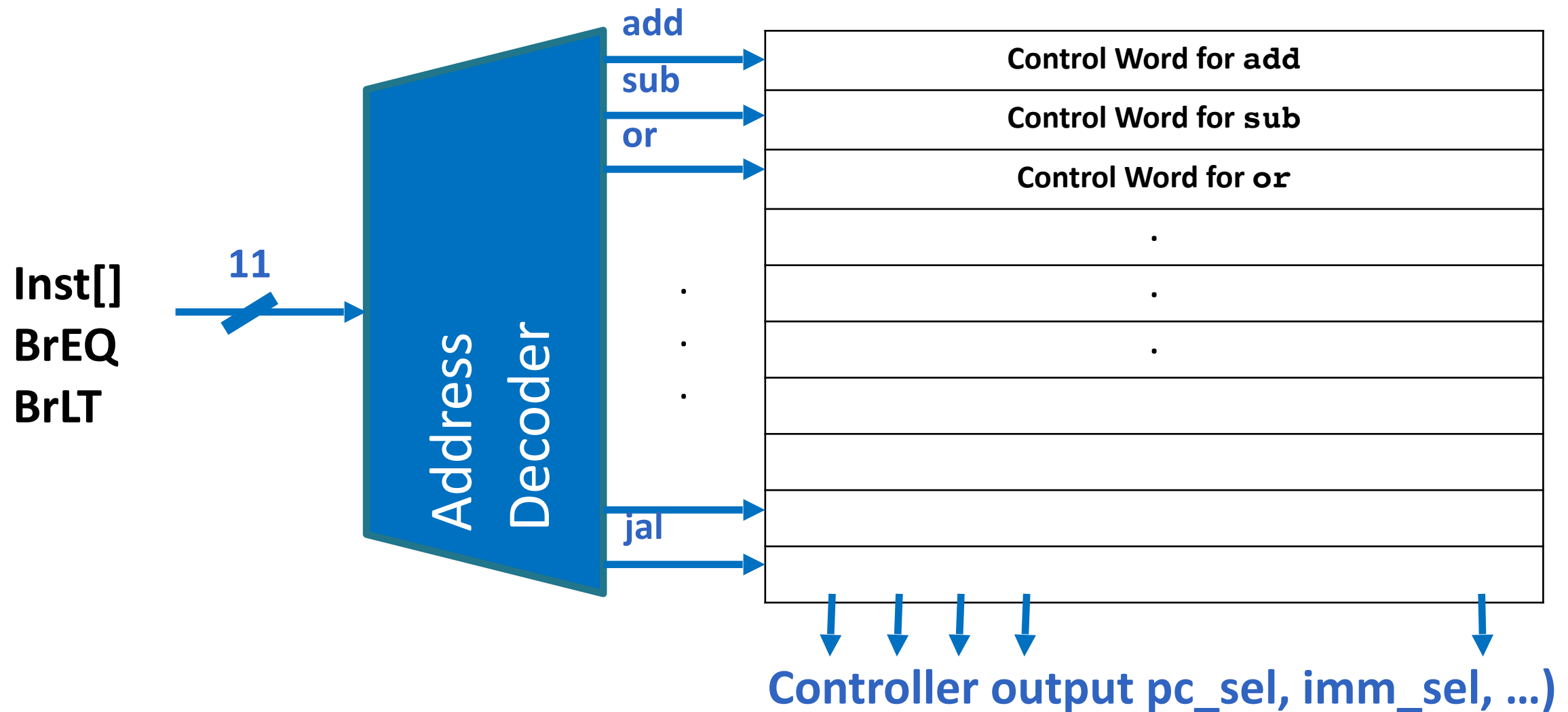

Extra Consideration for Expansion

imm[11:5]	rs2	rs1	funct3	imm[4:0]	opcode	S-type
7	5	5	3	5	7	

Assembly: `sw/sh/sb rs2, imm(rs1)`

imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	SB
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	SH
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	SW

$$SB = \overline{i[14]} \overline{i[13]} \overline{i[12]} \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]} i[1] i[0]$$

$$SH = \overline{i[14]} \overline{i[13]} i[12] \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]} i[1] i[0]$$

$$SW = \overline{i[14]} i[13] \overline{i[12]} \overline{i[6]} i[5] \overline{i[4]} \overline{i[3]} \overline{i[2]} i[1] i[0]$$

RV32I

Finally



```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

Anything can be represented
as a *number*,
i.e., data or instructions

```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```

ISA

High Level Language
Program (e.g., C)

Compiler

Assembly Language
Program (e.g., RISC-V)

Assembler


Machine Language
Program (RISC-V)

*Machine
Interpretation*

Hardware Architecture Description
(e.g., block diagrams)

*Architecture
Implementation*

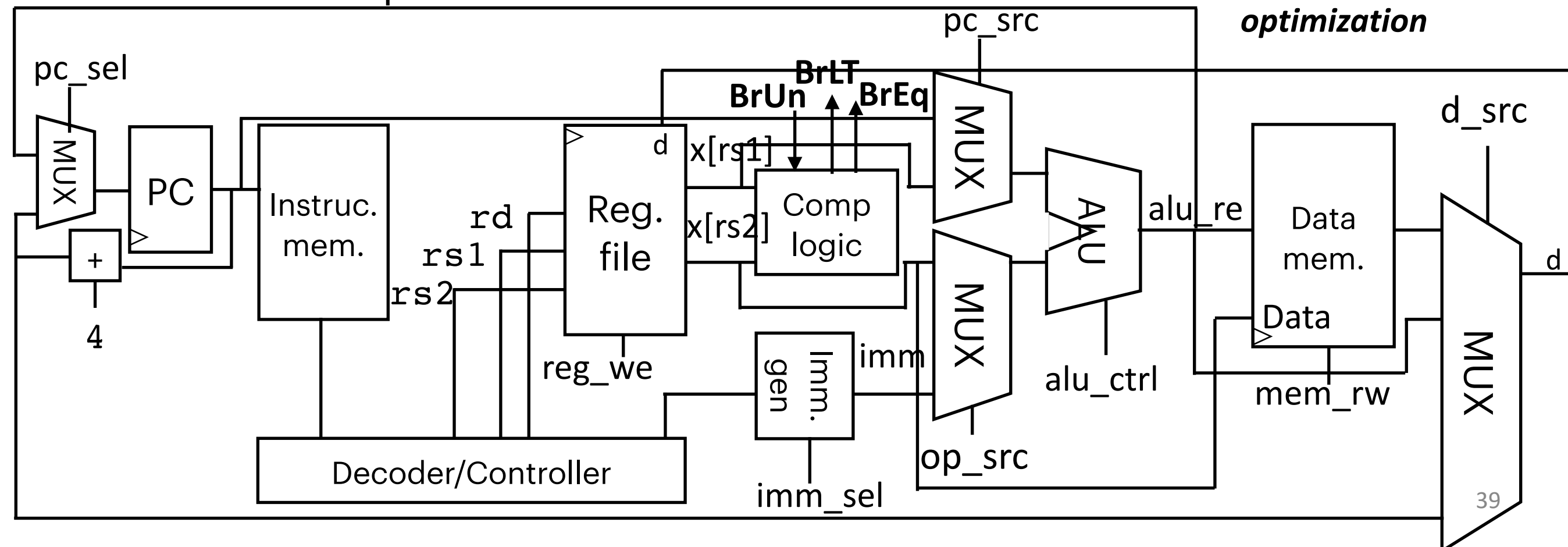**Single-core simple
CPU w/o any
optimization**




Summary

- We have built a processor!
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
 - Critical path changes
- 5 Phases of execution
 - IF, ID, EX, MEM, WB
 - Not all instructions are active in all phases
- Controller specifies how to execute instructions
 - Implemented as ROM or logic

Bottleneck

Instru.	IF = 300 ps	ID = 100 ps	EX = 200 ps	MEM = 300 ps	WB = 100 ps	Total
add	X	X	X		X	700 ps
beq	X	X	X			600 ps
jal	X	X	X		X	700 ps
lw	X	X	X	X	X	1000 ps
sw	X	X	X	X		900 ps

 

Great Ideas in Computer Architecture

- Abstraction (Layers of Representation / Interpretation)
- Moore's Law
- Principle of Locality/Memory Hierarchy
- Parallelism
- Performance Measurement and Improvement
- Dependability via Redundancy

“Iron Law” of Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}}$$

$$\frac{\text{Instructions}}{\text{Program}}$$

RISC vs. CISC

- ISA-relevant
- Compiler
- What task, complexity
- Etc.

“Iron Law” of Processor Performance

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}}$$

$$\frac{\text{Cycles}}{\text{Instruction}}$$


- Microarchitecture implementation or circuit design
- ISA

Timing Diagram (Consider delays)

Instru.	IF = 300 ps	ID = 100 ps	EX = 200 ps	MEM = 300 ps	WB = 100 ps	Total
lw	X	X	X	X	X	1000 ps

$\frac{\text{Cycles}}{\text{Instruction}}$ (CPI)

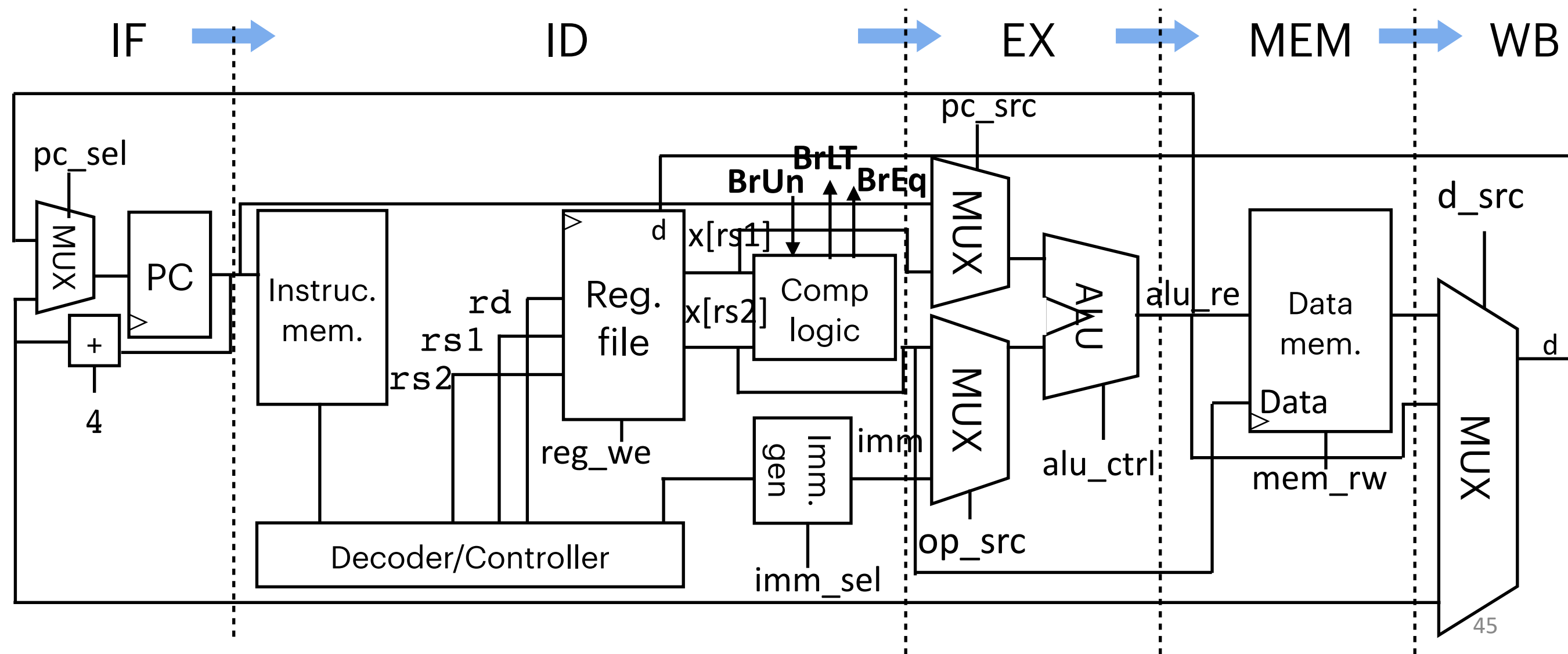
$\frac{\text{Time}}{\text{Cycle}}$ (Critical path; technology; TPD etc.)



Timing Diagram (Consider delays)

Instru.	IF = 300 ps	ID = 100 ps	EX = 200 ps	MEM = 300 ps	WB = 100 ps	Total
lw	X	X	X	X	X	1000 ps
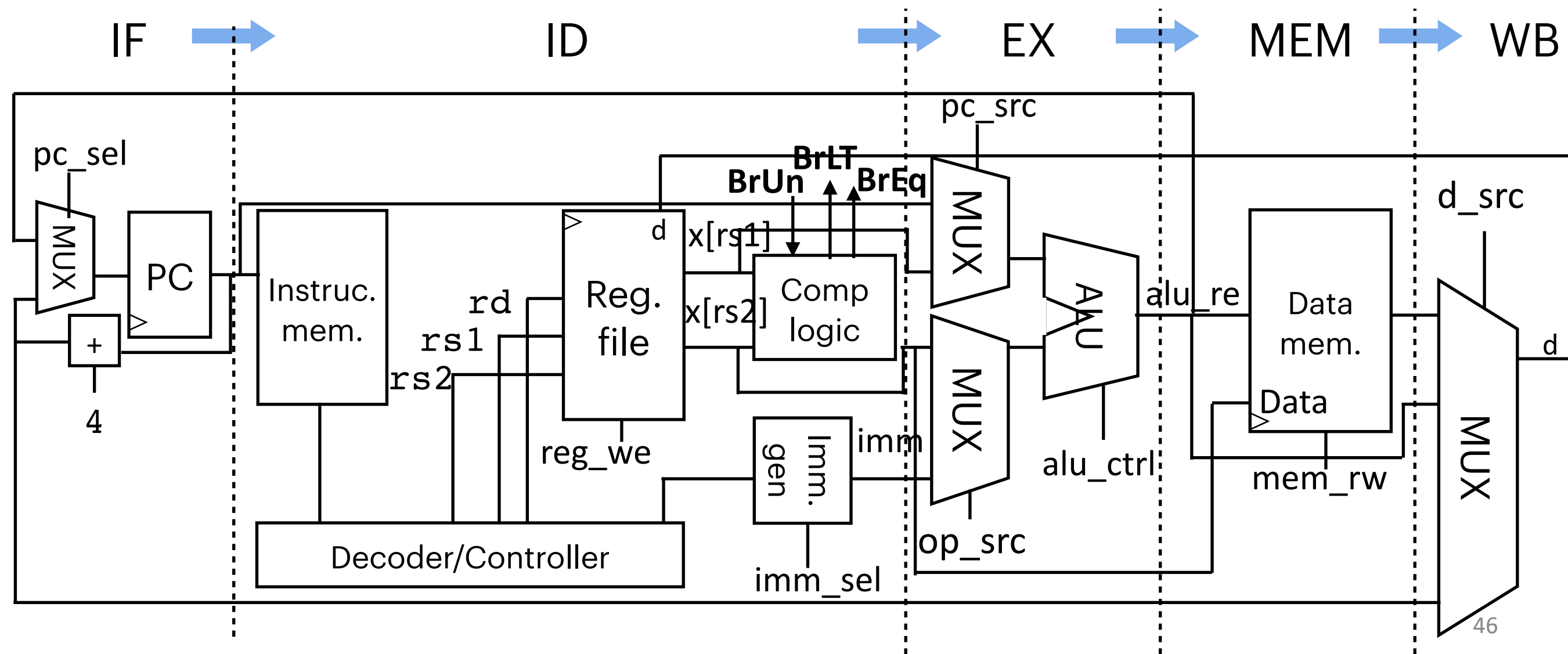
$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}}$$



Pipeline: Improve Time/Program

- Instruction: PCR test: 1. scan QR code; 2. get the tube; 3. sample
- 5 seconds for each step:
- Single-cycle (once for all)



$$\frac{\textit{Time}}{\textit{Program}} = \frac{\textit{Instructions}}{\textit{Program}} \times \frac{\textit{Clock cycles}}{\textit{Instruction}} \times \frac{\textit{Time}}{\textit{Clock cycle}}.$$

Multi-cycle


- Instruction: PCR test: 1. scan QR code; 2. get the tube; 3. sample
- 5 seconds for each step
- Multi-cycle or multi-step



$$\frac{\textit{Time}}{\textit{Program}} = \frac{\textit{Instructions}}{\textit{Program}} \times \frac{\textit{Clock cycles}}{\textit{Instruction}} \times \frac{\textit{Time}}{\textit{Clock cycle}}.$$


Pipeline

- PCR test in pipeline

 


$$\frac{\textit{Time}}{\textit{Program}} = \frac{\textit{Instructions}}{\textit{Program}} \times \frac{\textit{Clock cycles}}{\textit{Instruction}} \times \frac{\textit{Time}}{\textit{Clock cycle}}.$$

Analogy in our CPU Design


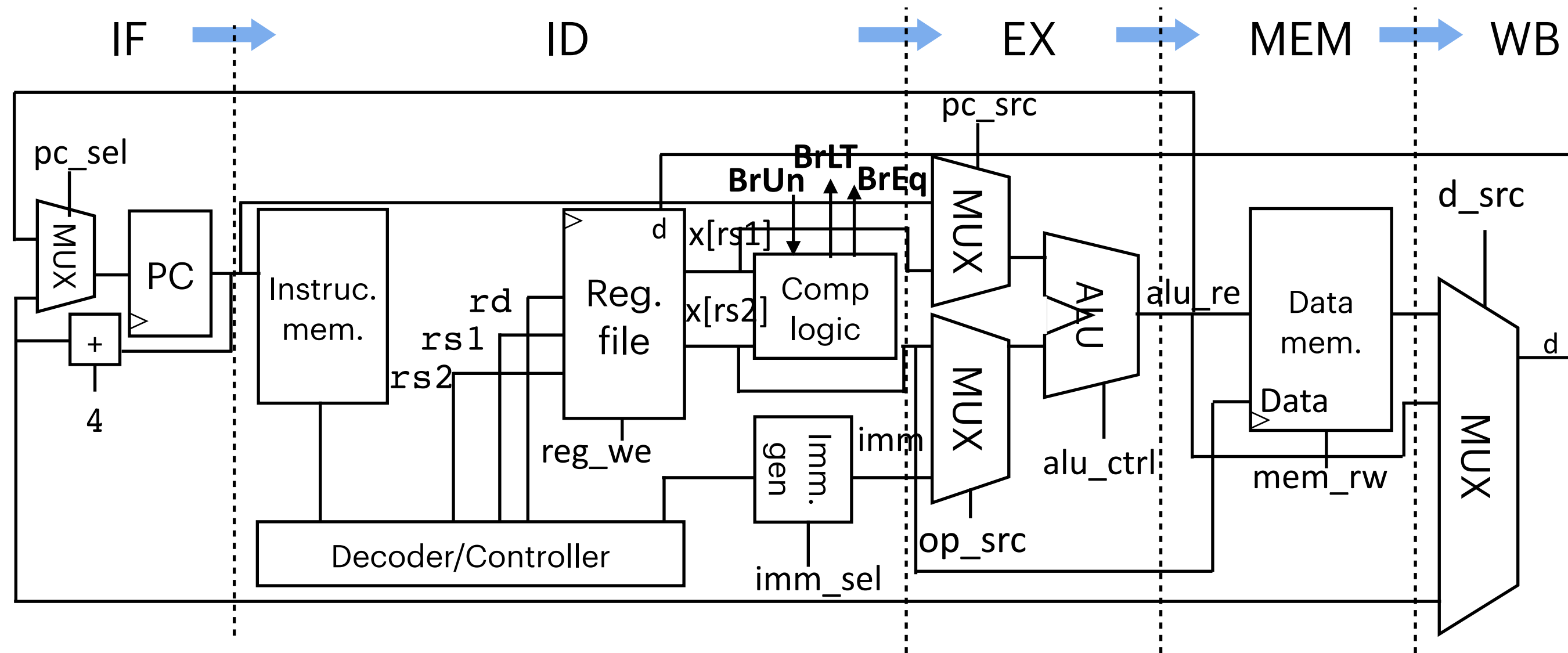


$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Clock cycles}}{\text{Instruction}} \times \frac{\text{Time}}{\text{Clock cycle}}.$$


Simplify the Model

 

Recall DFFs

  

Simplify the Model

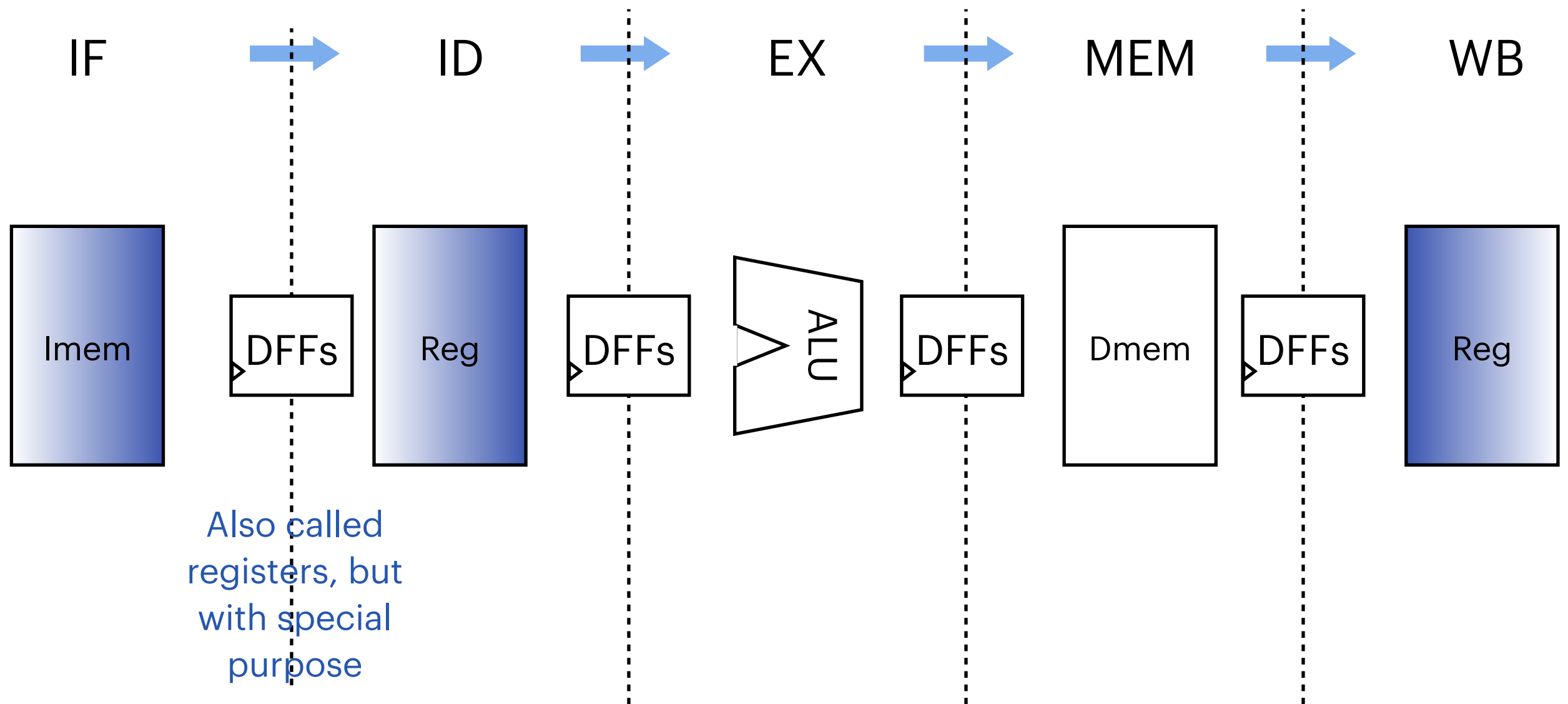

$$\frac{\text{Time}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Cycles}}{\text{Instruction}} \cdot \frac{\text{Time}}{\text{Cycle}}$$